
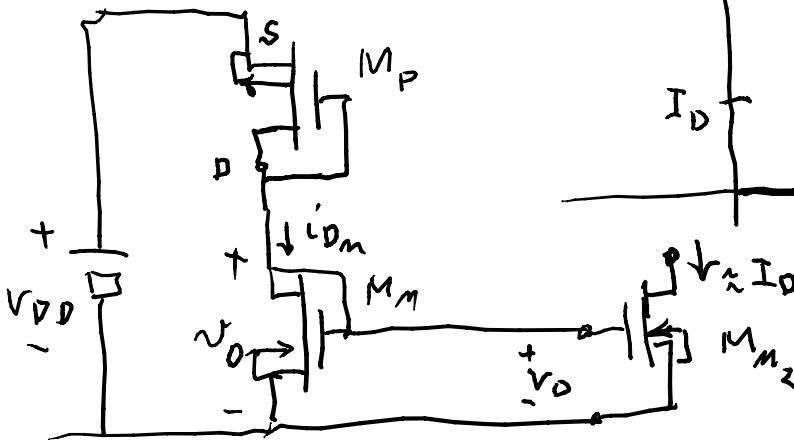
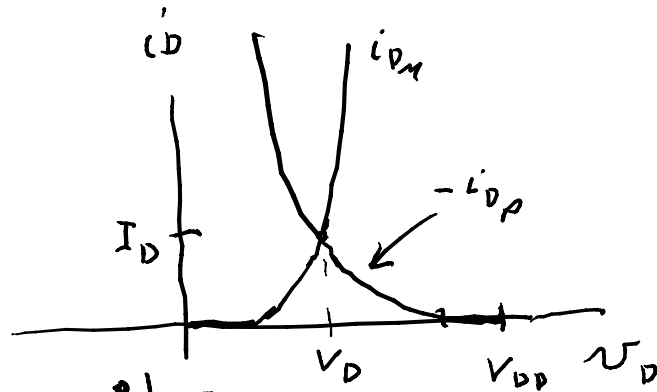
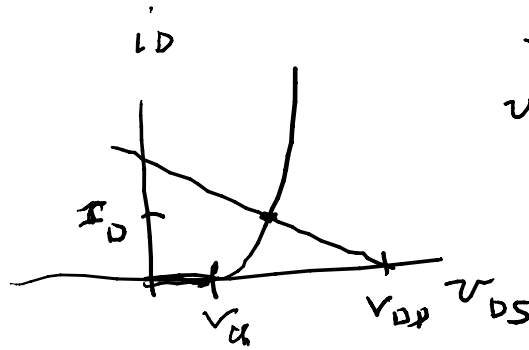
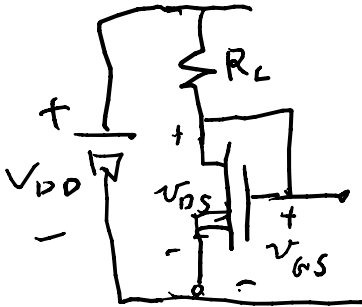


# How to make a MOS capacitor

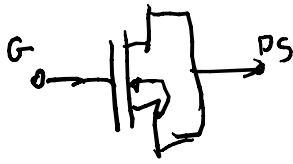

How to design for a given  $I_D$  (ignore  $\lambda$ ,  $\lambda=0$ )

$$I_{Dn} = \frac{K_{Pn}}{2} \frac{W_n}{L_n} (V_{GS} - V_{TO_n})^2 \quad V_{GS} = V_D$$


$$-I_{Dp} = I_{Sp} = \frac{K_{Pp}}{2} \frac{W_p}{L_p} (V_{DD} - V_D - |V_{TO_p}|)^2 \quad \text{assume } V_{TO_n} = -V_{TO_p}$$

$$\therefore (V_D - V_{TO_n})^2 = \frac{I_D}{\frac{K_{Pn}}{2} \frac{W_n}{L_n}} \Rightarrow V_D = V_{TO_n} + \sqrt{\frac{I_D}{\frac{K_{Pn}}{2} \frac{W_n}{L_n}}}$$


drop as turn on  $M_n$

$$M_p \Rightarrow V_{DD} - V_D - V_{TO_p} = \sqrt{\frac{I_D}{\frac{K_{Pp}}{2} \frac{W_p}{L_p}}} \Rightarrow V_{DD} - V_{TO_n} - \sqrt{\frac{I_D}{\frac{K_{Pn}}{2} \frac{W_n}{L_n}}} - |V_{TO_p}| = \sqrt{\frac{I_D}{\frac{K_{Pp}}{2} \frac{W_p}{L_p}}}$$

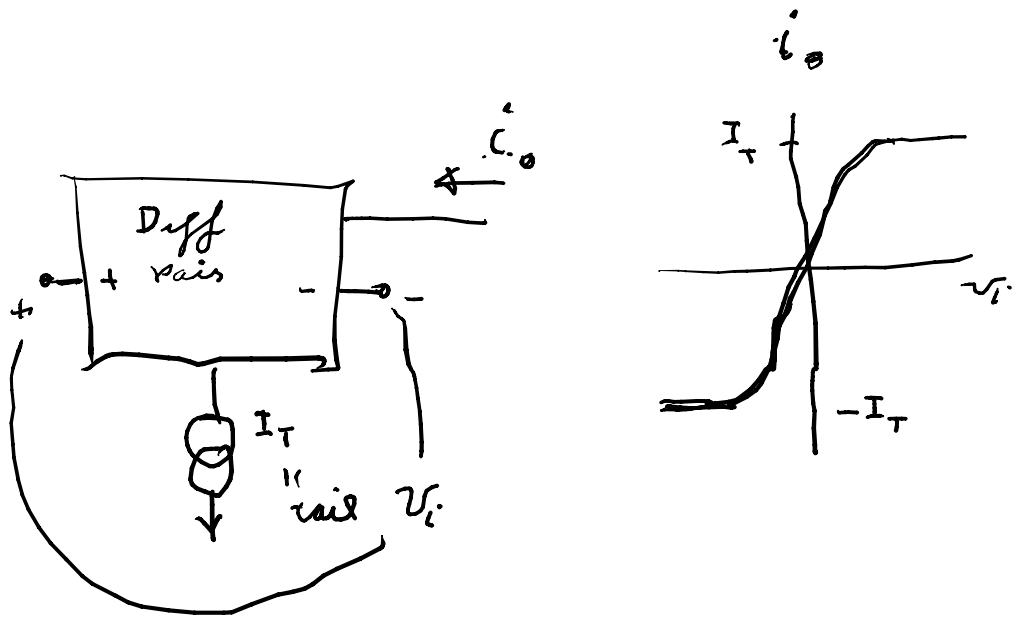can solve for  $\left(\frac{W}{L}\right)_p \rightarrow \left(\frac{W}{L}\right)_n$  to give  $I_D$



MOS differential pair

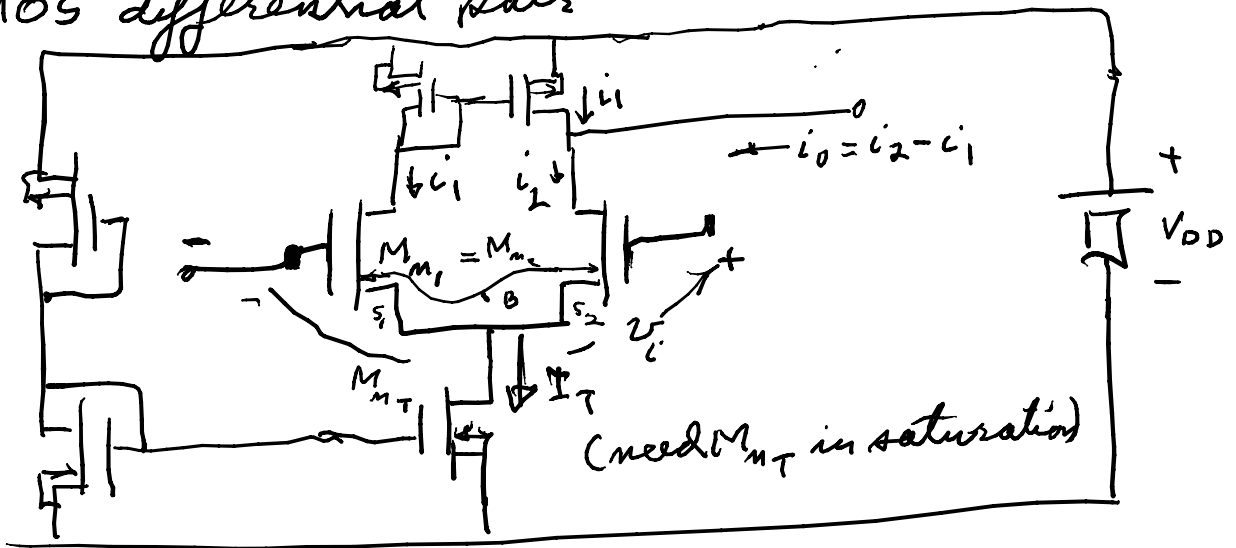

$$\begin{aligned} i_1 + i_2 &= I_T & 2i_2 &= I_T + i_o \\ i_2 - i_1 &= i_o & 2i_1 &= I_T - i_o \end{aligned}$$

$$i_1 = I_D = \frac{k_p W}{2 L} (V_{GS} - V_{th})_{M_{n1}}^2, \quad i_2 = I_D = \frac{k_p W}{2 L} (V_{GS} - V_{th})_{M_{n2}}^2$$

$$v_{L^+} = V_{GS_2} - V_{GS_1} = V_{th_{M_{n1}}} + \sqrt{\frac{i_2}{\frac{k_p W}{2 L}}} - \left( V_{th_{M_{n1}}} + \sqrt{\frac{i_1}{\frac{k_p W}{2 L}}} \right)$$

$$v_i = \sqrt{\frac{i_2}{\frac{k_p W}{2 L}}} - \sqrt{\frac{i_1}{\frac{k_p W}{2 L}}} \Rightarrow v_i^2 = \frac{i_2}{\frac{k_p W}{2 L}} + \frac{i_1}{\frac{k_p W}{2 L}} - 2 \frac{\sqrt{i_1 i_2}}{\frac{k_p W}{2 L}}$$

$$\frac{KPV}{2L} \cdot v_i^2 = i_1 + i_2 - 2\sqrt{i_1 i_2} = I_T - 2\sqrt{i_1(i_0 + i_1)} = I_T - 2\sqrt{i_1 i_2}$$

$$a v_i^2, \quad a = \frac{KPV}{2L} \quad \left( \frac{a v_i^2 - I_T}{2} \right)^2 = \frac{(I_T - i_0) \cdot (I_T + i_0)}{2 \cdot 2}$$

$$= \frac{1}{4} (I_T^2 - i_0^2)$$

$$\Rightarrow i_0^2 = I_T^2 - (a^2 v_i^4 - 2I_T a v_i^2 + I_T^2)$$

$$\Rightarrow i_0 = \pm \sqrt{2I_T a} v_i \sqrt{1 - \frac{a v_i^2}{2I_T}}$$

(use + for given solubility)

$$\text{max at } \frac{a v_i^2}{I_T} = 1$$

$$\Rightarrow v_i = \pm \sqrt{I_T/a}$$

$$\Rightarrow i_{0 \max} = + \sqrt{2I_T a} \cdot \sqrt{\frac{I_T}{2a}} = I_T$$