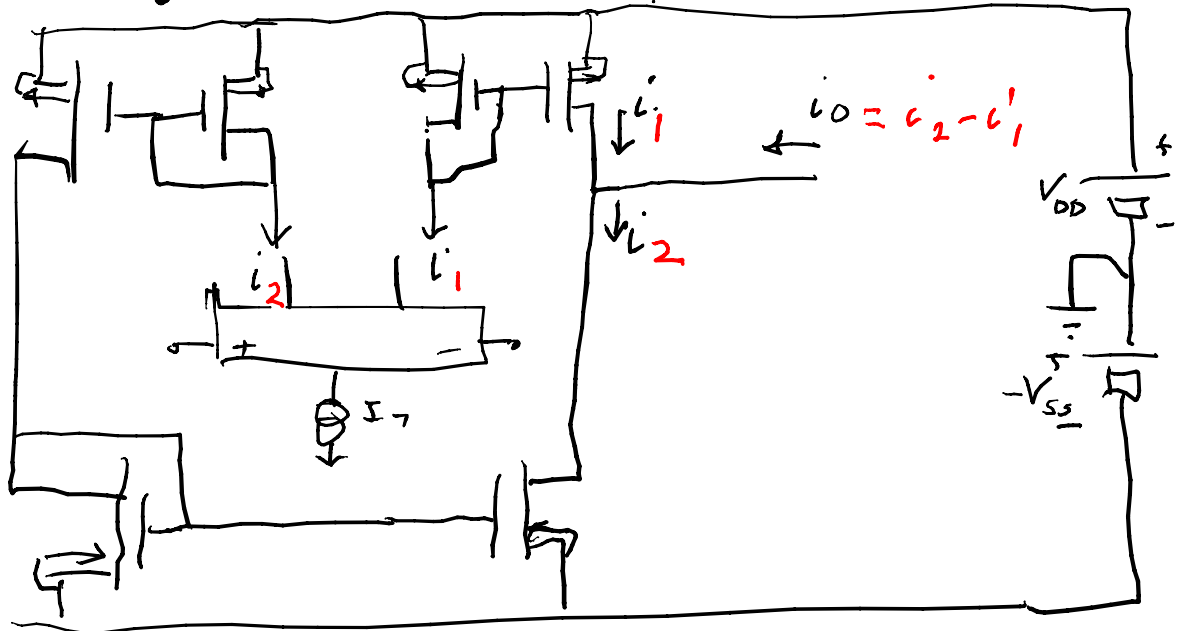


$$i_o = \begin{cases} I_T & v_i > \sqrt{I_T/a} \\ \sqrt{2I_T a} v_i \sqrt{1 - \frac{a v_i^2}{2I_T}} & -\sqrt{I_T/a} \leq v_i \leq +\sqrt{I_T/a} \\ -I_T & v_i \leq -\sqrt{I_T/a} \end{cases} \quad a = \frac{K_P W}{2 L}$$


$$\frac{d i_o}{d v_i} = G_m = \sqrt{2I_T a} \cdot \sqrt{1 - \frac{a v_i^2}{2I_T}} + \sqrt{2I_T a} v_i \frac{1 \times (-2a v_i / 2I_T)}{\sqrt{1 - \frac{a v_i^2}{2I_T}}}$$


@  $v_i = 0$ , slope near origin  $\Rightarrow \sqrt{2I_T a} = G_m @ v_i = 0$

VCCS = voltage controlled current source




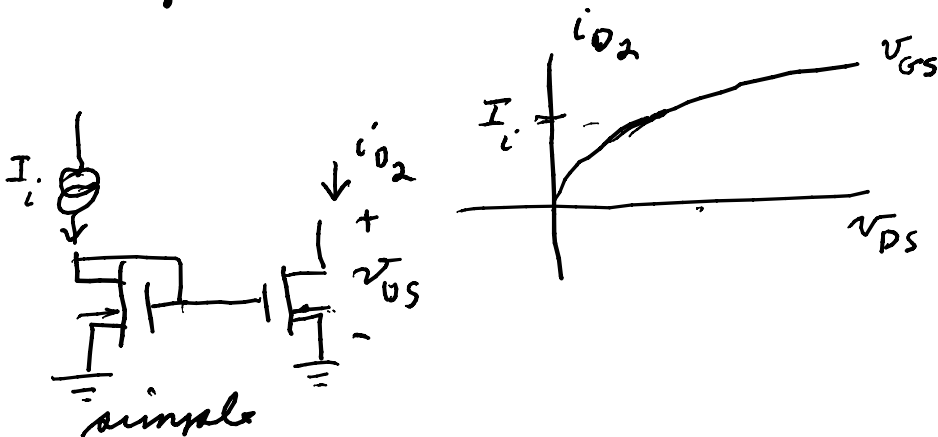improved current mirror  $\Rightarrow$  use cascode connection




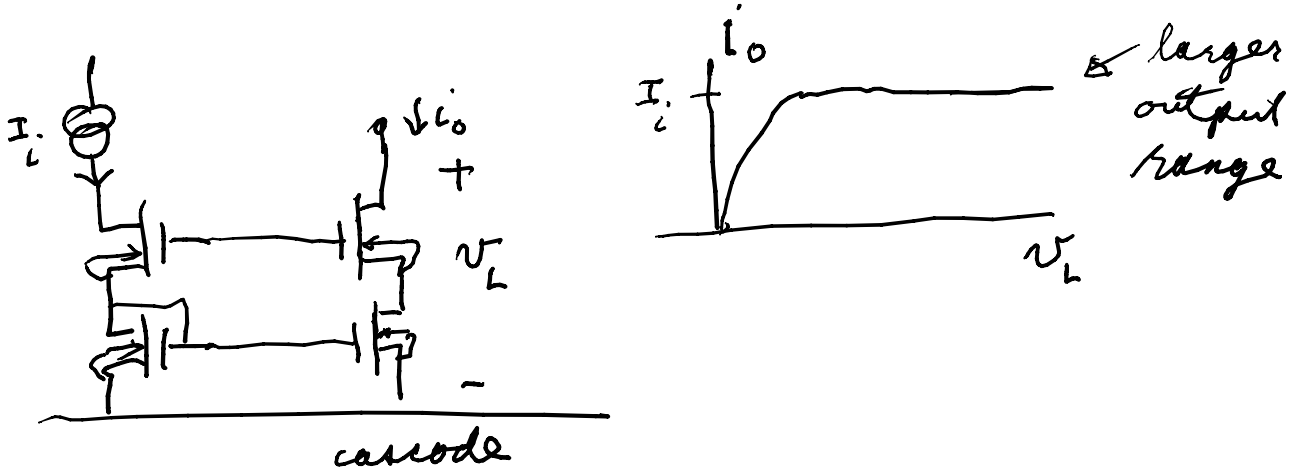

BJT diff pair

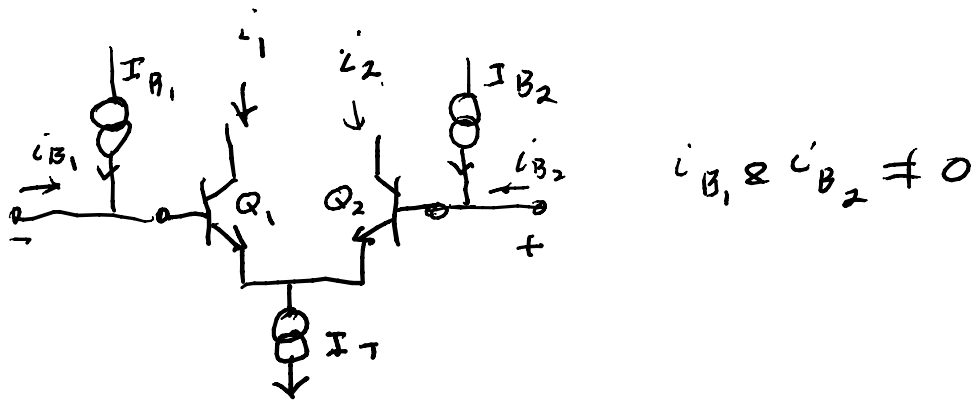

Use Darlington pair for  $Q_1$  &  $Q_2$

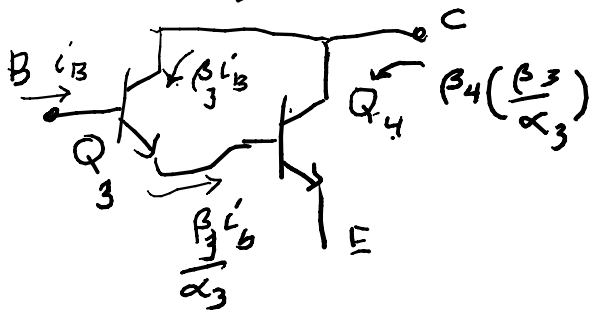


$$I_C = \beta_3 I_B + \beta_4 \frac{\beta_3}{\alpha_3} I_B$$

$$\approx \beta_3 \beta_4 I_B$$

$$I_o = I_T \tanh\left(\frac{V_i}{2V_T}\right)$$

Here still get for BJT diff pair

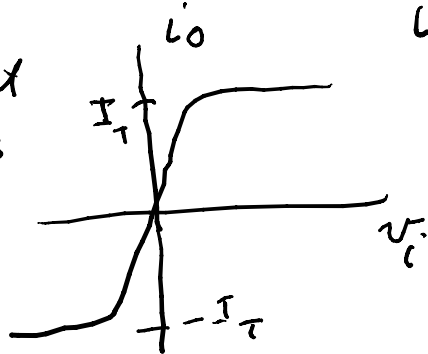

$$\tanh x = \frac{\sinh x}{\cosh x} = \frac{e^x - e^{-x}}{e^x + e^{-x}}$$

$$\frac{dI_o}{dV_i} = I_T \frac{d \tanh(V_i/2V_T)}{dV_i} = \frac{I_T}{2V_T} \cdot \frac{d \tanh(x)}{dx} \Rightarrow$$

$$\frac{d(e^x - e^{-x}) / (e^x + e^{-x})}{dx} = \frac{e^x + e^{-x}}{e^x + e^{-x}} + (-1) \frac{(e^x - e^{-x})(e^x - e^{-x})}{(e^x + e^{-x})^2} = 1 - \tanh^2 x$$

$$\frac{d i_o}{d v_i} = \frac{I_T}{2V_T} (1 - \tanh^2(v_i/2V_T)); \quad G_m |_{v_i=0} = \frac{I_T}{2V_T}$$

inverters



using CMOS

