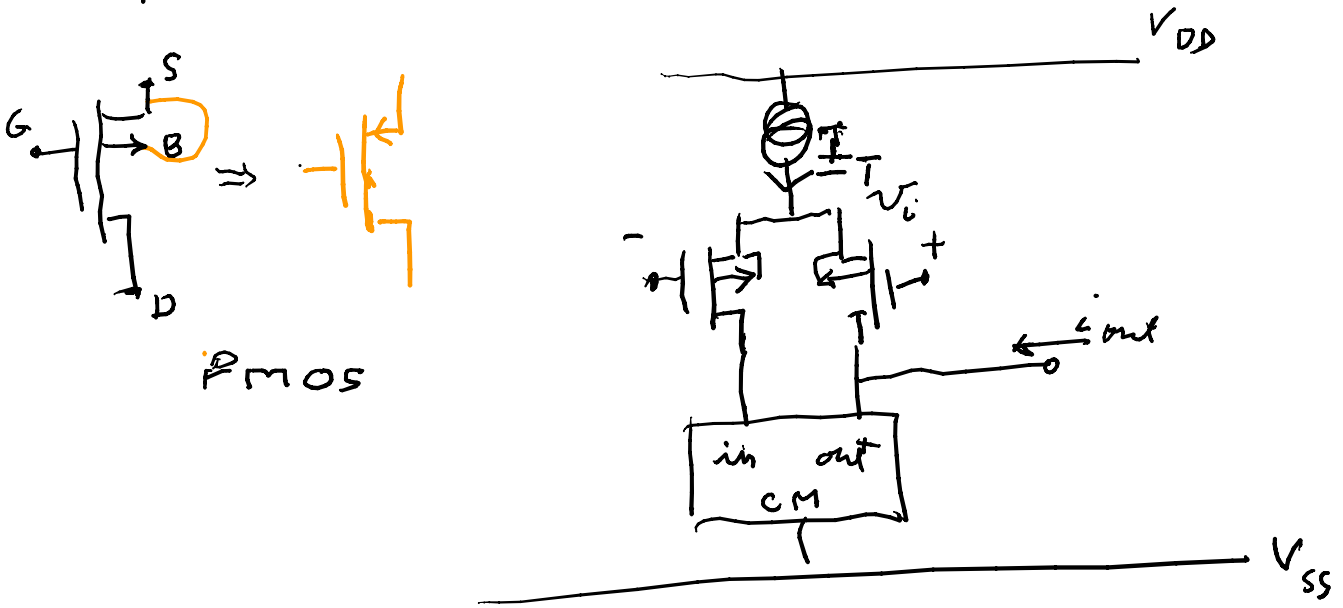



$\sigma_{A_{02}}$ PMOS diff. pair



if use BJT

$$i_o = I_T \tanh\left(\frac{v_i}{2V_T}\right) \approx I_T \cdot \frac{v_i}{2V_T}$$

for $|v_i|$ small





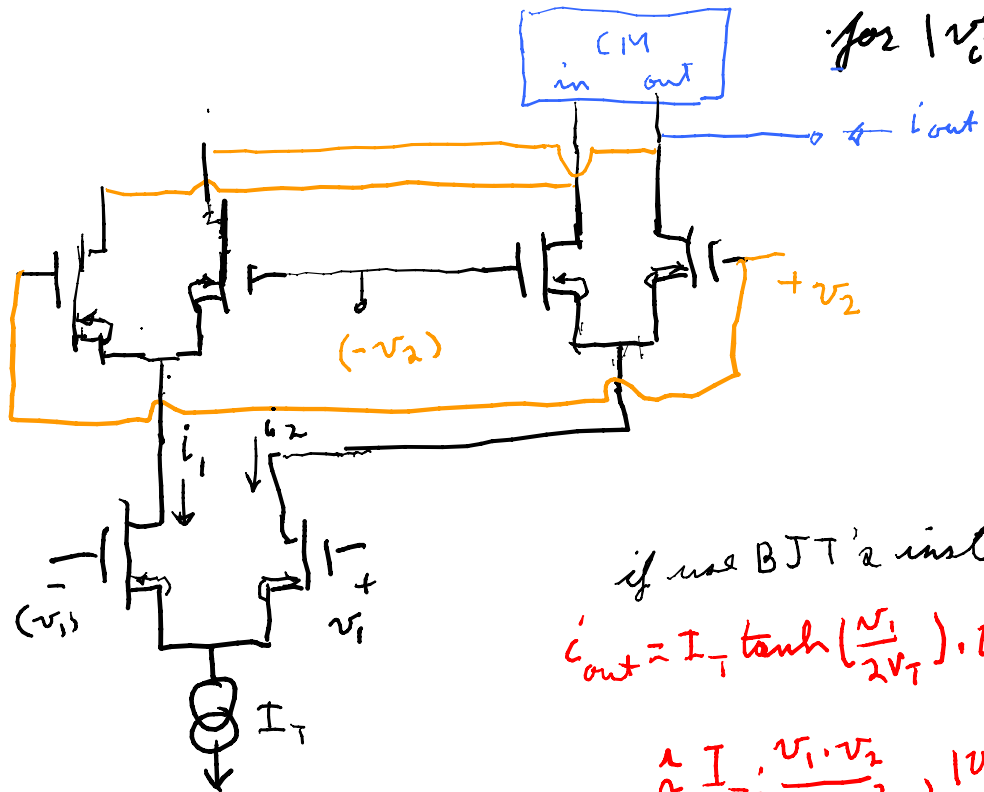


if use BJT's instead

$$i_{out} = I_T \tanh\left(\frac{v_1}{2V_T}\right) \cdot \tanh\left(\frac{v_2}{2V_T}\right)$$

$$\approx I_T \cdot \frac{v_1 \cdot v_2}{4V_T^2}, \quad |v_1|, |v_2| \text{ small}$$

Inverter:

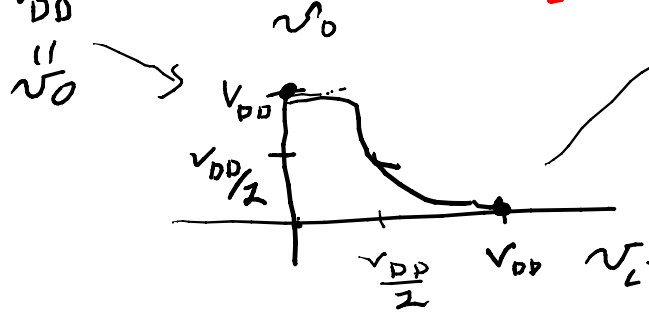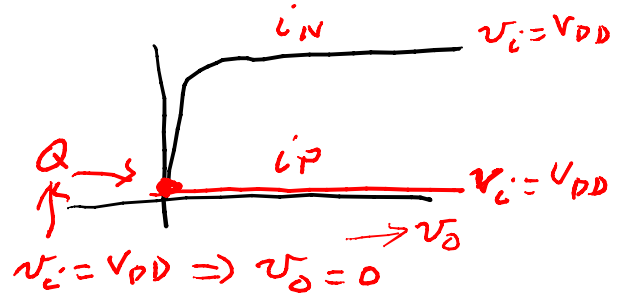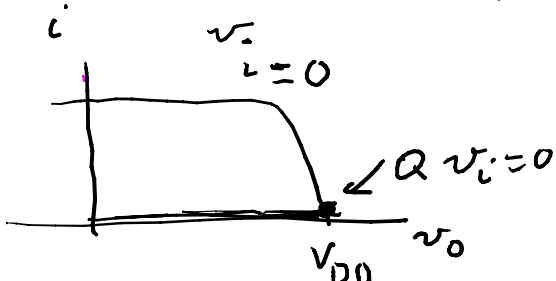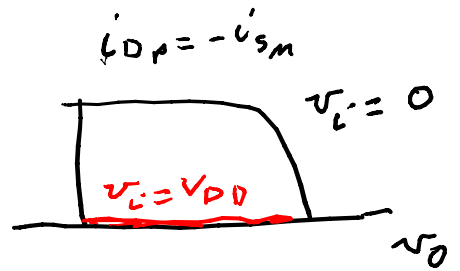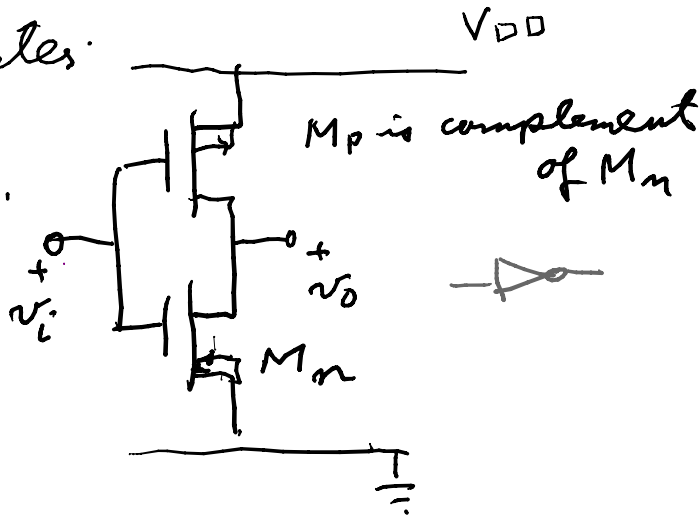

if $V_{SS} < 0$
 V_{DD}
 $-V_{DD}$




at $v_i = (V_{DD} + V_{SS})/2$, M_n & M_p are in saturation

if $V_{SS} = 0$, $i_{Dn} = \frac{k_p}{2} \frac{W}{L} (v_i - V_{th})^2 (1 + \lambda v_o)$



$-i_{Dp} = \frac{k_p}{2} \frac{W}{L} (V_{DD} - v_i - |V_{thp}|)^2 (1 + \lambda_p [V_{DD} - v_o])$

set $i_{Dn} = -i_{Dp}$ & solve for v_o vs v_i (only when M_p & M_n are in saturation)

In cascade

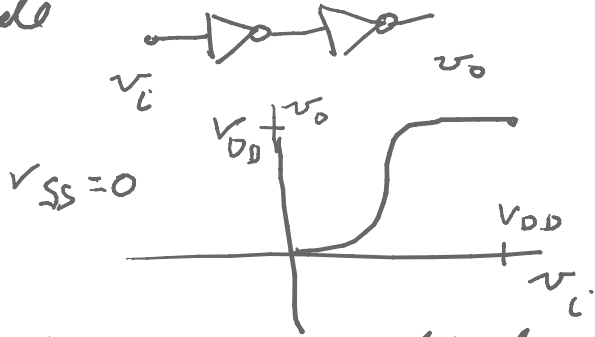


if $v_o = v_i$ by feedback.

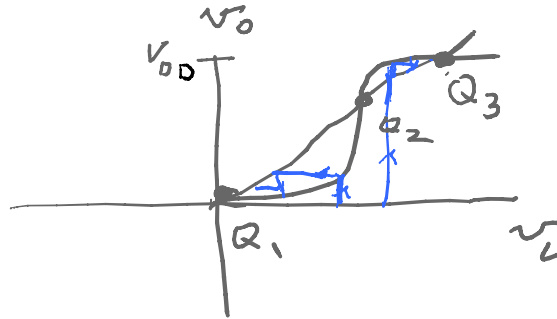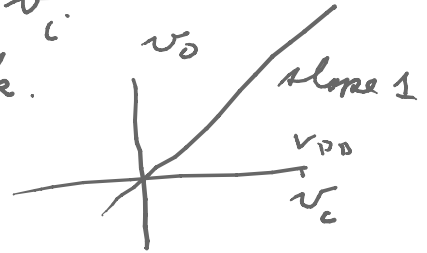

Q_1 & Q_3 are stable but Q_2 is not

if $v_i = v_i + \epsilon$
 $Q_2 \downarrow$

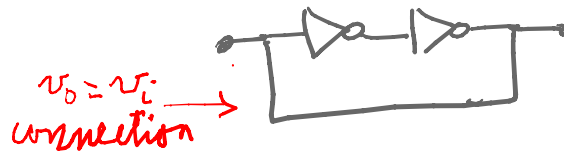goes to v_{Q_3}
 if $\epsilon > 0$
 (or v_{Q_1} if $\epsilon < 0$)



memory
 a good binary
 memory as
 Q_1 & Q_3 are stable