
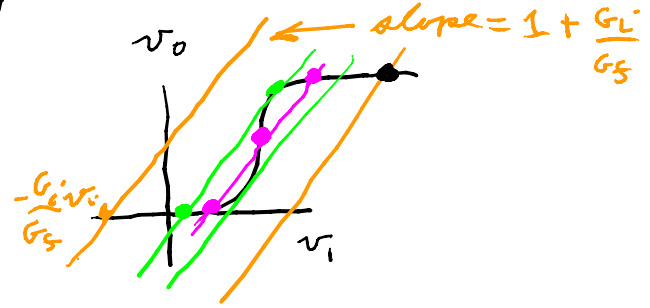




Hysteresis, p. 1357-1364

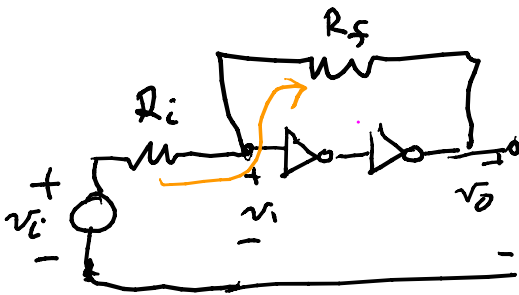


$$G_i(v_i - v_1) = G_s(v_1 - v_o)$$

$$G_s v_o = (G_i + G_s)v_1 - G_i v_i$$

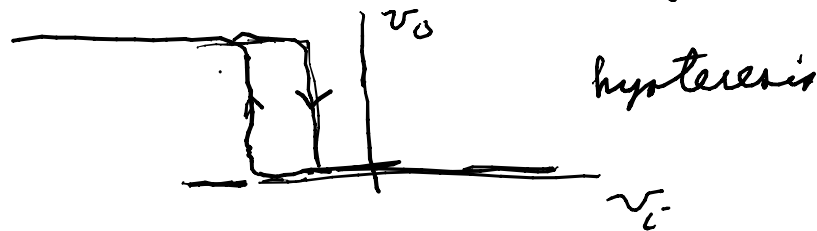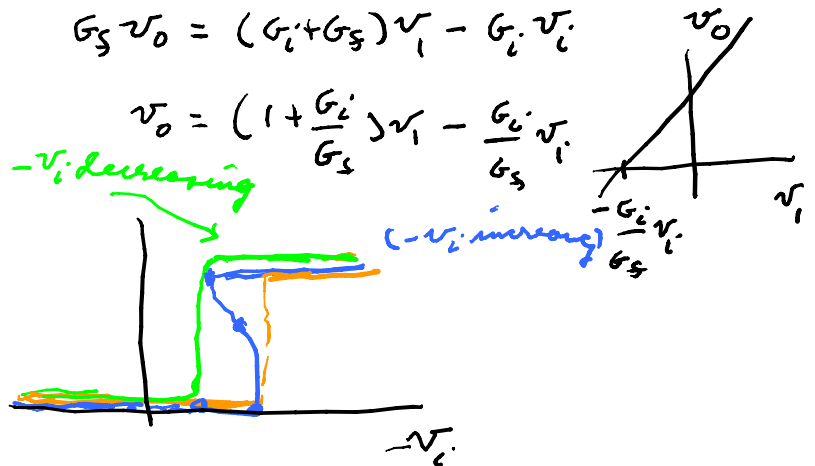
$$v_o = \left(1 + \frac{G_i}{G_s}\right)v_1 - \frac{G_i v_i}{G_s}$$



CMOS inverters, crystal oscillators

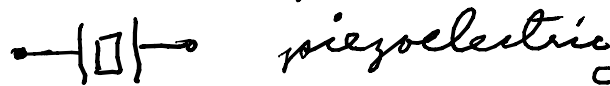

$Z(s) \Rightarrow$

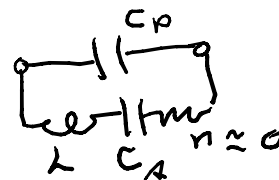

$$Y(s) = \frac{1}{Z(s)}$$

$$= C_p s + \frac{1}{s^2 L + \frac{1}{C_A}} = C_p s + \frac{C_A s^2}{1 + LC_A s^2}$$

$$= \frac{C_p s^3 + LC_A C_p s + C_A}{1 + LC_A s^2}$$

sinusoidal steady state

$$Z(s) = \frac{LC_s s^2 + 1}{A(LC_s C_p s^2 + C_p + C_s)}$$

(positive real lossless
 C is $R=0 \Rightarrow$ lossless
 not lossless if $R \neq 0$)

↓
 $P_{ave} = \text{Re } V^* I$
 quantity $= \frac{V^* I + V I^*}{2}$
 $= \frac{[V^* y(j\omega) V + V y^*(j\omega) V^*]}{2}$
 $= \frac{V^* (y(j\omega) + y(-j\omega)) V}{2} = 0$

as quantity
 is lossless
 if $R=0$

$= \text{Re } y(j\omega) = 0$
 $y(j\omega) = \frac{j\omega(-LC_s C_p \omega^2 + C_p + C_s)}{1 - LC_s \omega^2}$
 is purely imaginary

$2 \text{Re } f(s) = f(s) + f^*(s)$

if $s = j\omega \Rightarrow 2 \text{Re } f(s) = f(j\omega) + f(-j\omega)$
 $s = j\omega$


$2 \text{Ev } f(s) = f(s) + f(-s)$

$2 \text{Ev } f(j\omega) = 2 \text{Re } f(j\omega)$ if $f^*(j\omega) = f(-j\omega) = f(-j\omega)$

as $\text{Re } Z(j\omega) = 0 \Rightarrow \text{Ev } Z(s) = 0$

$\text{Re } y(j\omega) = 0 \Rightarrow \text{Ev } y(s) = 0 \Rightarrow y(s)$ is an odd function of s for a lossless circuit

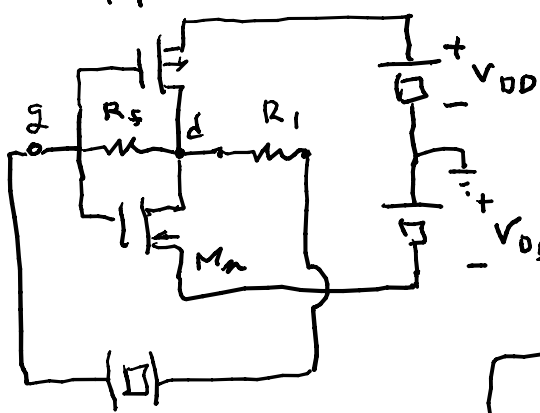
the circuit for oscillation give signals of the form $e^{j\omega_0 t}$



for $C_{gd} = 0$
 $C_{gs} = \frac{1}{3} W L C_{ox}$ } saturation


P. 702

at V_{DS} or V_{GS} by bias

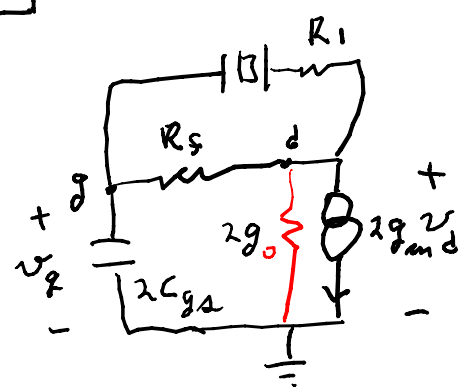

Phase oscillator

↓ simplify $R_s = 0, g_o = 0, v = 0$

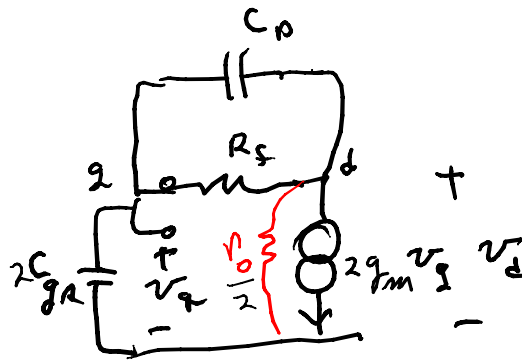

$$1) \quad 2g_m v_g = G_S (v_g - v_d) + C_p (v_g - v_d)$$

$$2) \quad 2C_{gs} \cdot v_g = 2C_p (v_d - v_g) + G_S (v_d - v_g)$$

$$3) \quad 2(-C_{gs} s + g_m) v_g = 0 \Rightarrow v_g \neq 0$$

if $s = g_m / C_{gs}$

\Rightarrow unstable if $R_s, v, g_o = 0$

no cont ignore

(most important is g_o)

For $g_o = 0$, add $2g_o v_d$ to 1) & 3) $\Rightarrow v_d = \frac{C_{gs} s - g_m}{g_o} v_g$

or 1) becomes

$$\left[2g_m - G_S - C_p s + (C_p s + G_S) \frac{(C_{gs} s - g_m)}{g_o} \right] v_g = 0$$

and if $v_g \neq 0$ then the coefficient = 0, set it = 0 & look for roots for oscillations of type $s = j\omega$

$$\left[2g_m - G_S - j\omega C_p + (G_S + j\omega C_p) \left(\frac{j\omega C_{gs}}{g_o} - \frac{g_m}{g_o} \right) \right] = 0$$

\therefore set the real part = 0 & imaginary = 0

$$\text{Re: } 2g_m - G_S - G_S \frac{g_m}{g_o} - \omega^2 C_p \frac{C_{gs}}{g_o} = 0 \Rightarrow g_m \left(2 - \frac{G_S}{g_o} \right) - \left(G_S + \omega^2 \frac{C_p C_{gs}}{g_o} \right) = 0$$

$$\text{Im: } -\omega C_p + \omega G_S \frac{C_{gs}}{g_o} - \omega C_p \frac{g_m}{g_o} \Rightarrow \frac{G_S C_{gs}}{g_o} - C_p \left[1 + \frac{g_m}{g_o} \right] = 0$$

\therefore can design for a desired $\omega = \omega_0$ via G_S & g_m (g_m via biasing)
(note $g_o \neq 0$ is needed) over limited range