

$$T(s) = \frac{1}{s^2 + a_{n-1}s^{n-1} + \dots + a_1s + 1} \quad \text{on normalization}$$

$$\frac{1}{|T(j\omega)|^2} = \frac{1}{T(j\omega)T^*(j\omega)} = \frac{1}{T(j\omega)T(-j\omega)} = 1 + \omega^{2n}$$

$$\Rightarrow \frac{1}{T(s)} \cdot \frac{1}{T(-s)} = 1 + (-1)^n s^{2n} \Rightarrow P(s) = 1 + (-1)^n s^{2n}$$


derive its zeros

$$T(s)T(-s) = P(s) = 1 + (-1)^n s^{2n} \Rightarrow s^{2n} = (-1)^{-n} = \begin{cases} -1 & n \text{ even} \\ +1 & n \text{ odd} \end{cases} = e^{j(\pi + 2\pi k)}$$

n even $s^{2n} = -1$; $s_{\text{root}} = 2n$ th roots of -1 ; $-1 = e^{j(\pi + 2\pi k)}$

$$s_k = e^{j \frac{(\pi + 2\pi k)}{2n}}; \quad k = 0, 1, \dots, 2n$$
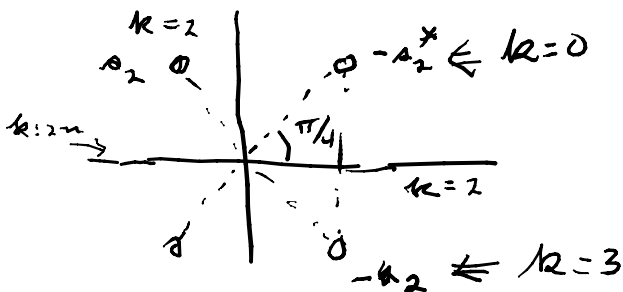
$$\begin{aligned} n=2, k=1 & \Delta = 3\pi/4 \\ & = 2 \Delta = 5\pi/4 \\ & = 0 \Delta = \pi/4 \\ k=3 & \Delta = \pi/4 \end{aligned}$$



$$\underbrace{\hspace{10em}}_{T(s)} \quad \underbrace{\hspace{10em}}_{T(-s)}$$



$$\begin{aligned} s_2 &= e^{j 5\pi/4} \\ &= -\cos 45^\circ + j \sin 45^\circ \\ &= -\frac{1}{\sqrt{2}} + j \frac{1}{\sqrt{2}} \end{aligned}$$

$$\begin{aligned} n=2 \\ T(s) &= \frac{1}{s^2 + a_1s + 1} \\ &= \frac{1}{(s - s_2)(s - s_2^*)} \\ &= \frac{1}{\left(s + \frac{1}{\sqrt{2}} - j \frac{1}{\sqrt{2}}\right) \left(s + \frac{1}{\sqrt{2}} + j \frac{1}{\sqrt{2}}\right)} \\ &= \frac{1}{s^2 + \frac{2}{\sqrt{2}}s + 1} \end{aligned}$$

$$T(s) = \frac{1}{s^2 + \sqrt{2}s + 1}$$

for any $n \quad 1 + (-1)^n 2^{2n}$
 $\textcircled{a} \quad s = j1 = 1 + (-1)^n (1+j)^{2n} = 2$

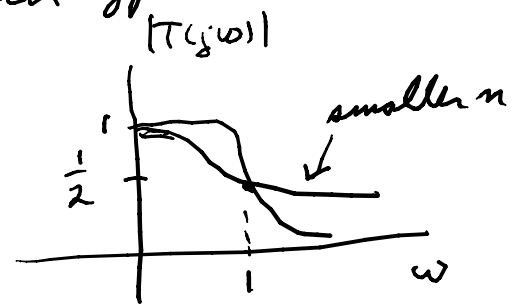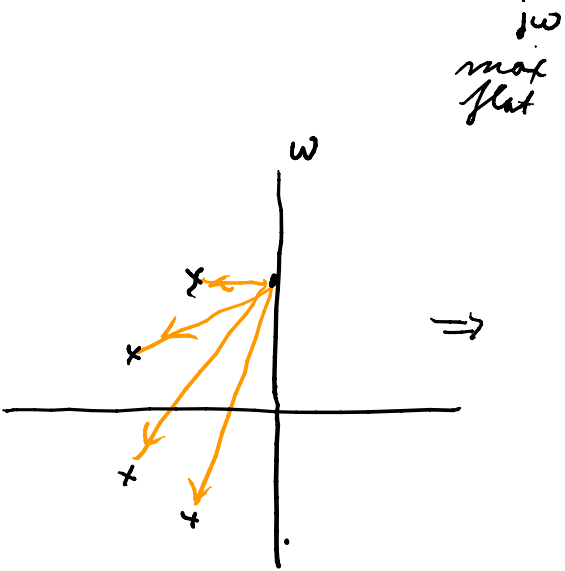
$\therefore \textcircled{a} \quad j\omega = j1, \quad T(s) = \frac{1}{2} = \text{cut off}$



$$T(s) = \frac{1}{\sum \text{mag}(j\omega \text{ to pole term})}$$

for poles on unit circle & equally spaced in ω get max flat

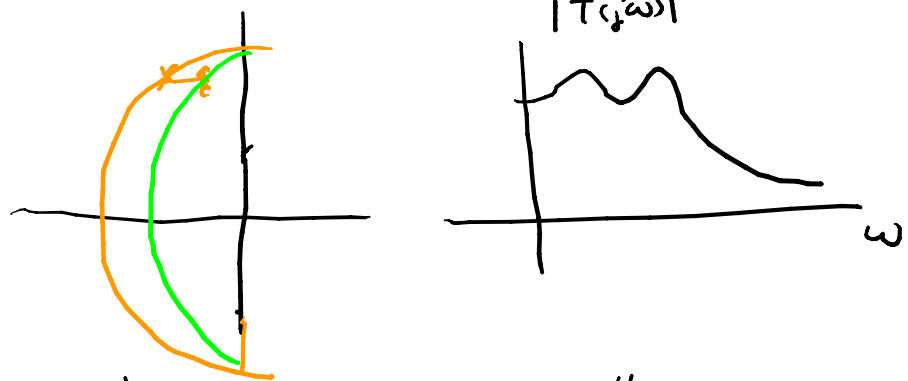So if poles onto an ellipse can get equal ripple



Given $T(s) = \frac{b_{m-1}s^{m-1} + \dots + b_0}{s^m + a_{m-1}s^{m-1} + \dots + a_1s + a_0} = \frac{y}{u}$

how to design a circuit?

$$\begin{bmatrix} x_1 \\ x_2 \\ \vdots \\ x_m \end{bmatrix} = \begin{bmatrix} 0 & 1 & 0 & \dots & 0 \\ 0 & 0 & 1 & \dots & 0 \\ \vdots & \vdots & \vdots & \ddots & \vdots \\ 0 & 0 & \vdots & \dots & 1 \\ -a_0 & -a_1 & \dots & \dots & -a_{m-1} \end{bmatrix} \begin{bmatrix} x_1 \\ x_2 \\ \vdots \\ x_m \end{bmatrix} + \begin{bmatrix} 0 \\ 0 \\ \vdots \\ 0 \\ b_0 \end{bmatrix} u$$

$$y = [b_0 \dots \dots a_{m-1}] \begin{bmatrix} x_1 \\ \vdots \\ x_m \end{bmatrix}$$

companion matrix form
 $\dot{x} = \begin{bmatrix} x_1 \\ \vdots \\ x_m \end{bmatrix}$
 = state

$$\dot{x}_1 = x_2 = x_2 = a x_1 \quad a = d/dt$$

$$\dot{x}_2 = x_3 = \ddot{x}_1, \quad x_3 = a^2 x_1$$


$$a^n x_m = a^n x_1 = -a_0 x_1 - a_1 a x_1 - \dots - a_{n-1} a^{n-1} x_1 + b u$$

$$(a^n + a_{n-1} a^{n-1} + \dots + a_0) x_1 = b u$$

$$y = [c_0 \dots c_{n-1}] \begin{bmatrix} x_1 \\ a x_1 \\ \vdots \\ a^{n-1} x_1 \end{bmatrix} = [c_{n-1} a^{n-1} + \dots + c_0] b u$$

$$a^n + a_{n-1} a^{n-1} + \dots + a_0$$

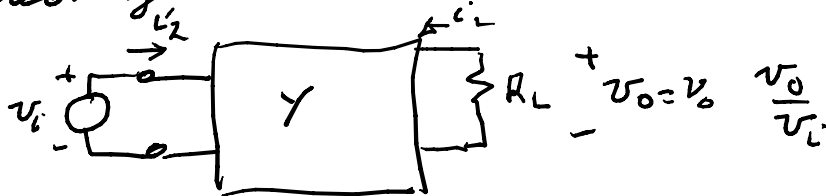To create a transfer voltage function from admittances



$$\begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix}; \quad i_2 = -G_L v_0$$

$$= y_{21} v_1 + y_{22} v_0$$

$$(-G_L - y_{22}) v_0 = y_{21} v_i$$

$$\frac{v_0}{v_i} = \frac{-y_{21}}{G_L + y_{22}} \quad (ex = \frac{1}{a^2 + \sqrt{2}a + 1})$$

$$\text{if } G_L = 1 \Rightarrow \frac{v_0}{v_i} = \frac{\sqrt{2}a + 1}{1 + \frac{\sqrt{2}a}{a^2 + 1}}$$

