

Open book open notes but not open computers; 100 points total (75 minutes); if stuck go on to the next problem. Good luck

For the following problems use $V_{DD}=10V$.

For the npn transistors: $\beta = 100$, $V_A=100V$, $C_{\pi} = 10pFd$, $C_{\mu} = 0$; bias $V_{BE}=0.7$

For pnp transistors, assume they are completely complementary to the npn ones.

For the NMOS transistors: $K_P=5 \times 10^{-4}$, $V_{TO}=1$, $LAMBDA=0.01$, $W/L=$ to be chosen.


For PMOS transistors, they are completely complementary to the NMOS ones.

1. (30 points, 20 min)

Design a current mirror using two pnp transistors and a resistor to source a current of 3mA. If this gives 3mA at an output voltage of 8V determine the output current at 9V.

2. (30 points, 20 min)

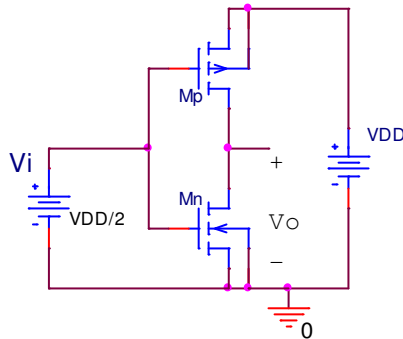- a) Find I_S for M_p when $W/L=1$.
- b) Give the power delivered by the two batteries.



3 (40 points, 25 min)

For the following circuit assume that W/L is chosen such that V_o is biased to $V_o = 3V$

- a) Give numerically the transistor's source current I_S , g_m and g_o .
- b) Draw the small signal equivalent circuit including C_{gs} & C_{gd} using generic symbols (= without numerical values).
- c) Find (without numerical values) the small signal voltage gain, $v_o/v_i(s)$ and give its poles and zeros.
- d) Evaluate numerically the poles and zeros when $C_{gs}=C_{gd}=5pFd$.

