


303H Fall 2013
 Homework 2 – due 09/24/13

1. 50 points (Transistor biasing)

Use the following configuration to carry out four different cases of biasing, one each for each of the four different transistors, an NPN 2N3904, a PNP 2N3906, a NMOS mnmosis, and a PMOS mpmosis. Assume that node a is the base of a BJT or the gate of a MOS, that node L is the collector of an NPN, the emitter of a PNP, the drain of an NMOS and the source of a PMOS (node f is the remaining node of the transistor) [assume the MOS transistors have the bulk tied to the source]

Bias all transistors so that for the BJTs $|I_C| = 10\text{mA}$ and for the CMOS $|I_D|$ is $100\mu\text{A}$ (assume $|V_{BE}|=0.7\text{V}$ and R_a and R_b are in the MEG Ohm range and R_f as close to 100 Ohms as is reasonable)

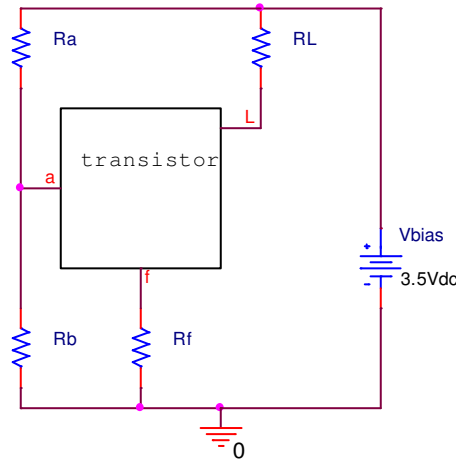Give the Q point voltage and current values for each transistor and compare.



2. 50 points (BJT & MOS small signal equivalents)

For each of the transistors biased in problem 1 draw the small signal pi equivalent circuit with the element values including g_m .