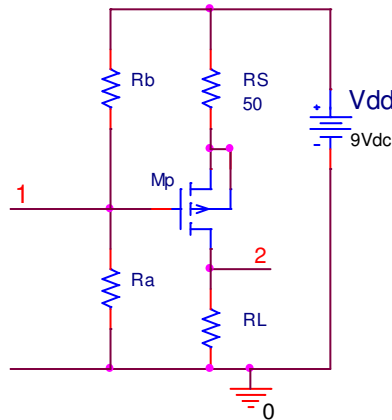


1. 50 points (PMOS biasing)

Bias the PMOS 4007 in the following circuit to have a Q point at $V_{GS} = -3V$, $V_{DS} = -6V$. For this assume an $R_S = 50\Omega$, $V_{dd} = 9V$, and one of R_a or R_b of $20\text{Meg}\Omega$. Check using Spice. Draw the small signal equivalent circuit and give the small signal low frequency voltage gain, $A_v = V_{20}/V_{10}$ (include R_S)



2. 50 points (Differential Pair amplifier)

Using seven CMOS 4007 transistors, $V_{dd} = -V_{ss} = 9V$ and a third battery V_{4tail} for biasing (using CMOS diodes) for a tail current of 2mA , design a differential pair VCCS. Check your design using Spice (submit your Spice circuit and I_{out} plot). For the transistors you can use breakout transistors with the models that are on the web.

Do this two different ways, one with the main pair being NMOS and again with them being PMOS. Discuss differences.