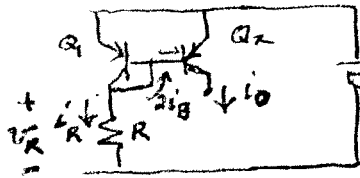


#1.



$$i_{E1} = i_{E2} = -\frac{1}{\alpha} i_{C1} = -\frac{1}{\alpha} i_{C2} ; i_{C0} = -i_{C2} = 3 \times 10^{-3} \text{ A}$$

$$i_{R} = -i_{C1} - 2i_{B} = -(\beta i_{B} - 2i_{B}) = -(2 + \beta) i_{B}$$

$$\beta i_{B} = i_{C2} = -i_{C0} \Rightarrow i_{B} = -\frac{i_{C0}}{\beta} \Rightarrow i_{R} = \frac{2 + \beta}{\beta} \cdot i_{C0}$$

$$\Rightarrow i_{R} = \left(\frac{102}{100} \right) \cdot 3 \times 10^{-3} = 3.06 \text{ mA}$$

$$V_{R} = V_{DD} - V_{BE} = 9.3 = R i_{R} = R \times 3.06 \times 10^{-3} \Rightarrow R = \frac{9.3}{3.06} \times 10^3 = 3.04 \text{ K}\Omega$$

since $i_{C}(V_{BE}) = i_{C0} \left(1 + \frac{V_{BE}}{V_A} \right) \Rightarrow i_{C0} = \frac{3 \times 10^{-3}}{1 + 1/100} = i_{C}(8)$

$$\Rightarrow i_{C}(9) = \frac{3 \times 10^{-3}}{1 + 1/100} \left(1 + \frac{1}{100} \right) = \frac{101}{102} \times 3 \times 10^{-3} = 2.971 \times 10^{-3} = 2.97 \text{ mA}$$

(vs. 3.06 design)

#2. For complementary M_p & M_n , $v_o = V_{DD}/2$ when $v_i = V_{DD}/2$

as both transistors are in saturation as

$$|V_{GS}| - |V_{TO}| = 5 - 1 = 4 < 5 = |V_{DS}|$$

$$i_S = \frac{K_P}{2} \cdot \frac{W}{L} \cdot (|V_{GS}| - |V_{TO}|)^2 (1 + \lambda |V_{DS}|) = \frac{5}{2} \times 10^{-4} (5 - 1)^2 (1 + 0.01 \times 5)$$

a) $= \frac{5 \times 16}{2} \times (1.05) \times 10^{-4} = 4.20 \times 10^{-3} \text{ A}$


b) as no current flows in V_i , its power delivered is 0.

The power out of V_{DD} is $i_S \times V_{DD} = 42 \times 10^{-3} \text{ Watts}$

3. a) $I_S = V_0/R_L = 3V/2k\Omega = \frac{3}{2} \times 10^{-3} A$

$g_m = \left. \frac{\partial I_S}{\partial V_{GS}} \right|_{I_S = 1.5mA}$; M_p is in saturation as $|V_{GS}| = 10 - 8 = 2$
 $|V_{GS}| - |V_{TO}| = 2 - 1 = 1 < 10 - 3 = 7 = |V_{DS}|$
 $= \frac{2 I_S}{(|V_{GS}| - |V_{TO}|)} = \frac{3 \times 10^{-3}}{1} = 3 mS$

$g_o = \left. \frac{\partial I_S}{\partial V_{DS}} \right|_{I_S = 1.5mA} = \frac{\lambda I_S}{(1 + \lambda |V_{DS}|)} = \frac{0.01 \times \frac{3}{2} \times 10^{-3}}{1 + 0.01 \times 7} = \frac{1.5 \times 10^{-5}}{1.07} \approx 1.40 \times 10^{-5} S$

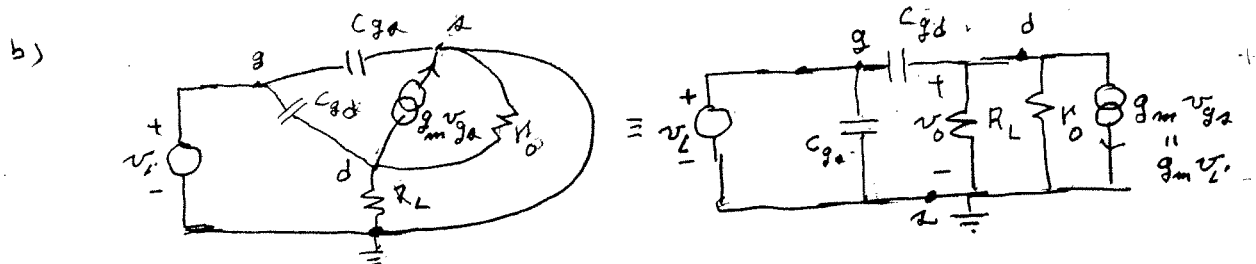

c) use KCL @ d-n:

$$i_{C_{gd}} = i_{C_{gs}}(v_i - v_o) = i_{R_L} + i_{r_o} + g_m v_{gs} = (G_L + g_o) v_o + g_m v_i$$

$$\Rightarrow (sC_{gd} - g_m) v_i = (sC_{gd} + [G_L + g_o]) v_o$$

$$\Rightarrow \frac{v_o(s)}{v_i} = \frac{C_{gd}(s - g_m/C_{gd})}{C_{gd}(s + \frac{G_L + g_o}{C_{gd}})} = \frac{s - \frac{g_m}{C_{gd}}}{s + \frac{G_L + g_o}{C_{gd}}}$$

zero: $s = g_m/C_{gd}$, pole: $s = -\frac{G_L + g_o}{C_{gd}}$

d) zero: $s = \frac{3 \times 10^{-3}}{5 \times 10^{-12}} = \frac{3}{5} \times 10^9 = 0.6 \times 10^9 \text{ (radian Hertz)}$

pole: $s = -\left(\frac{\frac{10^{-3}}{2} + 1.4 \times 10^{-5}}{5 \times 10^{-12}}\right) = -\frac{(50 + 1.4) \times 10^{-5}}{5 \times 10^{-12}} = -10.28 \times 10^7 \text{ (radian Hertz)}$