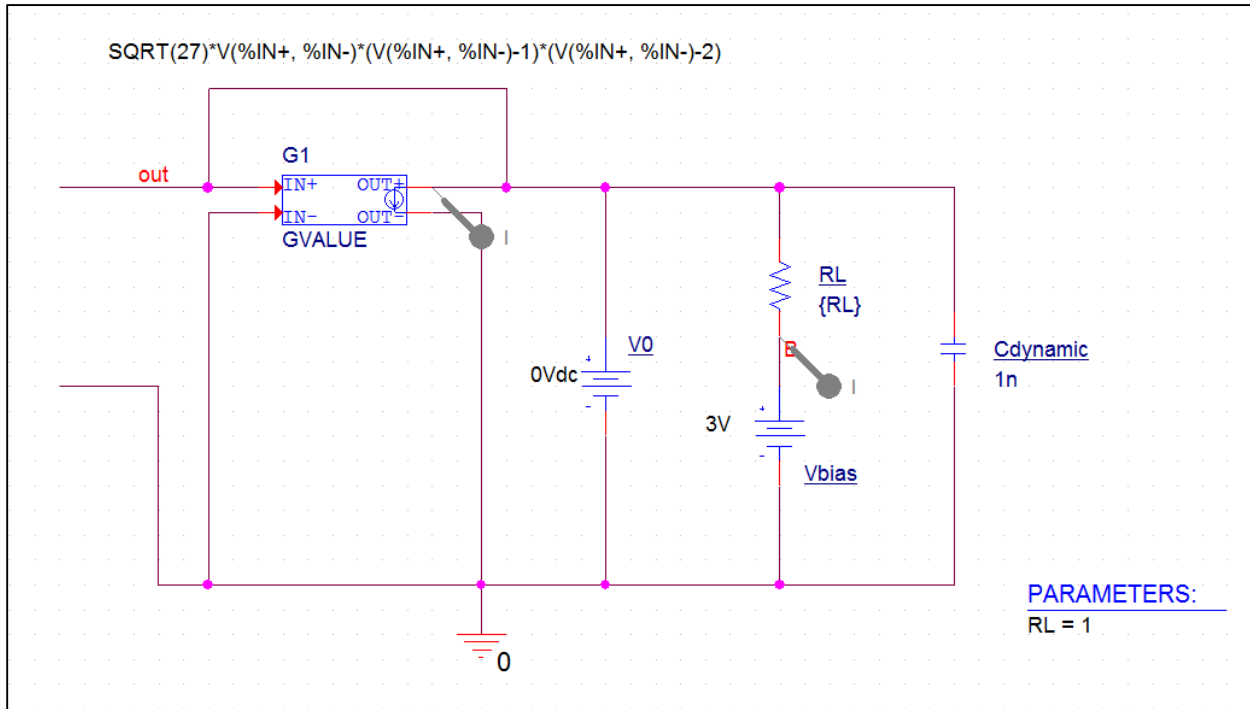



Homework 1 Solutions

Problem#1


Circuit Schematic



(A) bias (active)

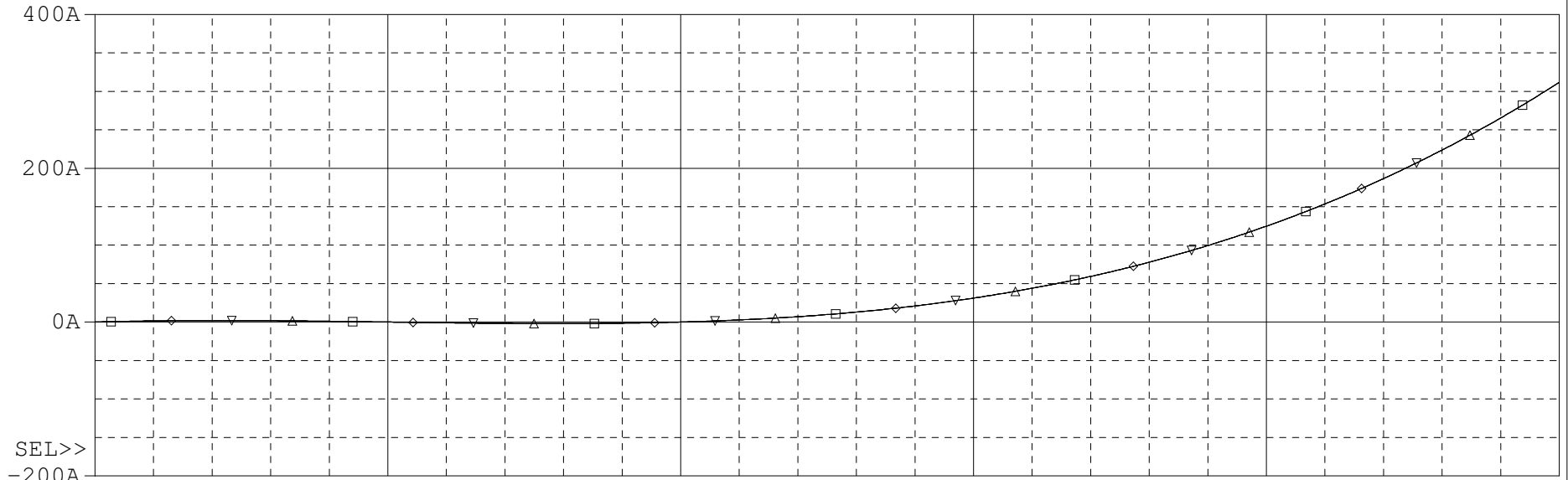


□ ◇ ▽ △ I (G1)

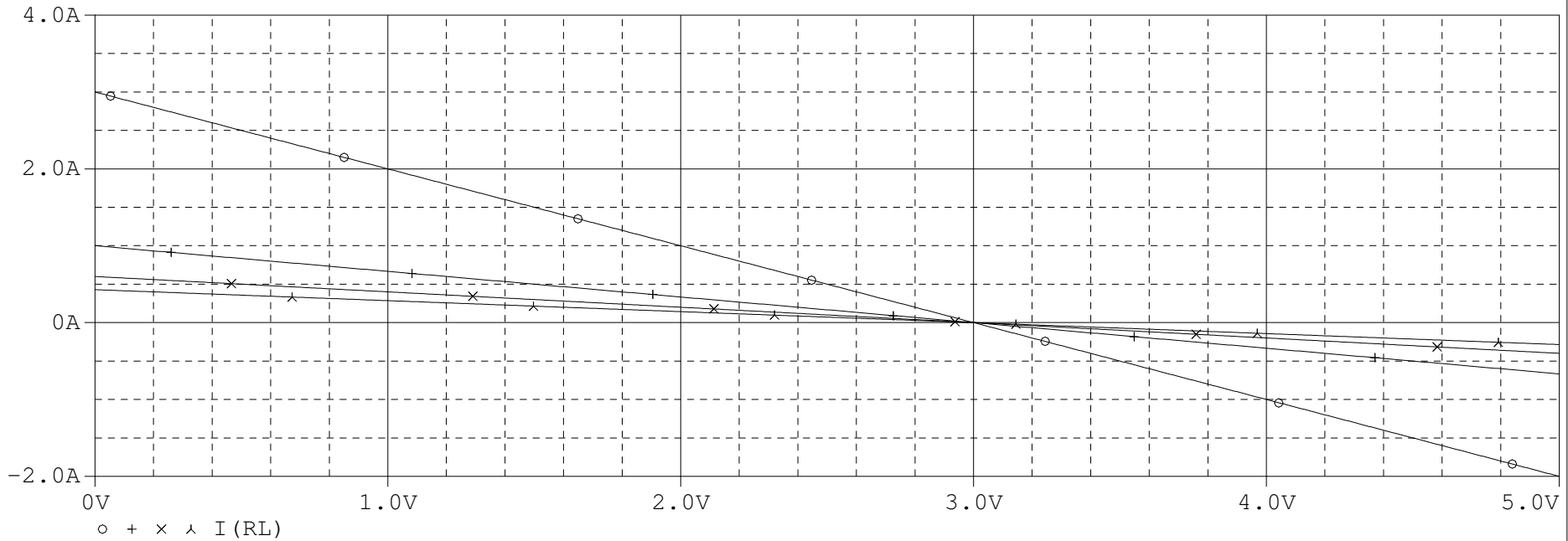


○ + × * I (RL)

V_V0

(A) bias (active)

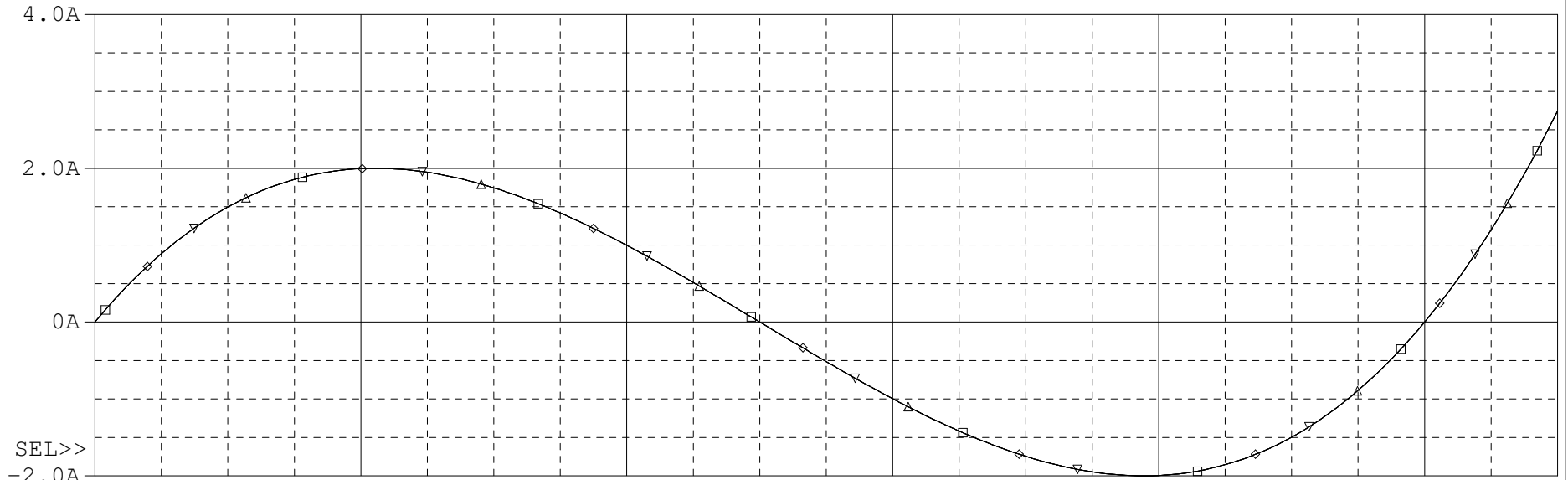




□ ◇ ▽ △ I (G1)

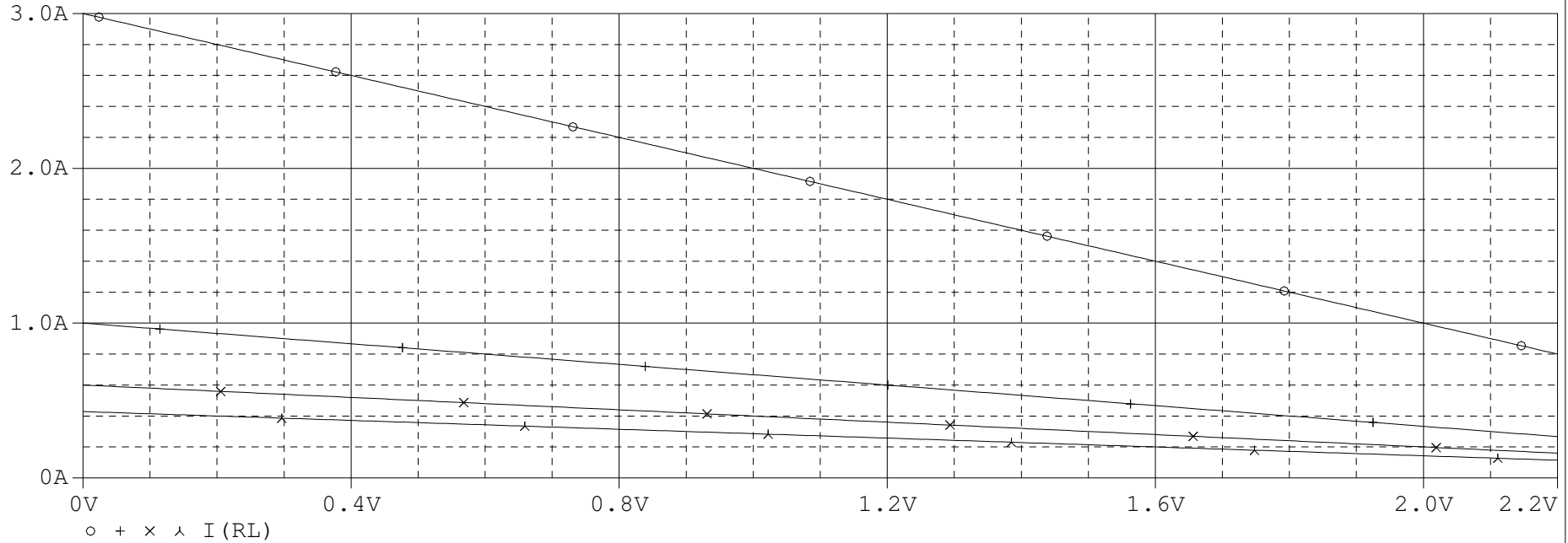


○ + × ^ I (RL)

V_V0

Problem # 2

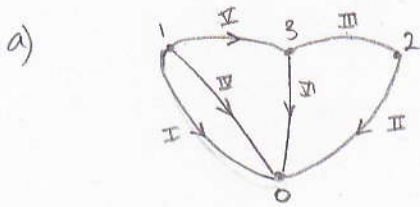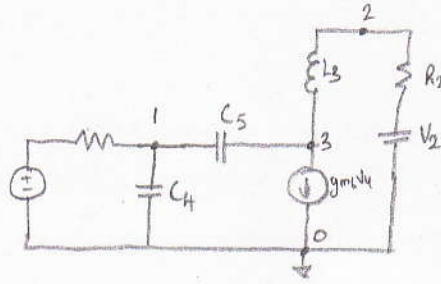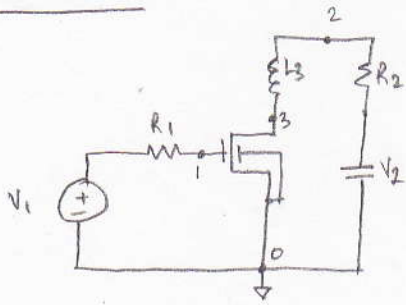




oriented graph

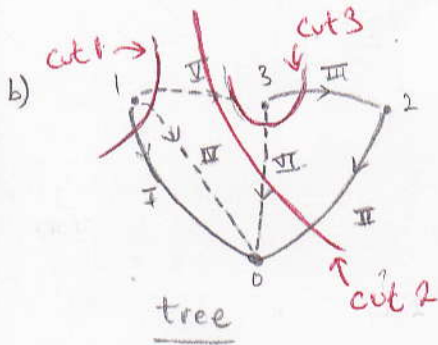

— = tree branches
 --- = link branches

$$C = \begin{bmatrix} 0 \\ 0 \\ 0 \end{bmatrix} = \begin{bmatrix} 1 & 0 & 0 & 1 & 1 & 0 \\ 0 & 1 & 0 & 0 & -1 & 1 \\ 0 & 0 & 1 & 0 & -1 & 1 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \\ i_4 \\ i_5 \\ i_6 \end{bmatrix}$$

C = Cut-set

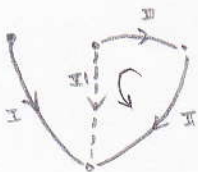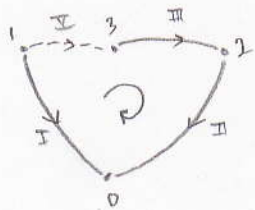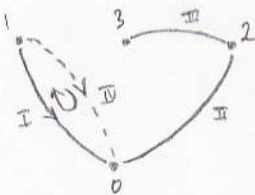

$$T = \begin{bmatrix} 0 \\ 0 \\ 0 \end{bmatrix} = \begin{bmatrix} -1 & 0 & 0 & 1 & 0 & 0 \\ -1 & 1 & 1 & 0 & 1 & 0 \\ 0 & -1 & -1 & 0 & 0 & 1 \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \\ v_3 \\ v_4 \\ v_5 \\ v_6 \end{bmatrix}$$

T = tie set

c) from circuit:

$$\left. \begin{aligned} v_1 &= i_1 R_1 \\ v_2 &= i_2 R_2 \\ v_3 &= sL_3 i_3 \\ sC_4 v_4 &= i_4 \\ sC_5 v_5 &= i_5 \\ i_6 &= g_m v_4 \end{aligned} \right\}$$

$$\begin{bmatrix} i_1 \\ i_2 \\ i_3 \\ i_4 \\ i_5 \\ i_6 \end{bmatrix} = \begin{bmatrix} 1/R_1 & 0 & 0 & 0 & 0 & 0 \\ 0 & 1/R_2 & 0 & 0 & 0 & 0 \\ 0 & 0 & 1/sL_3 & 0 & 0 & 0 \\ 0 & 0 & 0 & sC_4 & 0 & 0 \\ 0 & 0 & 0 & 0 & sC_5 & 0 \\ 0 & 0 & 0 & g_m & 0 & 0 \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \\ v_3 \\ v_4 \\ v_5 \\ v_6 \end{bmatrix}$$

$$\begin{bmatrix} v_1 \\ v_2 \\ 0 \\ 0 \\ 0 \\ 0 \end{bmatrix}$$

Admittance Matrix

Source vector

$$AV = Bi$$

$$\begin{bmatrix} 1 & 0 & 0 & 0 & 0 & 0 \\ 0 & 1 & 0 & 0 & 0 & 0 \\ 0 & 0 & 1 & 0 & 0 & 0 \\ 0 & 0 & 0 & sC_4 & 0 & 0 \\ 0 & 0 & 0 & 0 & sC_5 & 0 \\ 0 & 0 & 0 & g_m & 0 & 0 \end{bmatrix} V = \begin{bmatrix} R_1 & 0 & 0 & 0 & 0 & 0 \\ 0 & R_2 & 0 & 0 & 0 & 0 \\ 0 & 0 & sL_3 & 0 & 0 & 0 \\ 0 & 0 & 0 & 1 & 0 & 0 \\ 0 & 0 & 0 & 0 & 1 & 0 \\ 0 & 0 & 0 & 0 & 0 & 1 \end{bmatrix} i$$

$$AC^T = A \begin{bmatrix} 1 & 0 & 0 \\ 0 & 1 & 0 \\ 0 & 0 & 1 \\ 1 & 0 & 0 \\ 1 & -1 & -1 \\ 0 & 1 & 1 \end{bmatrix} = \begin{bmatrix} 1 & 0 & 0 \\ 0 & 1 & 0 \\ 0 & 0 & 1 \\ sC_4 & 0 & 0 \\ sC_5 & -sC_5 & -sC_5 \\ g_m & 0 & 0 \end{bmatrix}$$

$$BT^T = B \begin{bmatrix} -1 & -1 & 0 \\ 0 & 1 & -1 \\ 0 & 1 & -1 \\ 0 & 0 & -1 \end{bmatrix} = \begin{bmatrix} -R_1 & -R_1 & 0 \\ 0 & R_2 & -R_2 \\ 0 & sL_3 & -sL_3 \\ 1 & 0 & 0 \\ 0 & 1 & 0 \\ 0 & 0 & 1 \end{bmatrix}$$

$$[AC^T | -BT^T] = \begin{bmatrix} 1 & 0 & 0 & R_1 & R_1 & 0 \\ 0 & 1 & 0 & 0 & -R_2 & R_2 \\ 0 & 0 & 1 & 0 & -sL_3 & sL_3 \\ sC_4 & 0 & 0 & -1 & 0 & 0 \\ sC_5 & -sC_5 & -sC_5 & 0 & -1 & 0 \\ g_m & 0 & 0 & 0 & 0 & -1 \end{bmatrix}$$

$$SEx = \bar{A}x + \bar{B}U$$

$$s \begin{bmatrix} 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & -L_3 & L_3 \\ C_4 & 0 & 0 & 0 & 0 & 0 \\ C_5 & -C_5 & -C_5 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 \end{bmatrix} x = \begin{bmatrix} -1 & 0 & 0 & -R & -R_1 & 0 \\ 0 & -1 & 0 & 0 & R_2 & -R_2 \\ 0 & 0 & -1 & 0 & 0 & 0 \\ 0 & 0 & 0 & 1 & 0 & 0 \\ 0 & 0 & 0 & 0 & 1 & 0 \\ g_m & 0 & 0 & 0 & 0 & 1 \end{bmatrix} x + \begin{bmatrix} v_1 \\ v_2 \\ 0 \\ 0 \\ 0 \\ 0 \end{bmatrix}$$