
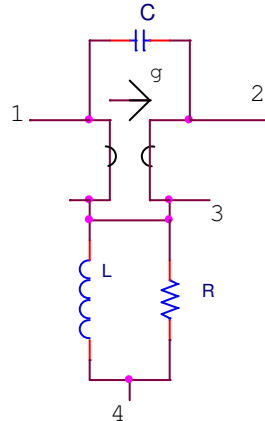


610 Fall 2013 – Homework 4 due Th 10/10/13

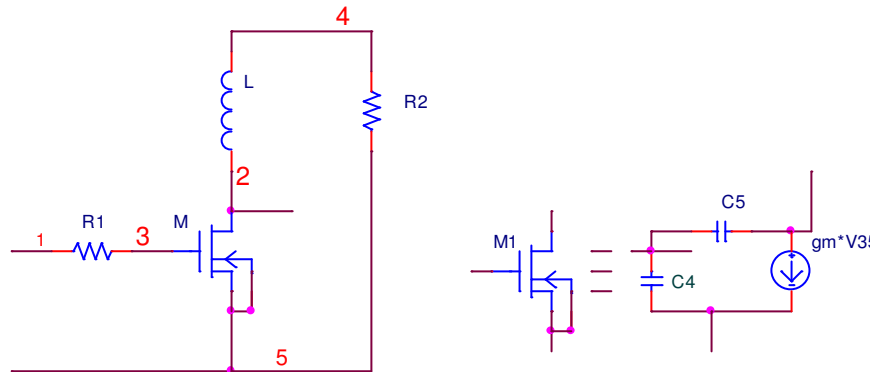1. (25 points) (indefinite Y to 2-port Z) For the following circuit
 - a) Give the indefinite admittance matrix $Y_{ind}(s)$.
 - b) Ground node 4 and eliminate node 3 to give the 2-port $Y(s)$; obtain $Z(s)=Y(s)^{-1}$



2. (10 points) (Even part zeroes) For the result of Problem 1, give the even part of $Y(s)$ and the even part of $Z(s)$, compare, and discuss the even part zeros in terms of $G=1/R$
3. (15 points) (load z in terms of input z) Using the 2-port $Y(s)$ of problem 1, set $C=G=0$
 - a. Find the load impedance $z_L(s)$ in terms of the input impedance $z(s)$.
 - b. Relate to the Richards function of the text and discuss the possibility for lossless synthesis.
4. (50 points) (step response of amplifier) The following 2-port circuit has the input port at nodes 1-5 and the output at nodes 2-5. Assume that $C5$ can be ignored ($C5=0$)
 - a. Give the transfer function $T(s)=V_{2-5}(s)/V_{1-5}(s)$ when fed by a voltage source and having an open-circuit load.
 - b. Assume $C4=C$ and $R1=R2=R$, and normalize $C = R = 1$. Give the normalized $T(s)$ and find the poles and zeros (in terms of g_m and L).
 - c. Give the unit step response of this normalized circuit. From it give the impulse response by taking the derivative.



[Optional, not for grading: repeat Problem 4 for $C5=C4$. Discuss why we know there is at least one real pole or zero]