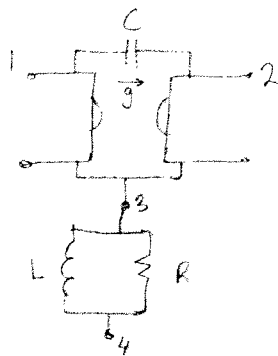


Homework #4

Problem #1



$$i_1 = g(v_2 - v_3)$$

$$i_3 = g(v_3 - v_2)$$



$$i_2 = g(v_3 - v_4)$$

$$i_4 = g(v_4 - v_3)$$

$$i_1 = sC(v_1 - v_2)$$

$$i_2 = sC(v_2 - v_1)$$

$$i_3 = \frac{1}{sL}(v_3 - v_4)$$

$$i_4 = \frac{1}{sL}(v_4 - v_3)$$

$$i_3 = G_R(v_3 - v_4)$$

$$i_4 = G_R(v_4 - v_3)$$

$$Y_{ind} = \begin{bmatrix} sC & -sC+g & -g & 0 \\ -sC-g & sC & g & 0 \\ g & -g & \frac{1}{sL}+G_R & \frac{1}{sL}-G_R \\ 0 & 0 & \frac{1}{sL}-G_R & \frac{1}{sL}+G_R \end{bmatrix}$$

Ground node 4:

$$V_{ext} = \begin{bmatrix} sC & -sC+g & -g \\ -sC-g & sC & g \\ g & -g & \frac{1}{sL}+G_R \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix}$$

$$Y_{2port} = Y_{11} - Y_{12} Y_{12}^{-1} Y_{22}$$

$$= \begin{bmatrix} sC & -sC+g \\ -sC-g & sC \end{bmatrix} - \frac{1}{\frac{1}{sL}+G_R} \begin{bmatrix} -g \\ g \end{bmatrix} \begin{bmatrix} g & -g \end{bmatrix}$$

$$= \begin{bmatrix} sC & -sC+g \\ -sC-g & sC \end{bmatrix} - \frac{1}{\frac{1}{sL}+G_R} \begin{bmatrix} -g^2 & g^2 \\ g^2 & -g^2 \end{bmatrix}$$

$$Y_{2port} = \begin{bmatrix} sC + \frac{sLg^2}{1+sLG_R} & g-sC - \frac{sLg^2}{1+sLG_R} \\ -g-sC - \frac{sLg^2}{1+sLG_R} & sC + \frac{sLg^2}{1+sLG_R} \end{bmatrix} = Y(s)$$

$$I(s) = Y(s)$$

$$I(s) = \begin{bmatrix} \frac{sC}{g^2} + \frac{sL}{(1+sLG_R)} & -\frac{1}{g} + \frac{sC}{g^2} + \frac{sL}{(1+sLG_R)} \\ \frac{1}{g} + \frac{sC}{g^2} + \frac{sL}{(1+sLG_R)} & \frac{sC}{g^2} + \frac{sL}{(1+sLG_R)} \end{bmatrix}$$

Problem #2

• Even Part of matrix $A(s) = \frac{1}{2}(A(s) + A(-s))$

∴ Even Part

$$\text{of } Y(s) = \frac{1}{2}(Y(s) + Y(-s))$$

$$= \frac{1}{2} \left[\begin{bmatrix} \frac{sC + sLg^2}{1+sLG_R} & -\frac{1}{g} - \frac{sC}{1+sLG_R} \\ -\frac{1}{g} - \frac{sC}{1+sLG_R} & \frac{sC + sLg^2}{1+sLG_R} \end{bmatrix} + \begin{bmatrix} -\frac{sC - sLg^2}{1-sLG_R} & \frac{1}{g} + \frac{sC}{1-sLG_R} \\ \frac{1}{g} + \frac{sC}{1-sLG_R} & -\frac{sC - sLg^2}{1-sLG_R} \end{bmatrix} \right]$$

$$\text{Even part of } Y(s) = \begin{bmatrix} \frac{s^2 L^2 g^2 G_R}{s^2 L^2 G_R^2 - 1} & \frac{1}{g} - \frac{s^2 L^2 g^2 G_R}{s^2 L^2 G_R^2 - 1} \\ -\frac{1}{g} - \frac{s^2 L^2 g^2 G_R}{s^2 L^2 G_R^2 - 1} & \frac{s^2 L^2 g^2 G_R}{s^2 L^2 G_R^2 - 1} \end{bmatrix}$$

Similarly:

$$\text{Even part of } I(s) = \begin{bmatrix} \frac{s^2 L^2 G_R}{s^2 L^2 G_R^2 - 1} & \frac{s^2 L^2 G_R^2}{s^2 L^2 G_R^2 - 1} - \frac{1}{g} \\ \frac{s^2 L^2 G_R^2}{s^2 L^2 G_R^2 - 1} + \frac{1}{g} & \frac{s^2 L^2 G_R^2}{s^2 L^2 G_R^2 - 1} \end{bmatrix}$$

Zeros

$$1 - \frac{s^2 L^2 \omega_p^2}{s^2 L^2 \omega_p^2 - 1} = 0$$

$$-1 - \frac{s^2 L^2 \omega_p^2}{s^2 L^2 \omega_p^2 - 1} = 0$$

$$(1) \quad s^2 L^2 \omega_p^2 - 1 = s^2 L^2 \omega_p^2$$

$$-1 s^2 L^2 \omega_p^2 + 1 = s^2 L^2 \omega_p^2$$

$$s = \pm \frac{1}{L} \sqrt{\frac{1}{\omega_p(\omega_p - 1)}}$$

$$s = \pm \frac{1}{L} \sqrt{\frac{1}{\omega_p(\omega_p + 1)}}$$

$$s = 0$$

$$\therefore \text{Zero of } E_1(\omega) \Rightarrow s = 0, \pm \frac{1}{L} \sqrt{\frac{1}{\omega_p(\omega_p \pm 1)}}$$

$$\frac{s^2 L^2 \omega_p^2}{s^2 L^2 \omega_p^2 - 1} - \frac{1}{\omega} = 0$$

$$\frac{s^2 L^2 \omega_p^2}{s^2 L^2 \omega_p^2 - 1} - \frac{1}{\omega} = 0$$

$$s = 0$$

(2)

$$s = \pm \frac{1}{L} \sqrt{\frac{1}{\omega_p(\omega_p - 1)}}$$

$$s = \pm \frac{1}{L} \sqrt{\frac{1}{\omega_p(\omega_p + 1)}}$$

$$\text{Zero of } E_2(\omega) \Rightarrow s = 0, \pm \frac{1}{L} \sqrt{\frac{1}{\omega_p(\omega_p \pm 1)}}$$

It is only proportional to ω_p

Problem #3

With $C=G=0$ we obtain:

$$Y(s) = \begin{bmatrix} sLq^2 & q - sLq^2 \\ -q - sLq^2 & sLq^2 \end{bmatrix} \quad Z(s) = \begin{bmatrix} sL & sL - \frac{1}{q^2} \\ sL + \frac{1}{q} & sL \end{bmatrix} \quad \Delta Z = \frac{1}{q^2}$$

find $Z_L(s)$ in terms of $Z_{in}(s)$

$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} \quad \begin{aligned} I_2 &= -\frac{1}{Z_L} V_2 \\ V_2 &= -Z_L I_2 \end{aligned}$$

$$V_2 = Z_{21} I_1 + Z_{22} I_2 \quad (\text{row 2})$$

$$-Z_L I_2 = Z_{21} I_1 + Z_{22} I_2$$

$$I_2 = (-Z_{21}) / (Z_{22} + Z_L) I_1$$

$$V_1 = Z_{11} I_1 + Z_{12} I_2$$

$$V_1 = Z_{11} I_1 - Z_{12} Z_{21} (Z_{22} + Z_L)^{-1} I_1$$



$$\frac{V_1}{I_1} = Z_{in} = Z_{11} - \frac{Z_{12} Z_{21}}{Z_{22} + Z_L} \quad \longrightarrow \quad Z_L = \frac{Z_{in} Z_{22} - [Z_{11} Z_{22} - Z_{12} Z_{21}]}{Z_{11} - Z_{in}}$$

$$Z_L = \frac{Z_{in} Z_{22} - \Delta Z}{Z_{11} - Z_{in}}$$

Plug in for $Z(s)$

$$Z_L = \frac{Z_{in} sL - \frac{1}{q^2}}{sL - Z_{in}}$$

Problem 4

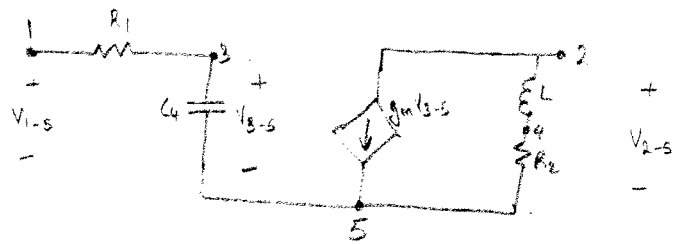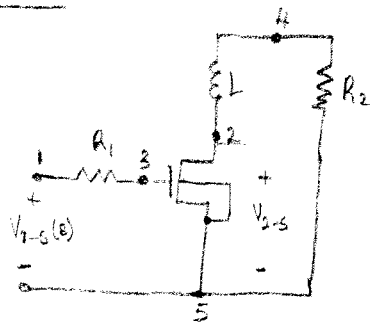

Find Y-2port:

$$\frac{R_1}{i_1 = G_1(V_1 - V_5)}$$

$$\frac{C_4}{i_5 = sC_4(V_5 - V_3)}$$

$$\frac{g_m}{i_2 = g_m(V_3 - V_5)}$$

$$\frac{1}{i_2 = \frac{1}{sL}(V_2 - V_4)}$$

$$\frac{R_2}{i_5 = G_2(V_5 - V_4)}$$

→ Get indefinite admittance:

$$Y_{\text{indef}} = \begin{bmatrix} G_1 & 0 & -G_1 & 0 & 0 \\ 0 & 1/sL & g_m & -1/sL & 0 \\ -G_1 & 0 & G_1 + sC_4 & 0 & -sC_4 \\ 0 & 1/sL & 0 & G_2 + 1/sL & -G_2 \\ 0 & 0 & -g_m - sC_4 & -G_2 & g_m + sC_4 + G_2 \end{bmatrix}$$

→ Input/output will be in terms of V_5 so let's take it as common ground → $Y_{4 \times 4}$
 → Now eliminate nodes 3 and 4 → $Y_{2\text{-port}}$

$$Y_{4 \times 4} = \begin{bmatrix} G_1 & 0 & -G_1 & 0 \\ 0 & 1/sL & g_m & -1/sL \\ -G_1 & 0 & G_1 + sC_4 & 0 \\ 0 & -1/sL & 0 & G_2 + 1/sL \end{bmatrix} = \begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix}$$

$$Y_{2\text{-port}} = Y_{11} - Y_{12} Y_{22}^{-1} Y_{21}$$

$$Y_{2\text{-port}} = \begin{bmatrix} \frac{G_1 sC_4}{G_1 + sC_4} & 0 \\ \frac{g_m G_1}{G_1 + sC_4} & \frac{G_2}{sL G_2 + 1} \end{bmatrix}$$

∴

$$\begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = Y_{2-port} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix}$$

with open-circuit load, $i_2 \rightarrow 0$

∴ from row #2:

$$0 = \frac{g_m g_1}{g_1 + sC_4} v_1 + \frac{g_2}{sLg_2 + 1} v_2$$

→ solve for v_2/v_1 :

$$\frac{v_2}{v_1}(s) = \frac{-g_m g_1 (sLg_2 + 1)}{g_2 (g_1 + sC_4)} = \frac{-g_m (sL + 1/g_2)}{1 + sC_4/g_1}$$

$$\therefore T(s) = \frac{-g_m (R_2 + sL)}{1 + sC_4 R_1}$$

compare to result from KCL/KVL on small signal

$$v_{gs} = v_1 \frac{1/sC_4}{1/sC_4 + R_1} \quad -g_m v_{gs} = \frac{v_2}{R_2 + sL}$$

$$\Rightarrow -g_m \frac{1}{sC_4 R_1 + 1} v_1 = v_2 \frac{1}{R_2 + sL} \quad \longrightarrow \quad \frac{v_2}{v_1} = \frac{-g_m (R_2 + sL)}{1 + sC_4 R_1}$$

b) $C_4 = C \quad R_1 = R_2 = R \quad R = C = 1$

$$\therefore T(s) = \frac{-g_m (1 + sL)}{1 + s}$$

poles: $s = -1$

zeros: $s = -1/L$

c) Step Response: $V(s) = \frac{1}{s}$

$$V_{2-s}(s) = \frac{1}{s} \cdot \frac{-g_m(1+sL)}{1+s} = \frac{-g_m}{s} + \frac{g_m(1-L)}{1+s}$$

$$\mathcal{L}^{-1}\left[\frac{-g_m}{s} + \frac{1-L}{1+s}\right] = [-g_m + g_m(1-L)e^{-t}]u(t)$$

$$\therefore V_{2-s}(t) = [-g_m + g_m(1-L)e^{-t}]u(t)$$

Impulse Response

$$\frac{d}{dt}V_{2-s}(t) = -g_mL\delta(t) - g_m(1-L)e^{-t}u(t)$$