

610 Fall 20123– Homework 6 Due Th 10/24/13

1. (20 points) (Lossless Synthesis) Synthesize by the two Cauer and the two Foster forms the lossless admittances and compare the results.

$$y_1(s) = \frac{s(s^2 + 4)}{(s^2 + 1)(s^2 + 5)}$$

$$y_2(s) = \frac{(s^2 + 1)(s^2 + 5)}{s(s^2 + 4)}$$

2. (20 points) (RC synthesis) Replace each L by an R in the above syntheses and give the resulting RC admittances. Compare degrees of the different $y(s)$ obtained, including LC versus RC.

3. (25 points) (Minimum $y(s)$) Show that $y(s) = [s^2 + s + 2] / [s^2 + s + 1]$ is PR with no pole or zero on the $j\omega$ axis. Sketch $\text{Re}(y(j\omega))$ and find the minimum value of $\text{Re}(y(j\omega)) = g$. Show that $z_1(s) = 1/[y(s) - g]$ is PR but still without a pole on the $j\omega$ axis; locate the even part zeroes of $z_1(s)$ and $y(s)$ and compare.

3. (35 points) (Synthesis from state equations) Set up the companion matrix form of state-variable equations for the admittance $y(s) = \frac{3s^2 + 2s + 1}{s^2 + 3}$. Check if this is a PR $y(s)$.

Synthesize the resulting 3-port admittance matrix, loaded in two unit capacitors, and check by analyzing the circuit that $y(s)$ results.

(Research type problem). Show that the following is positive-real and discuss the position and nature of its singularities (note that a limit of poles is an essential singularity and all real numbers are limits of rational numbers).

$$y(s) = \sum_{k=1}^{\infty} \sum_{m=1}^{\infty} \coth\left(s \frac{k}{m}\right)$$

Related to this is that the following formulas hold for the lossless positive-real \tanh and \coth which are related to transmission lines.

$$\tanh(s) = 2s \left[\sum_{n=0}^{\infty} \frac{1}{(s^2 + (n + \frac{1}{2})^2 \pi^2)} \right]$$

$$\coth(s) = \frac{1}{s} + 2s \left[\sum_{n=1}^{\infty} \frac{1}{(s^2 + (n\pi)^2)} \right]$$