

Problem #1

$$y_1(s) = \frac{s(s^2+4)}{(s^2+1)(s^2+5)} = \frac{s^3+4s}{s^4+6s^2+5}$$


$$y_2(s) = \frac{(s^2+1)(s^2+5)}{s(s^2+4)} = \frac{s^4+6s^2+5}{s^3+4s}$$

1st Case

$$Z_1(s) = \frac{s^4+6s^2+5}{s^3+4s}$$

$$\begin{array}{r} s \\ s^3+4s \overline{) s^4+6s^2+5} \\ \underline{s^4+4s^2} \\ 2s^2+5 \end{array} \quad \begin{array}{r} \frac{s}{2} \\ s^3+4s \overline{) s^3+\frac{5}{2}s} \\ \underline{s^3+4s} \\ \frac{3}{2}s \end{array} \quad \begin{array}{r} \frac{4s}{3} \\ \frac{3}{2}s \overline{) 2s^2+5} \\ \underline{2s^2} \\ 5 \end{array} \quad \begin{array}{r} \frac{3s}{10} \\ 5 \overline{) 5} \\ \underline{5} \\ 0 \end{array}$$
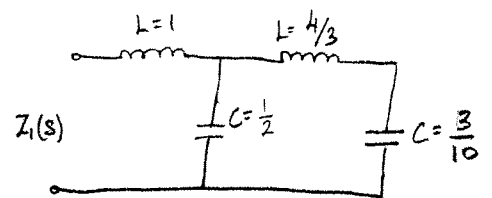
$$Z_1(s) = s + \frac{1}{\frac{1}{2}s + \frac{1}{\frac{4}{3}s + \frac{1}{\frac{3}{10}s}}}$$




2nd Case

$$Z_1(s) = \frac{5+6s^2+s^4}{4s+s^3}$$

$$\begin{array}{r} \frac{5}{4s} \\ 4s+s^3 \overline{) 5+6s^2+s^4} \\ \underline{5+\frac{5}{4}s^2} \\ \frac{19}{4}s^2+s^4 \end{array} \quad \begin{array}{r} \frac{16}{19s} \\ \frac{19}{4}s^2+s^4 \overline{) 4s+s^3} \\ \underline{4s+\frac{16}{19}s^3} \\ \frac{19}{4}s^2+\frac{19}{4}s^4 \end{array} \quad \begin{array}{r} \frac{19^2}{12s} \\ \frac{19}{4}s^2+\frac{19}{4}s^4 \overline{) 4s+\frac{16}{19}s^3} \\ \underline{4s+\frac{16}{19}s^3} \\ \frac{19}{4}s^2+\frac{19}{4}s^4 \end{array} \quad \begin{array}{r} \frac{3}{19s} \\ \frac{19}{4}s^2+\frac{19}{4}s^4 \overline{) \frac{19}{4}s^2+\frac{19}{4}s^4} \\ \underline{\frac{19}{4}s^2+\frac{19}{4}s^4} \\ 0 \end{array}$$

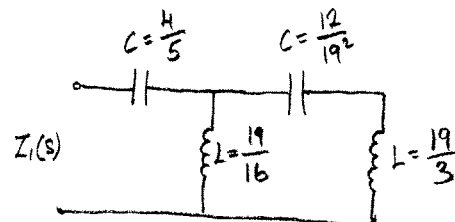
$$Z_1(s) = \frac{5}{4s} + \frac{1}{\frac{16}{19s} + \frac{1}{\frac{19^2}{12s} + \frac{1}{\frac{3}{19s}}}}$$



1st Foster

$$Z_1(s) = \frac{(s^2+1)(s^2+5)}{s(s^2+4)} = k_{\infty}s + \frac{k_0}{s} + \frac{2k_2s}{s^2+4}$$

$$\left. \begin{array}{l} s=0 \quad 5 = 4k_0 \rightarrow k_0 = \frac{5}{4} \\ s^2=-4 \quad -3 = -8k_2 \rightarrow k_2 = \frac{3}{8} \\ s^2=1 \quad 12 = 5k_{\infty} + 5k_0 + 2k_2 \rightarrow k_{\infty} = 1 \end{array} \right\} \begin{array}{l} \therefore \\ Z_1(s) = s + \frac{5}{4s} + \frac{2\left(\frac{3}{8}\right)s}{s^2+4} \\ L_1 = k_{\infty} \quad L_2 = \frac{2k_2}{\omega_2^2} \quad C_2 = \frac{1}{2k_2} \\ C_1 = \frac{1}{k_0} \quad \omega_2^2 = 4 \end{array}$$

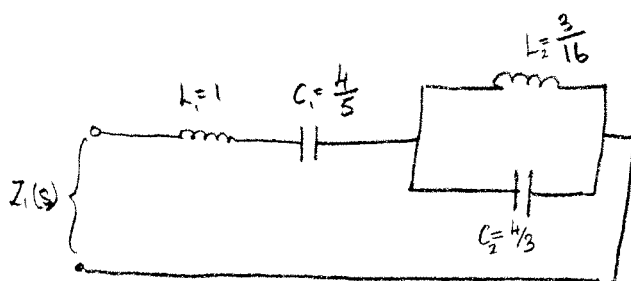

2nd Foster

$$Y_1(s) = \frac{s(s^2+4)}{(s^2+1)(s^2+5)} = k'_{\infty}s + \frac{k'_0}{s} + \frac{2k'_2s}{s^2+1} + \frac{2k'_4s}{s^2+5}$$

$$s(s^2+4) = k'_{\infty}s(s^2+1)(s^2+5) + \frac{k'_0}{s}(s^2+1)(s^2+5) + 2k'_2s(s^2+5) + 2k'_4s(s^2+1)$$


$$s^2=-1 \quad 3\sqrt{-1} = 2k'_2\sqrt{-1}(4) \rightarrow k'_2 = \frac{3}{8}$$

$$s^2=-5 \quad -\sqrt{-1} = 2k'_4\sqrt{-1}(-4) \rightarrow k'_4 = \frac{1}{8}$$

$$\left. \begin{array}{l} s=1 \quad 5 = 12k'_{\infty} + 12k'_0 + 5 \rightarrow k'_0 = -k'_{\infty} \\ s=2 \quad 16 = 90k'_{\infty} + \frac{45}{2}k'_0 + 16 \rightarrow k'_0 = -2k'_{\infty} \end{array} \right\} k'_0 = k'_{\infty} = 0$$

$$\therefore Y_1(s) = \frac{2\left(\frac{3}{8}\right)s}{s^2+1} + \frac{2\left(\frac{1}{8}\right)s}{s^2+5}$$
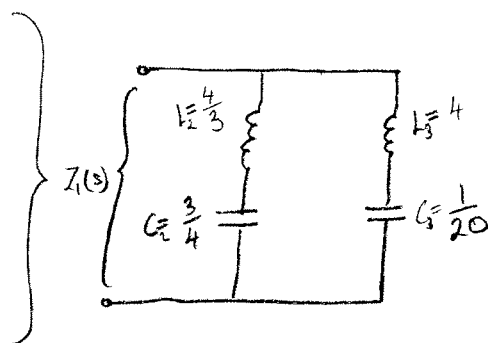
$$\begin{array}{llll} \omega_2^2 = 1 & C_1 = k'_0 = 0 & L_2 = \frac{1}{2k'_2} & L_3 = \frac{1}{2k'_4} \\ \omega_4^2 = 5 & L_1 = \frac{1}{k'_0} = \infty & C_2 = \frac{2k_2}{\omega_2^2} & C_3 = \frac{2k_4}{\omega_4^2} \end{array}$$




$y_2(s)$

1st Foster

$Z_2(s) = y_1(s) \therefore$ Use result of 2nd Foster on $y_1(s)$:

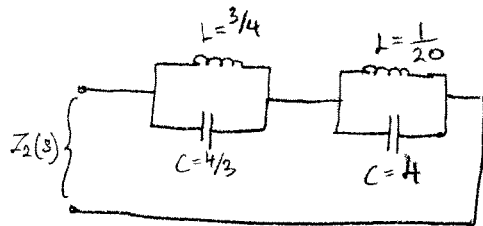
$$Z_2(s) = \frac{\frac{3}{4}s}{s^2+1} + \frac{\frac{1}{4}s}{s^2+5} = \frac{1}{\frac{4}{3}s + \frac{4}{3s}} + \frac{1}{4s + \frac{20}{s}}$$



2nd Foster

$y_2(s) = Z_2(s) \therefore$ Use result of 1st Foster on $y_1(s)$:
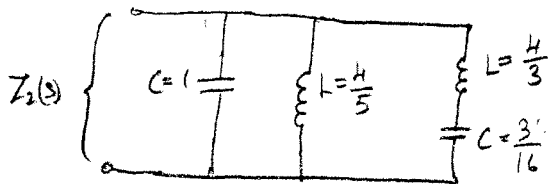
$$y_2(s) = s + \frac{5}{4s} + \frac{\frac{3}{4}s}{s^2+4} = s + \frac{5}{4s} + \frac{1}{\frac{4s}{3} + \frac{16}{3s}}$$




1st Cauer

$$y_2(s) = \frac{s^4 + 6s^2 + 5}{s^3 + 4s}$$

(Use result of)

- perform continued fraction expansion exactly as 1st Cauer for $Z_1(s)$
- result is an admittance instead of Impedance:
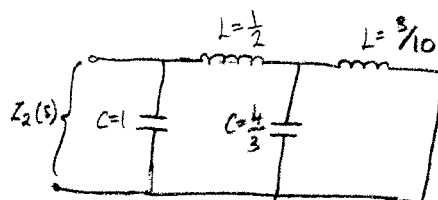
$$y_2(s) = s + \frac{1}{\frac{1}{2}s + \frac{1}{\frac{4}{3}s + \frac{1}{\frac{3}{10}s}}}$$




2nd Cauer

$$y_2(s) = \frac{5 + 6s^2 + s^4}{4s + s^3}$$

(Use result of)

- Perform continued fraction expansion exactly as 2nd Cauer for $Z_1(s)$:
- result is an admittance
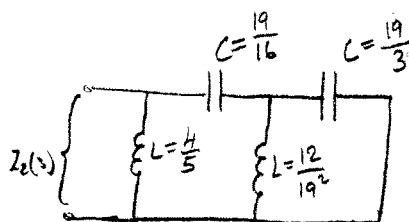
$$\therefore y_2(s) = \frac{5}{4s} + \frac{1}{\frac{16}{19s} + \frac{1}{\frac{19^2}{12s} + \frac{1}{\frac{3}{19s}}}}$$




• Comparing the Cauer forms, we see that Capacitors and Inductors between y_1 and y_2 have been interchanged. Also, the leading component appears in parallel in y_2 while it would be in series in y_1 .

• Comparing the Foster forms, we again see that the capacitor and inductor values have interchanged and series connections become parallel and vice versa. This is due to the fact that $y_1(s) = \frac{1}{y_2(s)}$


Problem #2

- Replacing each L by an R, we obtain the following circuits:

$y_1(s)$

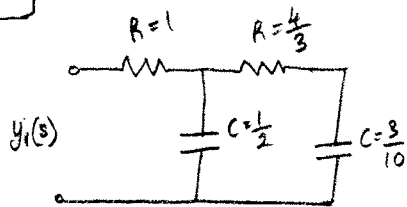

1st Cover

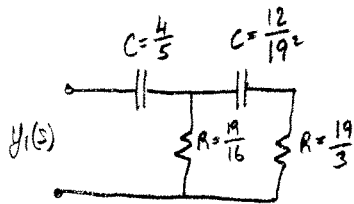

2nd Cover

From each RC circuit we obtain:


$$y_1(s) = \frac{s(s+4)}{(s+1)(s+5)}$$

$$y_2(s) = \frac{(s+1)(s+5)}{s+4}$$


Compared to the original LC:

$$y_1(s) = \frac{s(s^2+4)}{(s^2+1)(s^2+5)}$$
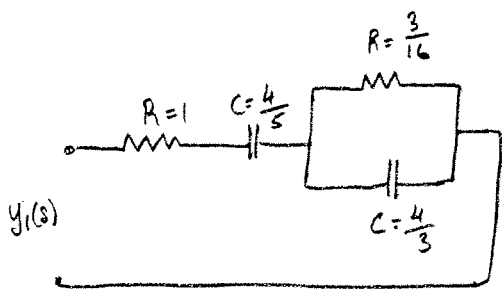
$$y_2(s) = \frac{(s^2+1)(s^2+5)}{s(s^2+4)}$$




1st Foster

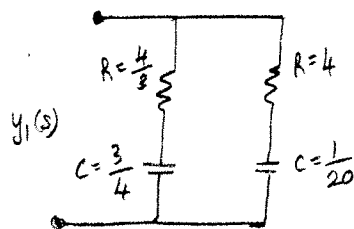


2nd Foster

$y_2(s)$

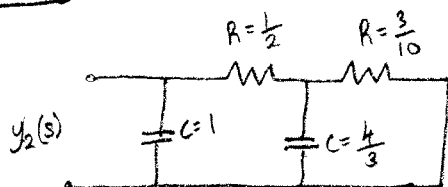

1st Cover

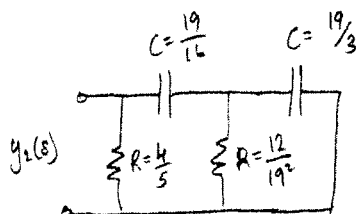


2nd Cover


• for $y_1(s)$ the degree of the numerator and denominator have reduced compared to the original LC circuit

• the same thing is observed with $y_2(s)$, however we see that the denominator degree has dropped by two

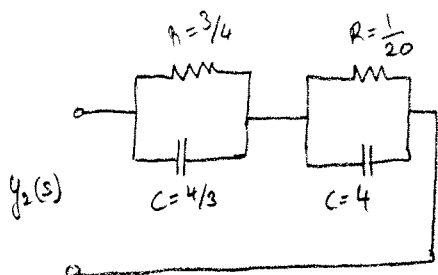• therefore $y_1(s)$ and $y_2(s)$ in the RC case are no longer inverses of each other.



1st Foster

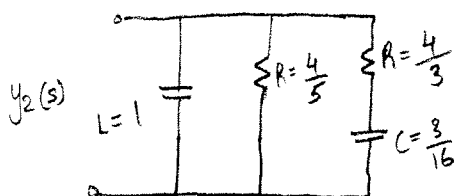

2nd Foster

Problem # 3

$$y(s) = \frac{s^2 + s + 2}{s^2 + s + 1}$$

$$y(j\omega) = \frac{2 - \omega^2 + j\omega}{1 - \omega^2 + j\omega} = \frac{(2 - \omega^2 + j\omega)(1 - \omega^2 - j\omega)}{(1 - \omega^2 + j\omega)(1 - \omega^2 - j\omega)} = \frac{\omega^4 - 2\omega^2 + 2 - j\omega}{\omega^4 - \omega^2 + 1}$$

$$\operatorname{Re}[y(j\omega)] = \frac{\omega^4 - 2\omega^2 + 2}{\omega^4 - \omega^2 + 1} = f(\omega)$$

Find minimum:

$$\left. \frac{df}{d\omega} \right|_{\omega=\omega_0} = \frac{2\omega^3(\omega^2 - 2)}{(\omega^4 - \omega^2 + 1)^2} = 0 \rightarrow \omega_0 = \pm\sqrt{2}, 0$$

from plot, $\omega=0$ is a maximum
 $\therefore \omega_0 = \pm\sqrt{2}$

$$g = f(\omega_0) = \frac{2^2 - 4 + 2}{2^2 - 2 + 1} = \frac{2}{3}$$

Show $y(s)$ is PR:

a) Find poles:

$$s^2 + s + 1 = 0 \rightarrow s_{1,2} = \frac{-1}{2} \pm j\frac{\sqrt{3}}{2}$$

$\hookrightarrow$ no poles in RHP $\checkmark$

b) no poles on $j\omega$ axis $\checkmark$

$$c) \operatorname{Re}[y(j\omega)] = \frac{\omega^4 - 2\omega^2 + 2}{\omega^4 - \omega^2 + 1} = \frac{(\omega^2 - 1)^2 + 1}{(\omega^2 - \frac{1}{2})^2 + \frac{3}{4}} \geq 0 \text{ for } 0 \leq \omega < \infty \checkmark$$

$\therefore y(s)$ is PR

Check zeroes/poles

$$s^2 + s + 2 \rightarrow s_{1,2} = \frac{-1}{2} \pm j\frac{\sqrt{7}}{2}$$

$$s^2 + s + 1 \rightarrow s_{1,2} = \frac{-1}{2} \pm j\frac{\sqrt{3}}{2}$$

No poles or zeroes on $j\omega$ axis

$Z_1(s)$

$$Z_1(s) = \frac{1}{y(s) - g} = \frac{1}{\frac{s^2 + s + 2}{s^2 + s + 1} - \frac{2}{3}} = \frac{3(s^2 + s + 1)}{s^2 + s + 4}$$

Show $Z_1(s)$ is PR:

a) poles: $s_{1,2} = \frac{-1}{2} \pm j\frac{\sqrt{15}}{2}$

$\hookrightarrow$ no poles in RHP $\checkmark$

b) no poles on $j\omega$ axis $\checkmark$

$$c) \operatorname{Re}[Z_1(j\omega)] = \frac{3(\omega^2 - 2)^2}{\omega^4 - 7\omega^2 + 16} = \frac{3(\omega^2 - 2)^2}{(\omega^2 - 4)^2 + \omega^2} \geq 0 \text{ for } 0 \leq \omega < \infty \checkmark$$

$\therefore Z_1(s)$ is PR

Even part zeroes

$$2 \sum_v [y(s)] = y(s) + y(-s) = \frac{2(s^4 + 2s^2 + 2)}{s^4 + s + 1} = 0$$

$$\Rightarrow s^4 + 2s^2 + 2 = 0$$

$$s_{1,2}^2 = -1 \pm j$$


$$s_{1,2} = \pm \sqrt{-1 \pm j}$$

$$2 \sum_v [z_1(s)] = z_1(s) + z_1(-s) = \frac{6(s^2 + 2)^2}{s^4 + 7s^2 + 16} = 0$$

$$(s^2 + 2)^2 = 0$$

$$s_{1,2}^2 = -2$$

$$s_{1,2} = \pm j\sqrt{2}$$

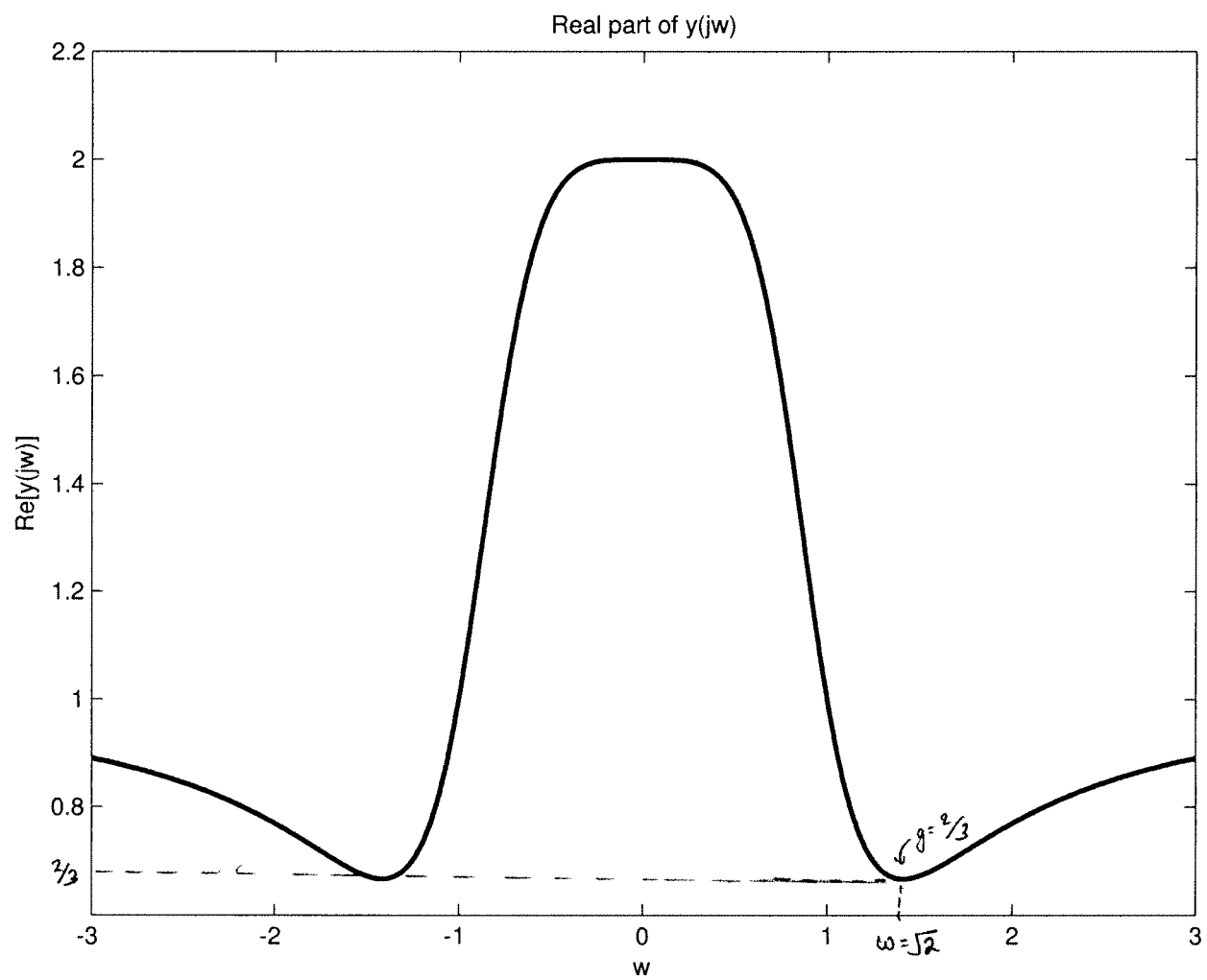

Problem #4

$$y(s) = T(s) = \frac{3s^2 + 2s + 1}{s^2 + 3} = 3 + \frac{2s - 8}{s^2 + 3} = D + \frac{C_1 s + C_0}{s^2 + a_1 s + a_0}$$

- map to state variable matrix form:

$$\begin{bmatrix} \dot{x}_1 \\ \dot{x}_2 \end{bmatrix} = \begin{bmatrix} 0 & 1 \\ -a_0 & -a_1 \end{bmatrix} \begin{bmatrix} x_1 \\ x_2 \end{bmatrix} + \begin{bmatrix} 0 \\ 1 \end{bmatrix} u \Rightarrow \begin{bmatrix} \dot{x}_1 \\ \dot{x}_2 \end{bmatrix} = \begin{bmatrix} 0 & 1 \\ -3 & 0 \end{bmatrix} \begin{bmatrix} x_1 \\ x_2 \end{bmatrix} + \begin{bmatrix} 0 \\ 1 \end{bmatrix} u \quad (\dot{x} = Ax + Bu)$$


$$y = [C_0 \ C_1] \begin{bmatrix} x_1 \\ x_2 \end{bmatrix} + Du \Rightarrow y = [-8 \ 2] \begin{bmatrix} x_1 \\ x_2 \end{bmatrix} + 3u \quad (y = Cx + Du)$$

- $T(s) = \frac{\text{output}}{\text{input}} = \frac{y}{u} \Rightarrow y = i_0 \quad u = V_{in}$

- Set up 3-port admittance loaded in with unit capacitors:

$$\begin{bmatrix} -\dot{x} \\ y \end{bmatrix} = \begin{bmatrix} -A & -B \\ C & D \end{bmatrix} \begin{bmatrix} x \\ u \end{bmatrix} \Rightarrow \begin{bmatrix} i_1 \\ i_2 \\ i_0 \end{bmatrix} = \underbrace{\begin{bmatrix} 0 & -1 & 0 \\ 3 & 0 & -1 \\ -8 & 2 & 3 \end{bmatrix}}_{Y_{3 \text{ port}}} \begin{bmatrix} V_1 \\ V_2 \\ V_{in} \end{bmatrix}$$

with corresponding circuit:

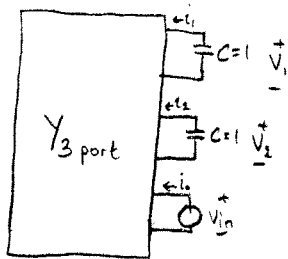

- Check result:

$$\left. \begin{aligned} i_1 &= -V_2 \\ i_2 &= 3V_1 - V_{in} \\ i_0 &= -8V_1 + 2V_2 + 3V_{in} \end{aligned} \right\} \text{from 3-port admittance}$$

$$\left. \begin{aligned} i_1 &= -sCV_1 = -sV_1 \\ i_2 &= -sCV_2 = -sV_2 \end{aligned} \right\} \text{at ports 1 and 2}$$

$$\therefore V_2 = sV_1$$

$$-sV_2 = 3V_1 - V_{in} \rightarrow V_1 = V_{in} \frac{1}{s^2 + 3}$$

$$V_2 = V_{in} \frac{s}{s^2 + 3}$$

$$i_0 = V_{in} \left[\frac{-8}{s^2 + 3} + \frac{2s}{s^2 + 3} + 3 \right]$$

$$T(s) = \frac{i_0}{V_{in}} = \frac{3s^2 + 2s + 1}{s^2 + 3}$$

$$y(s) = \frac{3s^2 + 2s + 1}{s^2 + 3}$$

Check PR:

$$y(s) = \frac{3s^2 + 2s + 1}{s^2 + 3}$$

poles: $s = \pm j\sqrt{3}$

$$\text{Residue}_{s=j\sqrt{3}}[y(s)] = \frac{-9 + 1 + j2\sqrt{3}}{j2\sqrt{3}} = 1 + \frac{j4}{\sqrt{3}}$$

$$\text{Residue}_{s=-j\sqrt{3}}[y(s)] = \frac{-9 + 1 - j2\sqrt{3}}{-j2\sqrt{3}} = 1 - \frac{j4}{\sqrt{3}}$$

Residues of poles on $j\omega$ axis are
not real $\rightarrow$ function is not PR