

610 Fall 2013– Homework 7 Due Th 10/31/13

1. (30 points) (Maximally flat degree 3)  
Obtain a low pass and high pass degree 3 maximally flat transfer functions.
2. (30 points) ( $V_o/V_i$  transfer function)  
Use the transfer functions of problem 1 to synthesize degree 3 low and high pass maximally flat  $V_{out}/V_{in}(s)$  via  $V_{out}/V_{in} = -y_{21}/(1+y_{22})$ .
3. (40 points) (Sensitivity via adjoint)  
Using the adjoint circuit, for the low-pass circuit of problem 2 find the sensitivity of  $V_{out}/V_{in}$  to the (first input side) capacitor and then to the (first input side) inductor.