

Homework #7

ENEE 610

Problem #1

For odd n , roots will be as follows:

$$S_k = e^{j \frac{2k\pi}{2n}}$$

$$= e^{j \frac{k\pi}{n}}$$

$$S_k = e^{j \frac{k\pi}{3}} \quad k = 0, \pm 1, \pm 2, \dots, \pm(2n-1)$$

k	$\frac{k\pi}{3}$	
0	0	x
+1	$\pi/3$	x
-1	$-\pi/3$	x
+2	$2\pi/3$	o
-2	$-2\pi/3$	x
+3	π	o
-3	$-\pi$	x
+4	$4\pi/3$	o
-4	$-4\pi/3$	x
+5	$5\pi/3$	x
-5	$-5\pi/3$	x


We want roots in left half of complex plane for stability and for certain k , we obtain mirrored points

Therefore we remain with the following k

$$k=2 \rightarrow e^{j \frac{2\pi}{3}} = \frac{-1}{2} + j \frac{\sqrt{3}}{2}$$

$$k=3 \rightarrow e^{j\pi} = -1$$
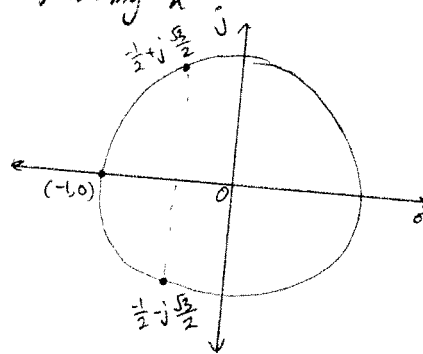
$$k=4 \rightarrow e^{j \frac{4\pi}{3}} = \frac{-1}{2} - j \frac{\sqrt{3}}{2}$$



$$\therefore T(s) = (s - [\frac{-1}{2} + j \frac{\sqrt{3}}{2}]) (s - [\frac{-1}{2} - j \frac{\sqrt{3}}{2}]) (s - (-1))$$

$$= s^3 + 2s^2 + 2s + 1$$

$$T(s) = \frac{1}{s^3 + 2s^2 + 2s + 1} \quad (\text{low pass})$$

For high pass, replace s with $\frac{1}{s}$:

$$T(s) = \frac{1}{(\frac{1}{s})^3 + \frac{2}{s^2} + \frac{2}{s} + 1}$$

$$T(s) = \frac{s^3}{s^3 + 2s^2 + 2s + 1} \quad (\text{high pass})$$

Problem # 2

Low Pass:

$$T(s) = \frac{1}{s^3 + 2s^2 + 2s + 1} = \frac{\frac{1}{(s^3 + 2s)}}{1 + \frac{2s^2 + 1}{s^3 + 2s}} = \frac{-y_{21}}{1 + \frac{y_{22}}{G_L}}$$


$$\frac{y_{22}}{G_L} = y_{22} = \frac{2s^2 + 1}{s^3 + 2s} \rightarrow Z_{22} = \frac{s^3 + 2s}{2s^2 + 1}$$

1st Cauer:


$$\begin{array}{c} \frac{3}{2} \\ 2s^2 + 1 \sqrt{\frac{s^3 + 2s}{s^3 + \frac{3}{2}}} \quad \frac{4s}{3} \\ \frac{3s}{2} \sqrt{\frac{2s^2 + 1}{2s^3}} \quad \frac{2s}{2} \\ 1 \sqrt{\frac{3s}{2}} \quad \frac{3s}{2} \\ \frac{3s}{2} \\ 0 \end{array}$$

$$\Rightarrow Z_{22} = \frac{s}{2} + \frac{1}{\frac{4s}{2} + \frac{1}{\frac{3s}{2}}}$$

So we obtain:

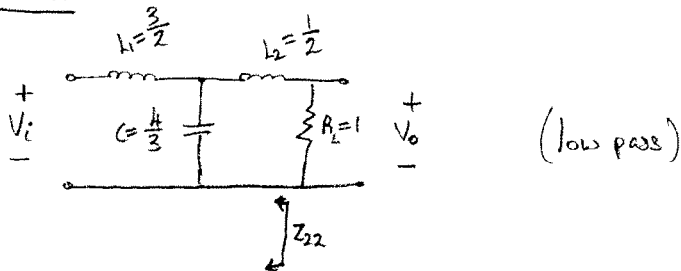


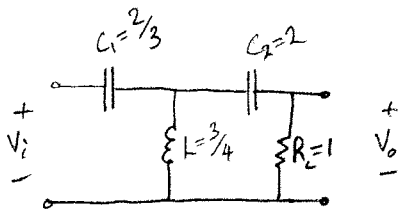To get a high pass circuit we replace capacitors with inductors and vice versa:




Problem #3

Original Circuit:

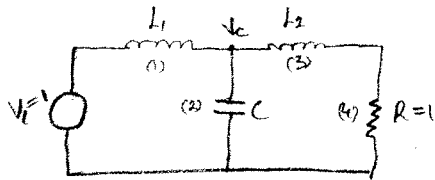

Adjoint Circuit:

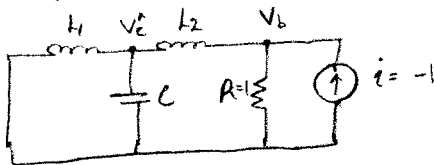

$$\frac{dT(s)}{dx} = \mathbf{V}_x^T \frac{\Delta \mathbf{Y}^T}{\Delta x} \mathbf{V}_x \quad \left[\begin{array}{l} \text{change in } T(s) \text{ with respect} \\ \text{to changes in component } x \end{array} \right]$$

$$S = \frac{\frac{dT(s)}{dx}}{\frac{T(s)}{x}} = \frac{x}{T(s)} \cdot \frac{dT(s)}{dx}$$

$$\mathbf{I}_b = \mathbf{Y} \mathbf{V}_b$$

$$\mathbf{I}_b = \begin{bmatrix} \frac{1}{sL_1} & 0 & 0 & 0 \\ 0 & sC & 0 & 0 \\ 0 & 0 & \frac{1}{sL_2} & 0 \\ 0 & 0 & 0 & \frac{1}{R} \end{bmatrix} \mathbf{V}_b$$

∴ if we look at C:

$$\frac{\Delta \mathbf{Y}}{\Delta C} = \begin{bmatrix} 0 & 0 & 0 & 0 \\ 0 & s & 0 & 0 \\ 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 \end{bmatrix}$$

The only non-zero element is at (2,2), so to compute $\mathbf{V}_x^T \frac{\Delta \mathbf{Y}^T}{\Delta x} \mathbf{V}_x$, we need only look at element (2) of $\mathbf{V}_x^T$ and $\mathbf{V}_x^a \rightarrow$ i.e. the voltage across component x

∴ from original circuit:

$$\frac{V_1 - V_c}{sL_1} = \frac{V_c}{(sL_2 + R) \parallel \frac{1}{sC}} \rightarrow V_c = V_x^T = \frac{1}{s^2 L_1 L_2 C + \frac{sL_1}{sL_2 + 1} + 1}$$

from adjoint circuit:

$$\left. \begin{array}{l} i = \frac{V_b}{R} + \frac{V_b}{sL_2 + sL_1 \parallel \frac{1}{sC}} \\ \frac{V_b - V_c^a}{sL_2} = \frac{V_c^a}{sL_1 \parallel \frac{1}{sC}} \end{array} \right\} V_c^a = V_x^a = \frac{-sL_1}{s^3 L_1 L_2 C + s^2 L_1 C + s(L_1 + L_2) + 1} = \frac{-3s}{2(s^3 + 2s^2 + 2s + 1)}$$

$$S = \frac{x}{T(s)} \cdot V_c \frac{\Delta Y}{\Delta x} V_c^a$$

$$S = \frac{-(s^3 L_1 L_2 C + s^2 L_1 C)}{s^3 L_1 L_2 C + s^2 L_1 C + s(L_1 + L_2) + 1} = \frac{-(3s^3 C + 6s^2 C)}{3s^3 C + 6s^2 C + 8s + 4} = -\frac{s^3 + 2s^2}{s^3 + 2s^2 + 2s + 1}$$

Similarly for inductor L_1 :

$$\left. \begin{array}{l} \frac{\Delta Y}{\Delta L_1} = \frac{-1}{sL_1^2} \\ V_L = V_c - V_c^a = V_c - 1 \\ V_L^a = V_c^a \end{array} \right\} S = \frac{s^3 L_1 L_2 C + s^2 L_1 C + sL_1}{s^3 L_1 L_2 C + s^2 L_1 C + s(L_1 + L_2) + 1} = \frac{4s^3 L_1 + 8s^2 L_1 + 6sL_1}{4s^3 L_1 + 8s^2 L_1 + s(6L_1 + 3) + 6} = -\frac{2s^3 + 4s^2 + 3s}{2s^3 + 4s^2 + 4s + 2}$$