
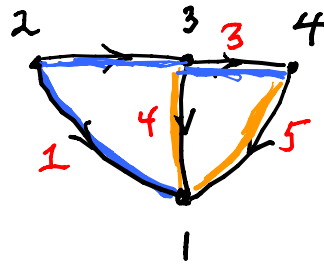


For next week see if you can get PSpice especially look @ Gvalue = VCCS (gain = any function) & PARAM

Graphs of a network

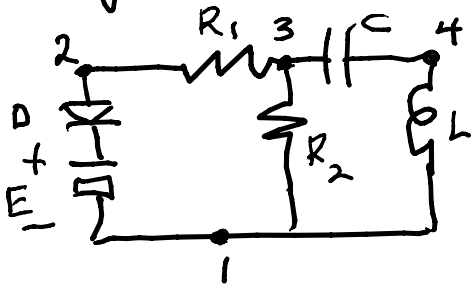

• = node, # = $n = 4$

— = branches, # $b = 5$

oriented branch $\xrightarrow{+}$
 \xrightarrow{i}
 $+ v -$

$v \times i =$ power into branch component

— = tree branches
 # = $t = 3 = n - 1$

— = co-tree = link
 # = l

$$\Rightarrow b - l = t = n - 1$$


$$t = \# \text{ of KCL} = n - 1$$

$$l = \# \text{ of KVL} = b - t = b - (n - 1)$$

KCL = Σ currents into a sphere \Rightarrow circle in projection onto the plane
 $= 0$

do for each tree branch


cut sets
C

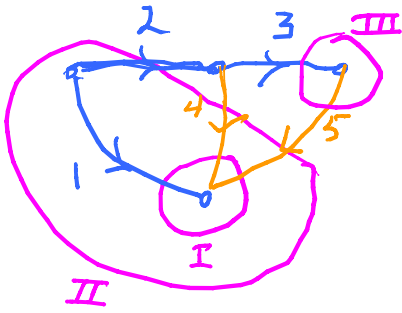

$$\begin{matrix} \text{I} \\ \text{II} \\ \text{III} \end{matrix} \begin{bmatrix} 0 \\ 0 \\ 0 \end{bmatrix} = \begin{bmatrix} 1 & 0 & 0 & 1 & 1 \\ 0 & 1 & 0 & -1 & -1 \\ 0 & 0 & 1 & 0 & -1 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \\ i_4 \\ i_5 \end{bmatrix} \left. \vphantom{\begin{bmatrix} 0 \\ 0 \\ 0 \end{bmatrix}} \right\} i_t$$


$\begin{matrix} \text{I}_3 \\ \text{II}_3 \\ \text{III}_3 \end{matrix} = \begin{matrix} 0_t \\ 0_t \\ 1_t \end{matrix}$

KVL for links

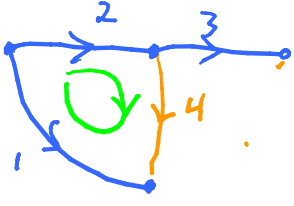

Tie sets
T

KVL link 2

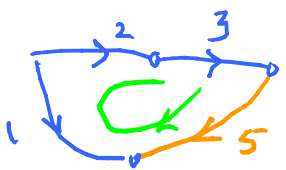

$$\begin{matrix} \text{link 1} \\ \text{link 2} \end{matrix} \begin{bmatrix} 0 \\ 0 \end{bmatrix} = \begin{bmatrix} -1 & 1 & 0 \\ -1 & 1 & 1 \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \\ v_3 \\ v_4 \\ v_5 \end{bmatrix} \left. \vphantom{\begin{bmatrix} 0 \\ 0 \end{bmatrix}} \right\} i_l$$

$\begin{matrix} 0_l \\ 0_l \end{matrix} = \begin{matrix} 0_2 \\ 0_2 \end{matrix} \quad v_T = \text{transpose} \quad \begin{matrix} 1_2 \\ 1_l \end{matrix}$

KCL $0_t = C \cdot i_b$ C is $t \times b$, cut set matrix, $\{0, 1, -1\}$ entries
 KVL $0_l = T \cdot v_b$ T is $l \times b$, tie set matrix, $\{0, 1, -1\}$ entries

$$P_{in}(t) = v_b^T \cdot i_b = 0$$

To see: given v_t we know all voltages, so assume

$$v_b = M_v \cdot v_t, \quad M \text{ is } b \times t; \quad i_b = M_i \cdot i_l$$

$$v_b = \begin{bmatrix} v_t \\ v_l \end{bmatrix} = \begin{bmatrix} 1_t \\ M_{21} \end{bmatrix} v_t \quad i_b = \begin{bmatrix} i_t \\ i_l \end{bmatrix} = \begin{bmatrix} M_{11} \\ 1_l \end{bmatrix} i_l$$

$$P_{in} = v_b^T \cdot i_b = v_t^T \begin{bmatrix} 1_t & M_{21}^T \end{bmatrix} \cdot \begin{bmatrix} M_{11} \\ 1_l \end{bmatrix} i_l = v_t^T \underbrace{\begin{bmatrix} M_{11} + M_{21}^T \end{bmatrix}}_{=0_{t \times l}} i_l$$

= 0
(if finite circuit)

$$\Rightarrow M_{11} = -M_{21}^T$$

as v_t can be arbitrarily chosen
as can be i_l

$$\Rightarrow \text{gives } v_b = C^T \cdot v_t, \quad i_b = T^T i_l$$

(i.e. this is for a generic graph)

$$\begin{bmatrix} v_1 \\ v_2 \\ v_3 \\ v_4 \\ v_5 \end{bmatrix} = \begin{bmatrix} 1 & 0 & 0 \\ 0 & 1 & 0 \\ 0 & 0 & 1 \\ \hline 1 & -1 & 0 \\ 1 & -1 & -1 \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \\ v_3 \end{bmatrix}$$

$$\text{if } E = \left[\begin{array}{ccc|cc} 1 & 0 & 0 & 1 & 1 \\ 0 & 1 & 0 & -1 & -1 \\ 0 & 0 & 1 & 0 & -1 \end{array} \right]$$

$\underbrace{\hspace{10em}}_{I_3} \quad \quad \quad \color{blue}{\leftarrow}$

$$E^T = \begin{bmatrix} 1 & 0 & 0 \\ 0 & 1 & 0 \\ 0 & 0 & 1 \\ 1 & -1 & 0 \\ 1 & -1 & -1 \end{bmatrix}$$

Now know get t independent

KCL eqs & 2 independent

KVL eqs as $\text{rank } E = t, \text{ rank } D = 2$