



$$P_{in}(t) = v_b^T(t) i_b = v_1 i_1 + v_2 i_2 + v_3 i_3 + v_4 i_4 + v_5 i_5$$

$$v_b = C v_t, i_b = J^T i_x \Rightarrow v_t^T C J^T i_x = v_t^T M i_x = 0$$


if choose $v_2 = v_3 = 0, i_5 = 0 =$

$$P_{in} = v_t^T M i_x = [v_1 v_2 v_3] \begin{bmatrix} i_1 \\ i_2 \\ i_3 \\ i_4 \\ i_5 \end{bmatrix} = v_1 M_{14} i_4 = 0 \text{ for all } v, \& i_4 \Rightarrow M_{14} = 0$$

$$\Rightarrow M = C J^T = 0_{t \times x}$$


Given a finite graph choose a tree & then know the connections: $v_b = C v_t, i_b = J^T i_x, 0_t = C i_b, 0_x = J v_b$


Then use laws of elements

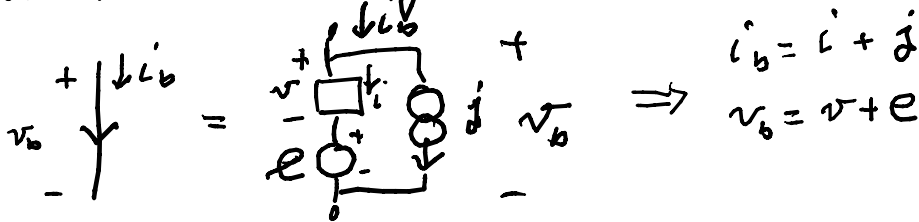

If linear then the component laws, $[v, i]$ are linearly related, if voltage controlled $i = g(v)$

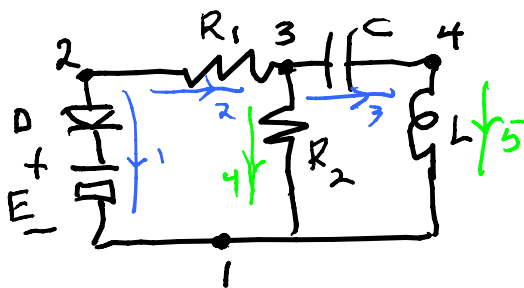
$$A v = B i \quad ; \quad A \& B \text{ constant}$$



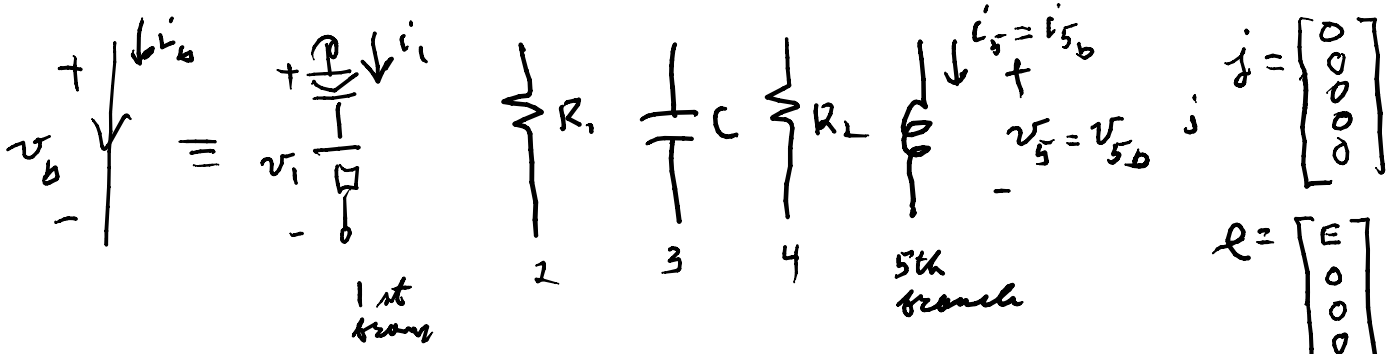

$$j = \begin{bmatrix} 0 \\ 0 \\ 0 \\ 0 \\ 0 \end{bmatrix}$$
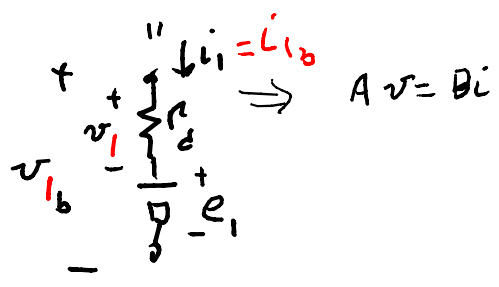
$$e = \begin{bmatrix} E \\ 0 \\ 0 \\ 0 \\ 0 \end{bmatrix}$$



$$v_1 = v_b i_1$$

$$v_2 = R_1 i_2$$

$$C v_3 = i_3$$

$$v_4 = R_2 i_4$$

$$v_5 = a h i_5$$

laws of components

$$\begin{bmatrix} 1 & 0 & 0 & 0 & 0 \\ 0 & 1 & 0 & 0 & 0 \\ 0 & 0 & C & 0 & 0 \\ 0 & 0 & 0 & 1 & 0 \\ 0 & 0 & 0 & 0 & 1 \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \\ v_3 \\ v_4 \\ v_5 \end{bmatrix} = \begin{bmatrix} v_b & 0 & 0 & 0 & 0 \\ 0 & R_1 & 0 & 0 & 0 \\ 0 & 0 & 1 & 0 & 0 \\ 0 & 0 & 0 & R_2 & 0 \\ 0 & 0 & 0 & 0 & a h \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \\ i_4 \\ i_5 \end{bmatrix}$$

$$a = d/dt$$