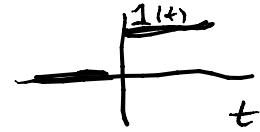


$$i(t) = c \frac{dv(t)}{dt} ; \quad 1(t) = \begin{cases} 1 & t > 0 \\ 0 & t < 0 \end{cases}$$




$$i(t)1(t) = c \frac{dv(t)}{dt} \cdot 1(t)$$

$$\begin{aligned} \frac{d(v(t)1(t))}{dt} &= \frac{dv(t)}{dt} \cdot 1(t) + v(t) \frac{d1(t)}{dt} ; \quad \frac{d1(t)}{dt} = \delta(t) \\ &= \frac{dv(t)}{dt} \cdot 1(t) + v(0) \delta(t) \end{aligned}$$


unit impulses
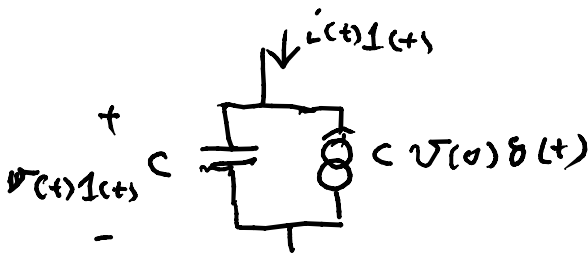
$$i(t)1(t) = c \frac{d(v(t)1(t))}{dt} - c v(0) \delta(t)$$




$$\int_{-\infty}^t i(\tau)1(\tau) d\tau = \int_{-\infty}^t c \frac{d(v(\tau)1(\tau))}{d\tau} d\tau - c v(0) \int_{-\infty}^t \delta(\tau) d\tau$$
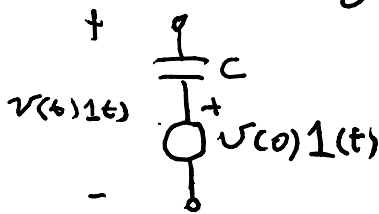
$$\Rightarrow \left(\int_0^t i(\tau)1(\tau) d\tau \right) 1(t) = c v(t)1(t) - c v(0)1(t)$$



Cases for $A v = B i$ where A^{-1} and/or B^{-1} don't exist

Ex: ideal transformers

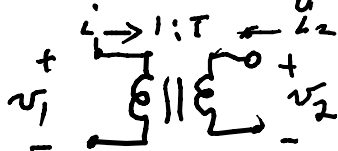

$$T v_1 = v_2, \quad i_1 = -T i_2$$



has power in zero

$$\begin{aligned} P_{in} &= v_1 i_1 + v_2 i_2 = v_1 i_1 + v_1 T i_2 \\ &= v_1 (i_1 + T i_2) = 0 \end{aligned}$$

$$\begin{bmatrix} -T & 1 \\ 0 & 0 \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix} = \begin{bmatrix} 0 \\ 1 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix} ; \quad \det A = \det B = 0$$

Syrator
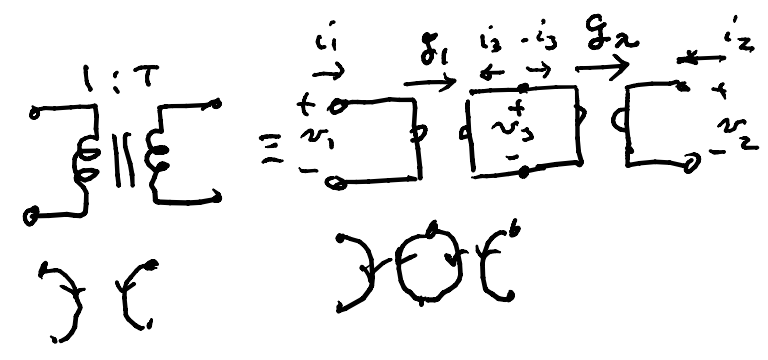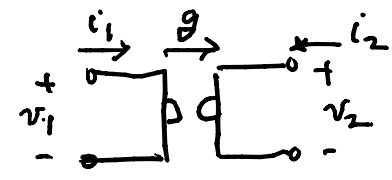
$$Y_{gys} = \begin{bmatrix} 0 & g \\ -g & 0 \end{bmatrix} = -Y_{gys}^T$$




has an admittance

$$\begin{aligned} i_1 &= g_1 v_3 \\ i_3 &= -g_1 v_1 = -(g_2 v_2) \\ i_2 &= -g_2 v_3 \end{aligned}$$

$$\left. \begin{aligned} v_3 = \frac{i_1}{g_1} = -\frac{i_2}{g_2} \Rightarrow i_1 = -\frac{g_1}{g_2} i_2 \\ -g_1 v_1 = -g_2 v_2 \Rightarrow v_2 = \frac{g_1}{g_2} v_1 \end{aligned} \right\} \text{ gives } T = \frac{g_1}{g_2}$$


Ex:

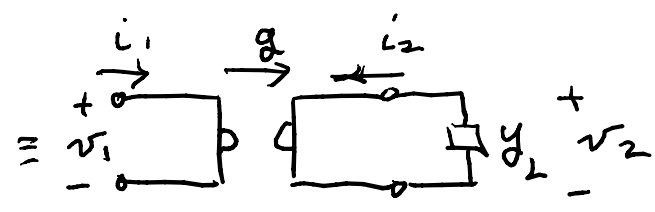


$$\begin{aligned} i_1 &= g v_2 \\ i_2 &= -y_L v_2 = -g v_1 \\ v_2 &= \frac{g}{y_L} v_1 \end{aligned}$$

$$i_1 = \frac{g^2}{y_L} v_1 \Rightarrow y_{in} = \frac{i_1}{v_1} = \frac{g^2}{y_L}$$
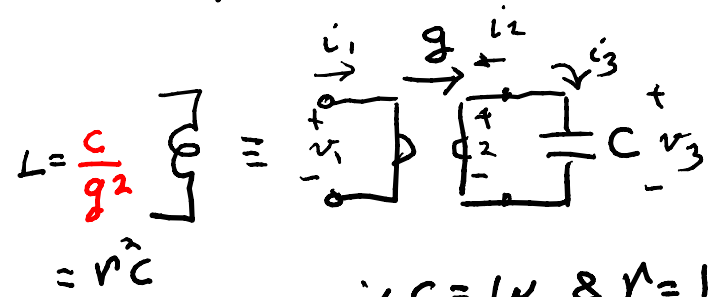
$$\text{if } y_L = sC \Rightarrow y_{in} = g^2 / sC = \frac{1}{sL} \Rightarrow L = g^2 / C$$



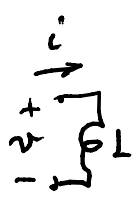if $C = 1\mu$ & $\nu = 1k\Omega$
then $L = 1$ Henry




$$Av = Bc \Rightarrow v = L di/dt = sLc \Rightarrow [1]v = [sL]i$$

$$\begin{bmatrix} 0 & g & 0 \\ -g & 0 & 0 \\ 0 & 0 & cL \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \\ v_3 \end{bmatrix} = \begin{bmatrix} 1 & 0 & 0 \\ 0 & 1 & 0 \\ 0 & 0 & 1 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix}$$

no derivative in B

derivative in B

Indefinite admittance

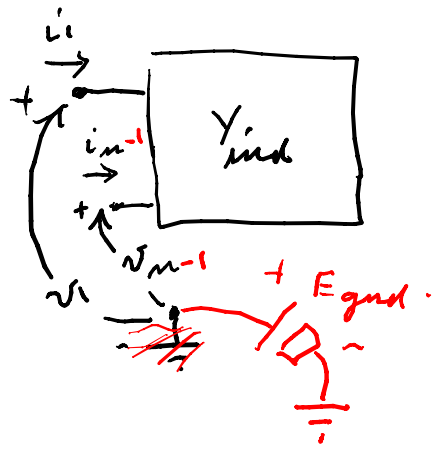

$$\begin{aligned}
 i = \begin{bmatrix} i_1 \\ \vdots \\ i_m \end{bmatrix} &= \begin{bmatrix} Y_{ind} \end{bmatrix} \begin{bmatrix} v_1 \\ \vdots \\ v_m \end{bmatrix} \\
 &= \begin{bmatrix} Y_{ind} \end{bmatrix} \begin{bmatrix} v_1 + E_{gnd} \\ \vdots \\ v_m + E_{gnd} \end{bmatrix} \\
 &= Y_{ind} v + E_{gnd} \underbrace{\begin{bmatrix} y_{11} + y_{12} + \dots + y_{1m} \\ \vdots \\ y_{m1} + y_{m2} + \dots + y_{mm} \end{bmatrix}}_0
 \end{aligned}$$

as i is unchanged so

the entries in a **row** sum to 0

also all currents sum to zero

Y_{ind} , all entries in any row sum to 0
 " " " " column " " 0

