




$$i = Y v$$

$$\sum_{j=1}^{m-1} i_j = 0 \Rightarrow \sum_i Y_{ij} = 0 \text{ for a fixed } j$$

and also by adding E to each v_j

$$\sum_j Y_{ij} = 0 \text{ for a fixed } i$$


Ex:
 Y_{ind}

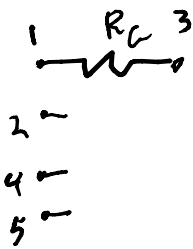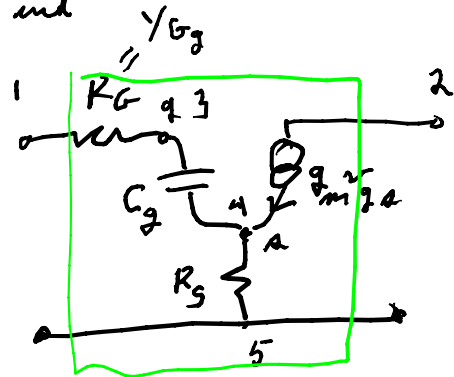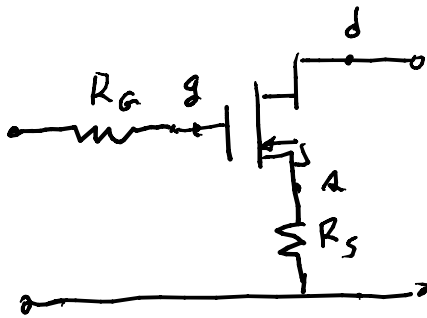

$$Y \Rightarrow \begin{cases} i_1 = G_g(v_1 - v_3) \\ i_3 = G_g(v_3 - v_1) \end{cases}$$

$$\Rightarrow Y_{R_g} = \begin{bmatrix} G_g & 0 & -G_g & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 \\ -G_g & 0 & G_g & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 \end{bmatrix}$$

for C_g

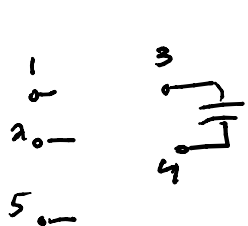


$$Y_{C_g} = \begin{bmatrix} 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 \\ G & 0 & \Delta C_g & -\Delta C_g & 0 \\ 0 & 0 & -\Delta C_g & \Delta C_g & 0 \\ 0 & 0 & 0 & 0 & 0 \end{bmatrix}$$

is indefinite


$$i_3 = \Delta C_g (v_3 - v_4)$$

$$i_4 = \Delta C_g (v_4 - v_3)$$

for $R_s = 1/G_s$

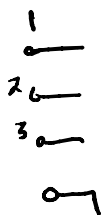
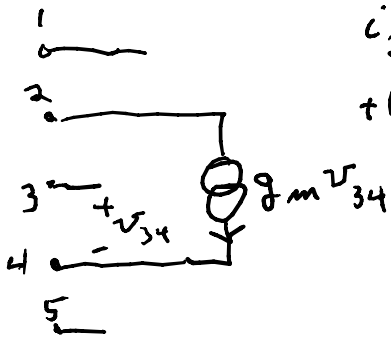
$$Y_{G_s} = \begin{bmatrix} 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & G_s & -G_s \\ 0 & 0 & 0 & -G_s & G_s \end{bmatrix}$$



$$i_2 = g_m(v_3 - v_4)$$

$$+i_4 = -g_m(v_3 - v_4) = g_m(-v_3 + v_4)$$

$$Y_{g_m} = \begin{bmatrix} 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & g_m & -g_m & 0 \\ 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & -g_m & g_m & 0 \\ 0 & 0 & 0 & 0 & 0 \end{bmatrix}$$

$$Y_{ind} = Y_{C_g} + Y_{G_s} + Y_{C_g} + Y_{g_m} = \begin{bmatrix} G_g & 0 & -G_g & 0 & 0 \\ 0 & 0 & g_m & -g_m & 0 \\ -G_g & 0 & G_g + AC_g & -AC_g & 0 \\ 0 & 0 & -AC_g - g_m & G_g + AC_g + g_m & -G_s \\ 0 & 0 & 0 & -G_s & +G_s \end{bmatrix}$$

To get the 2-port Y

set $i_3 = 0$ & $i_4 = 0$,

1st move ground to node 5; set $v_5 = 0$ (\Rightarrow ignore column 5 & i_5 is sum of other i 's so ignore row 5)

$$Y = \begin{bmatrix} G_g & 0 & -G_g & 0 \\ 0 & 0 & g_m & -g_m \\ -G_g & 0 & G_g + AC_g & -AC_g \\ 0 & 0 & -AC_g - g_m & G_g + AC_g + g_m \end{bmatrix} ; \begin{bmatrix} i_1 \\ i_2 \\ i_3 \\ i_4 \end{bmatrix} = \begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \\ v_3 \\ v_4 \end{bmatrix}$$

$C_5 = \frac{1}{s}$

$$\underline{0}_2 = \begin{bmatrix} 0 \\ 0 \end{bmatrix} = \begin{bmatrix} i_3 \\ i_4 \end{bmatrix} = Y_{21} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix} + Y_{22} \begin{bmatrix} v_3 \\ v_4 \end{bmatrix}$$

$$\text{solve for } \begin{bmatrix} v_3 \\ v_4 \end{bmatrix} = Y_{22}^{-1} (-Y_{21}) \begin{bmatrix} v_1 \\ v_2 \end{bmatrix} \Rightarrow \begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = (Y_{11} - Y_{12} Y_{22}^{-1} Y_{21}) \begin{bmatrix} v_1 \\ v_2 \end{bmatrix} = Y_{2-port} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix}$$

$$Y_{2-port} = Y_{11} - Y_{12} Y_{22}^{-1} Y_{21}$$

$$= \begin{bmatrix} G_g & 0 \\ 0 & 0 \end{bmatrix} - \begin{bmatrix} -G_g & 0 \\ g_m & -g_m \end{bmatrix} \begin{bmatrix} G_g + AC_g & -AC_g \\ -AC_g - g_m & G_g + AC_g + g_m \end{bmatrix} \begin{bmatrix} -G_g & 0 \\ 0 & 0 \end{bmatrix}$$

Duals: $v \rightarrow i_s = \text{dual}$ $i = cdv/dt$
 $i \rightarrow v_s$ $v_s = cd i_s/dt$

$Y = \begin{bmatrix} 0 & 0 \\ g_m & 0 \end{bmatrix} \Rightarrow Z_d = \begin{bmatrix} 0 & 0 \\ g_m & 0 \end{bmatrix} \Rightarrow$ voltage controlled
 by a current

dual of a graph \Rightarrow problem only planar graphs
 have dual graph



— dual branches
 — dual tree