

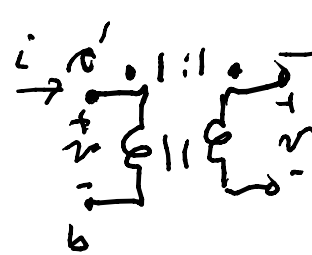
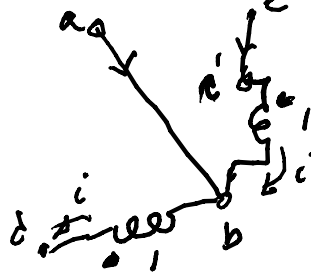
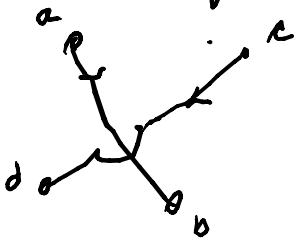
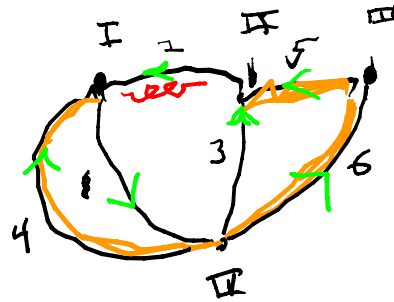



How to get a planar graph (for circuits)

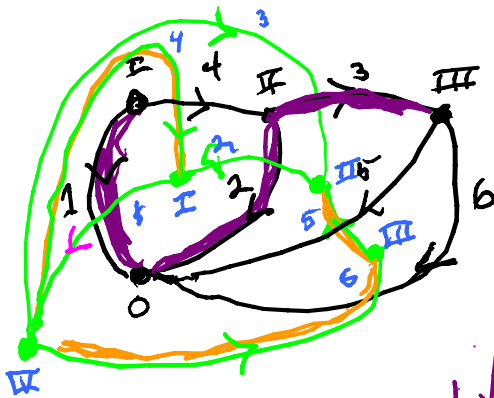

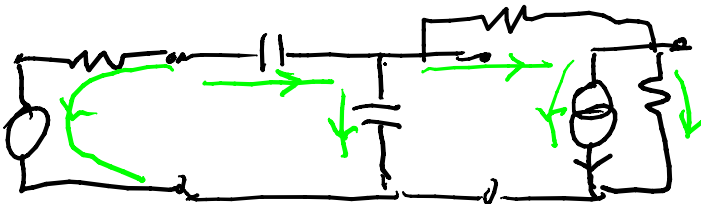same i & v laws as before but no branches cross




dual (oriented by)

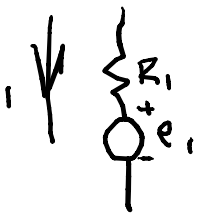

$$i = C \frac{dv}{dt}$$

$C = \text{const.}$
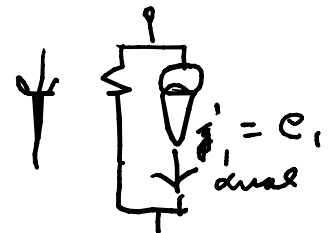
$$\Rightarrow \text{dual } v = C \frac{di}{dt} = L \frac{di}{dt}$$




$$G_{\text{dual}} = R_1$$

$$\text{if } C = C(t); \quad i = \frac{dq}{dt} = \frac{d(Cv)}{dt} = C \frac{dv}{dt} + \frac{dC}{dt} \cdot v$$


↑
time varying q

Norator & nullator:

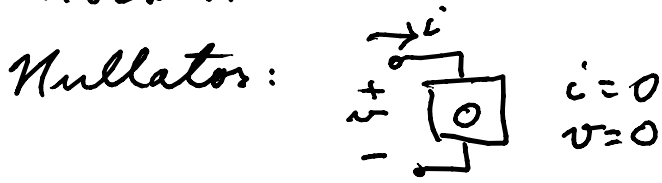

$$Av = Bi$$




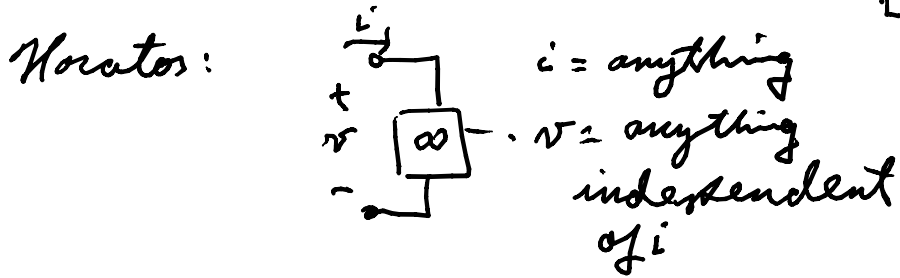
$$\begin{bmatrix} 1 \\ 0 \end{bmatrix} [v] = \begin{bmatrix} 0 \\ 1 \end{bmatrix} [i]$$



$$Av = Bi$$

$$\begin{bmatrix} 0 \\ 0 \end{bmatrix} v = \begin{bmatrix} 0 \\ 0 \end{bmatrix} i$$

ideal op-amp

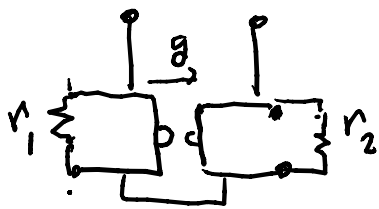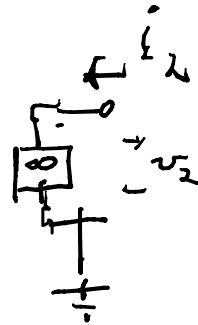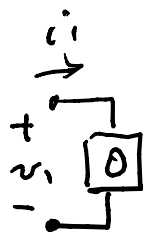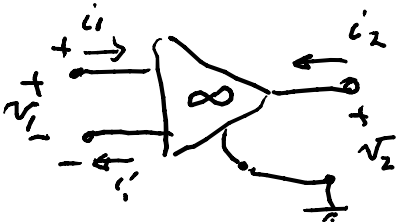


if $|g_1| = |g_2| = 1/g$

& one pos. & one neg

get a nullator or a norator

terminated 2-ports

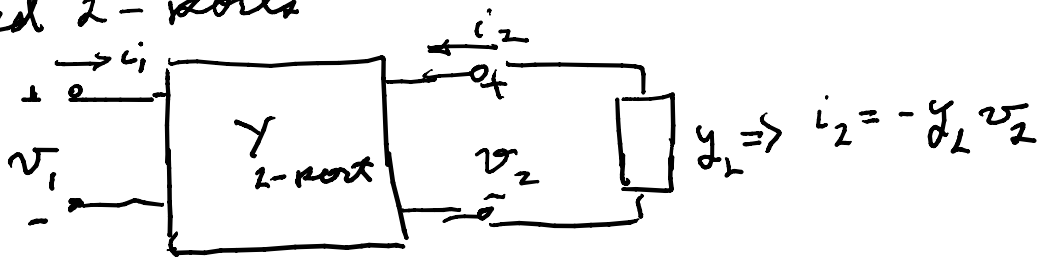

$$\begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix} = \begin{bmatrix} i_1 \\ -g_L v_2 \end{bmatrix}$$

last row $y_{21} v_1 + (y_{22} + g_L) v_2 = 0 \Rightarrow v_2 = -(y_{22} + g_L)^{-1} y_{21} v_1$

1st row $i_1 = y_{11} v_1 + y_{12} (-(y_{22} + g_L)^{-1} y_{21} v_1)$

$$i_1 = y_{in} v_1 \Rightarrow y_{in} = y_{11} - y_{12} [y_{22} + g_L]^{-1} y_{21}$$


of interest is g_L in terms of y_{in}

$$-(y_{in} - y_{sc}) = y_{12} [y_{22} + y_L]^{-1} y_{21} \quad \text{if } y_L \text{ is } 1 \times 1$$

$$= (y_{22} + y_L)^{-1} y_{12} y_{21}$$

$$(y_{22} + y_L)^{-1} = \frac{y_{11} - y_{in}}{y_{12} y_{21}} \Rightarrow y_{22} + y_L = \frac{y_{12} y_{21}}{y_{11} - y_{in}}$$
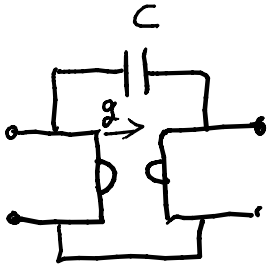
$$\Rightarrow y_L = -y_{22} + \frac{y_{12} y_{21}}{y_{11} - y_{in}} = \frac{y_{in} y_{22} - \Delta_y}{y_{11} - y_{in}}, \quad \Delta_y = y_{11} y_{22} - y_{21} y_{12}$$



$$Y = \begin{bmatrix} sC & -sC + g \\ -sC - g & sC \end{bmatrix}; \quad \Delta_y = (sC)^2 - (sC^2 - g^2) = g^2$$

$$y_L = \frac{sC y_{in} - g^2}{sC - y_{in}} =$$

use the Richards' function
p. 361