
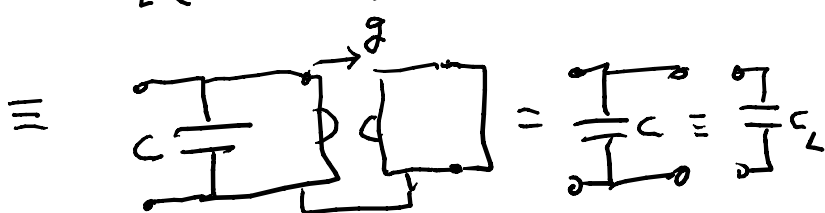



Ex $y_L = C_L A : \frac{y_{LL}}{y_L(k)} = \frac{k y_L(k) - A y_L(a)}{k y_L(a) - A y_L(k)} = \frac{k C_L k - A^2 C_L}{k C_L a - A C_L k}$

$$= \frac{C_L (k^2 - A^2)}{C_L (kA - kA)} \Rightarrow \frac{1}{y_{LL}} = 0 = \mathcal{Z}_{LL}$$

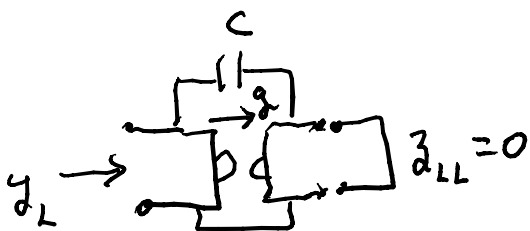


Ex2: $y = \frac{1}{LA}$
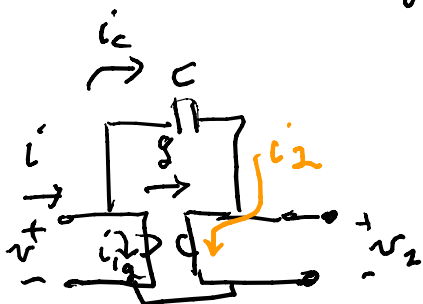
$$\frac{y_L}{y(k)} = \frac{k y(k) - A y(a)}{k y(a) - A y(k)} = \frac{k \frac{1}{LA} - A \frac{1}{LA}}{k \frac{1}{LA} - A \frac{1}{LA}} = \frac{\frac{1}{L} (1 - 1)}{\frac{1}{LA} (k^2 - A^2)} = 0$$



$i = i_1 + i_2$ of the gyrator

$y v_1 = i$

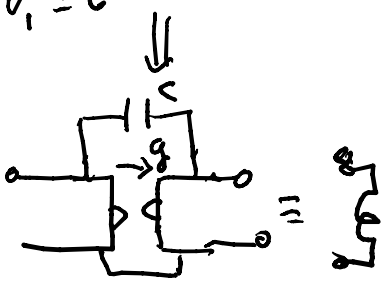

$$= g v_2 - g v_1 = g (v_2 - v_1)$$

$$i_c = CA(v_1 - v_2) = i_2 \Rightarrow v_2 - v_1 = \frac{-i_2}{CA}$$

$i = -g \cdot \frac{i_2}{CA}$ but $i_2 = -g v_1 = -g v$

$$\Rightarrow i = -g \frac{-g v}{CA} = \frac{g^2}{CA} v$$

$i = +\frac{g^2}{CA} v$

Passive circuit

$p_i(t) = v^T \cdot i(t)$, Passive if $E(t) = \int_{-\infty}^t p(\tau) d\tau, -\infty < t$
 energy in ≥ 0 (passive)

$$\Leftrightarrow \int_{-\infty}^{\infty} p(\tau) d\tau \geq 0$$

$$\int_{-\infty}^{\infty} v^{*T}(t) i(t) dt = \int_{-\infty}^{\infty} V^{*T}(j2\pi f) I(j2\pi f) df \quad \text{Parseval's theorem}$$

$$I(j\omega) = I(j2\pi f) = \int_{-\infty}^{\infty} i(t) e^{-j2\pi f t} dt = \text{Fourier transform}$$

$$\Rightarrow \int_{-\infty}^{\infty} V^{*T}(j\omega) Y(j\omega) V(j\omega) \frac{d\omega}{2\pi} \geq 0 \quad \text{for passivity}$$

$$\Rightarrow V^{*T} Y(j\omega) V \Rightarrow \frac{V^{*T} Y(j\omega) V + V^T Y^T(j\omega) V^*}{2}$$

$$\text{work with } \frac{V^{*T} Y(j\omega) V + V^{T*} Y^{Tx}(j\omega) V}{2} = \text{Re } V^{*T} Y(j\omega) V \geq 0$$

$$\Rightarrow \frac{V^{*T} (Y(j\omega) + Y^{Tx}(j\omega)) V}{2} \geq 0$$

(as $v(t) = v^*(t)$)

$$Y_{\text{hermitian}} = \frac{Y + Y^{Tx}}{2} \Rightarrow Y_{\text{hermitian}}(j\omega) \geq 0$$


" $\text{Re } y(j\omega)$ if Y is 1×1 matrix"

$$\text{Ex: } Y(s) = \begin{bmatrix} Cs & -Cs + g \\ -Cs - g & Cs \end{bmatrix}$$

$$\frac{Y(j\omega) + Y^T(j\omega)}{2} = \frac{1}{2} \left\{ \begin{bmatrix} j\omega C & -j\omega C + g \\ -j\omega C - g & j\omega C \end{bmatrix} + \begin{bmatrix} -j\omega C & j\omega C - g \\ +j\omega C + g & -j\omega C \end{bmatrix} \right\}$$

$$= \begin{bmatrix} 0 & 0 \\ 0 & 0 \end{bmatrix} \Rightarrow \begin{bmatrix} v_1^* & v_2^* \end{bmatrix} \begin{bmatrix} 0 & 0 \\ 0 & 0 \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix} \geq 0$$

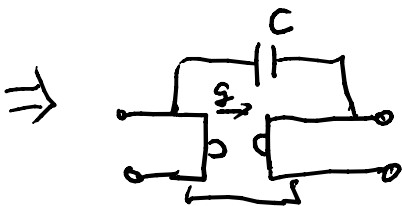for all $\begin{bmatrix} v_1 \\ v_2 \end{bmatrix}$



passive if $g \geq C \geq 0$ are real

Positive real needs $Y(s) + Y^{Tx}(s) \geq 0$ in $\sigma > 0$

$$\text{Ex: } y(s) = Cs \Rightarrow C(\sigma + j\omega) + C(\sigma - j\omega) = 2C\sigma \geq 0 \text{ in } \sigma > 0 \Rightarrow C \geq 0 \text{ for PR}$$

$V^{*T} Y(s) V$ has no poles in $\sigma > 0$ if rational, $A = \sigma + j\omega$

$e^{-(V^{*T} Y(s) V)}$ also is analytic in $\sigma > 0$

$$|e^{-(V^{*T} Y(s) V)}| = e^{-\operatorname{Re}(V^{*T} Y(s) V)} |e^{-j \operatorname{Im}(V^{*T} Y(s) V)}| = e^{-\operatorname{Re}(V^{*T} Y(s) V)}$$

by maximum modulus theorem $|e^{-V^{*T} Y(s) V}|$ is

maximum on $j\omega$ axis for the region $\sigma > 0$

$\Rightarrow \operatorname{Re}(V^{*T} Y(s) V) \geq 0$ in $\sigma > 0$

$$\frac{1}{2} (V^{*T} Y(s) V + V^{T*} Y(s) V) = \frac{1}{2} V^{*T} (Y(s) + Y(s)^{T*}) V \geq 0 \text{ for all } V \neq 0 \text{ in } \sigma > 0$$

Key of the positive real condition

Ex above: $\frac{Y(s) + Y(s)^{T*}}{2} = \frac{1}{2} \begin{bmatrix} cA + c^* A^* & -cA - c^* A^* + g - g^* \\ -cA - c^* A^* + g - g^* & cA + c^* A^* \end{bmatrix} = c \begin{bmatrix} 1 & -1 \\ -1 & 1 \end{bmatrix}$

1st condition is $Y(s)$ is real $\Rightarrow c$ real

? for PR is $c \begin{bmatrix} 1 & -1 \\ -1 & 1 \end{bmatrix}$ positive semi-definite (≥ 0) (is only if $c > 0$)

$$c \begin{bmatrix} v_1^* & v_2^* \end{bmatrix} \begin{bmatrix} 1 & -1 \\ -1 & 1 \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix} = c \begin{bmatrix} v_1^* & v_2^* \end{bmatrix} \begin{bmatrix} v_1 - v_2 \\ v_2 - v_1 \end{bmatrix} = [v_1^* v_1 - v_1^* v_2 + v_2^* v_2 - v_1 v_2^*] c$$

check for all v_1, v_2 as complex numbers true as all principal minors are > 0