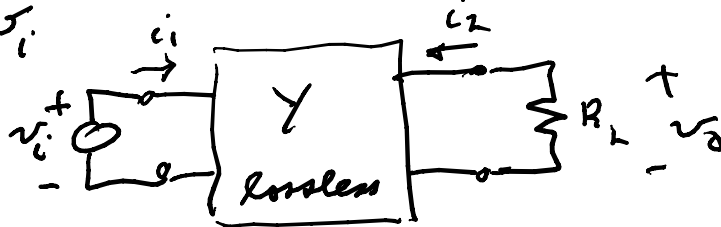


Synthesis  $v_o/v_i$

$$-i_2 = G_L v_o$$



$$-G_L v_o = \begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix} = \begin{bmatrix} v_i \\ v_o \end{bmatrix}$$

$$-(G_L + y_{22}) v_o = y_{21} v_i \Rightarrow \frac{v_o}{v_i} = \frac{-y_{21}}{G_L + y_{22}} = \frac{-y_{21}/G_L}{1 + y_{22}/G_L}$$

if  $\frac{v_o}{v_i}(s) = \frac{N(s)}{D(s)}$  &  $D(s) = \text{Hurwitz}$

$$= \epsilon D(s) + \text{odd } D(s) = \epsilon D(s) \left[ 1 + \frac{\text{odd } D(s)}{\epsilon D(s)} \right]$$

$$= \text{odd } (D(s)) \left[ 1 + \frac{\epsilon D(s)}{\text{odd } D(s)} \right]$$



and  $\therefore$  choose  $\frac{y_{22}}{G_L} = \frac{\text{odd } (D(s))}{\epsilon D(s)}$  or  $\frac{\epsilon D(s)}{\text{odd } (D(s))}$  these are reactance functions

Ex:  $T(s) = \frac{A_0}{s^2 + \sqrt{2}s + 1} = \text{Hurwitz}$  } max flat low pass

$$= \frac{A_0/(s^2+1)}{1 + \frac{\sqrt{2}s}{s^2+1}} = \frac{A_0/\sqrt{2}s}{1 + \frac{s^2+1}{\sqrt{2}s}}$$


Choose  $y_{22} = G_L \cdot \frac{\sqrt{2}s}{s^2+1}$  or  $y_{22} = G_L \left( \frac{s^2+1}{\sqrt{2}s} \right)$
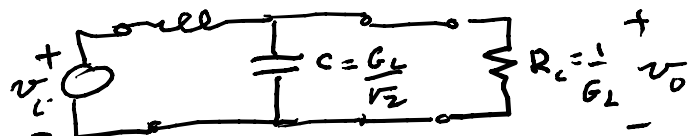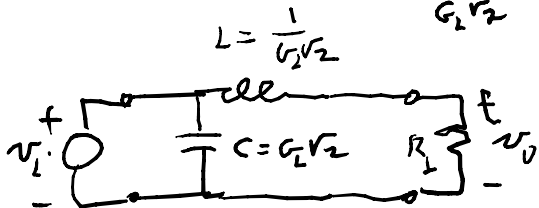
$$= \frac{1}{\frac{s}{G_L \sqrt{2}} + \frac{1}{2G_L \sqrt{2}}} = \frac{G_L \sqrt{2}}{s} + \frac{1}{\sqrt{2} G_L}$$




( $\therefore$  sy even) if  $D(s) = s^n + \dots$   $n = \text{odd}$  use this

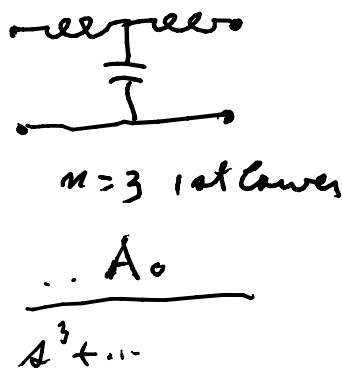
if  $D(s) = s^n + \dots$   $n = \text{even}$  (use this one here,  $n=2$ )



for high pass use 2nd order

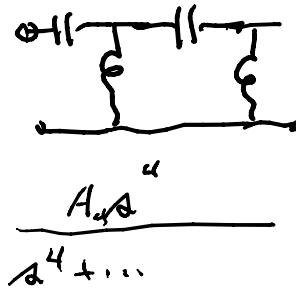


To find  $A_0$ , look at  $s=0$

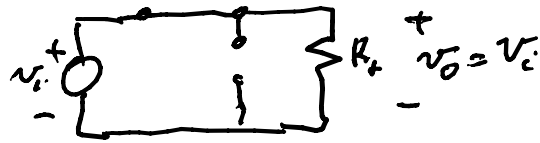

$$T(0) = \frac{A_0}{1} = \frac{v_o(0)}{v_i} = 1 \Rightarrow A_0 = 1$$


as another check

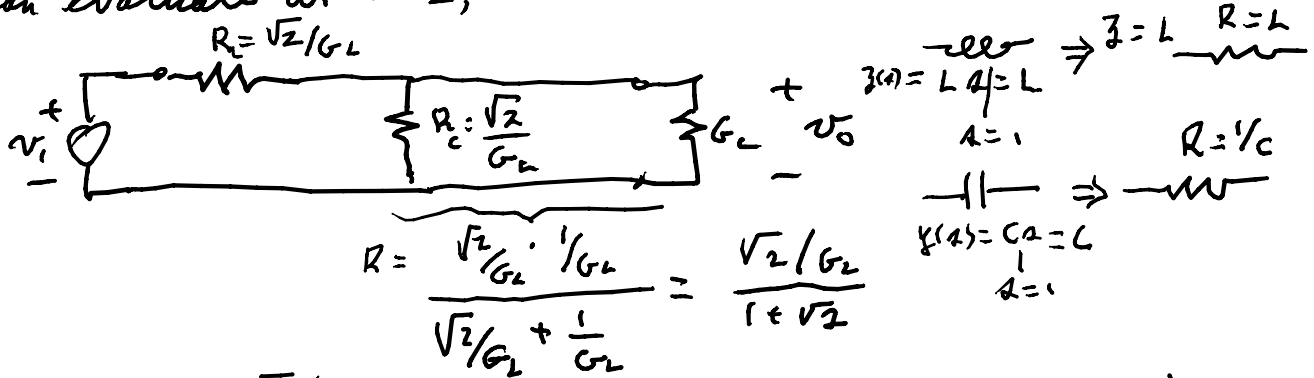can evaluate at  $s=1$ , a real number  $\Rightarrow$  resistive circuit



$$\frac{v_o}{v_i} = \frac{\frac{\sqrt{2}/G_L}{1+\sqrt{2}}}{\frac{\sqrt{2}}{G_L} + \frac{\sqrt{2}/G_L}{1+\sqrt{2}}} = \frac{1}{1+\sqrt{2}} = \frac{1}{2+\sqrt{2}} = T(1) = \frac{A_0}{1+\sqrt{2}+1} = \frac{A_0}{2+\sqrt{2}} \Rightarrow A_0 = 1$$

2-port

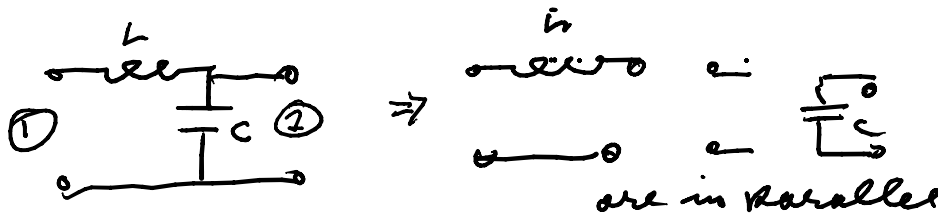

$$Y = \frac{1}{sL} \begin{bmatrix} 1 & -1 \\ -1 & 1 \end{bmatrix} + \begin{bmatrix} 0 & 0 \\ 0 & sC \end{bmatrix} = \begin{bmatrix} 1/sL & -1/sL \\ -1/sL & 1/sL + sC \end{bmatrix}$$


$$Ex: \frac{v_o}{v_i} = \frac{A_0(s^2+4)}{s^3+3s^2+2s+1} = \frac{A_0(s^2+4)/(3s^2+1)}{1 + \frac{s^3+2s}{3s^2+1}}$$

$$y_{22} = \frac{s^3 + 2s}{3s^2 + 1} = \frac{1}{3}s + \frac{5/3}{3s^2 + 1}$$

$$\frac{3s^2 + 1}{\frac{1}{3}s} \left( \frac{s^3 + 2s}{s^2 + \frac{1}{3}} \right)$$


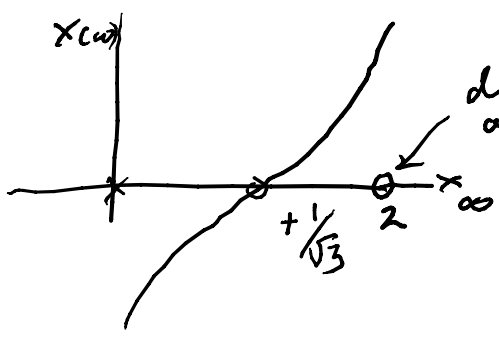
$$jB(\omega) = \frac{j5/3\omega}{-3\omega^2 + 1}$$



$$jX(\omega) = \frac{-3\omega^2 + 1}{5/3\omega}$$


to move, take out part of pole at  $\infty$  to move zero to 2

$$Z_{rem} = \frac{3s^2 + 1}{5/3s} = \frac{9}{5}s + \frac{1}{5/3s}$$


$$Z_{new} = \left(\frac{9}{5} - L_1\right)s + \frac{1}{5/3s} = \frac{\left(\frac{9}{5} - L_1\right)5/3s^2 + 1}{5/3s} \Rightarrow \left(3 - \frac{5}{3}L_1\right)(-4) + 1 = 0$$

$$\Rightarrow \frac{20}{3}L_1 = 11$$
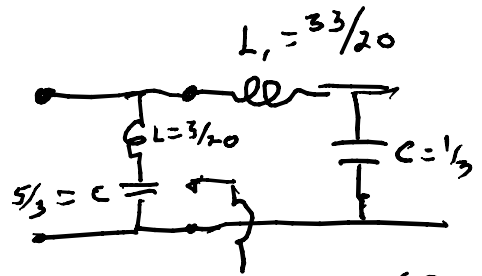
$$\Rightarrow L = \frac{3 \times 11}{20} = \frac{33}{20}$$



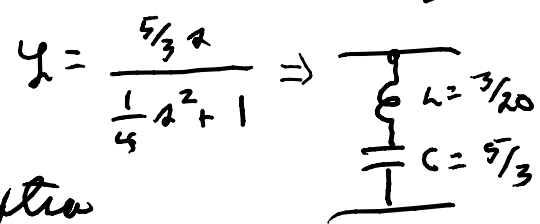
$$Z_{new} = \left(\frac{9}{5} - \frac{33}{20}\right)s + \frac{1}{5/3s} = \frac{36 - 33}{20}s + \frac{1}{5/3s} = \frac{3}{20}s + \frac{1}{5/3s}$$



has an extra element due to the partial pole removal at  $s = \infty$  to create the zero of transmission at  $s^2 = -4$

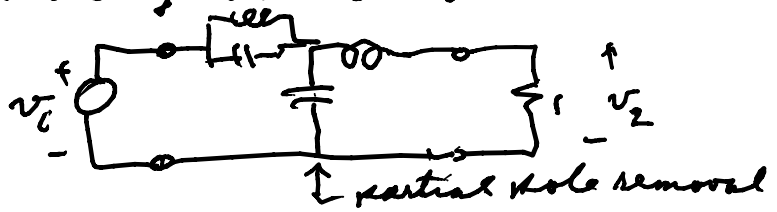if correctly divided by odd rather than even get correct circuit



has zero of  $\frac{v_2}{v_1}$  @  $s^2 = -4$

