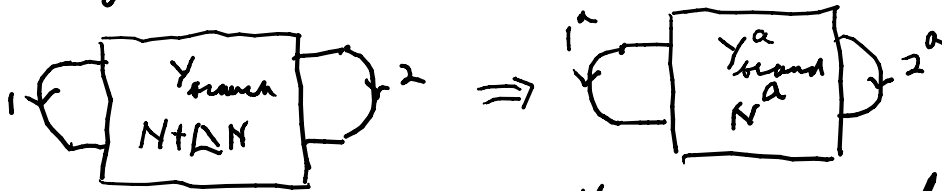


$$S_x^{T(a)} = \frac{dT(a)/dx}{T(a)/x} = \frac{x}{T(a)} \cdot \frac{dT(a)}{dx}$$

use adjoint circuit

adjoint



these have the same graph

$$i_b^T v_b = 0$$

$$i_b^{aT} v_b^a = 0$$

$$\text{also } i_b^T v_b^a = 0$$

$$\& i_b^{aT} v_b = 0$$

$$\begin{bmatrix} i_1 \\ i_2 \\ i_b \end{bmatrix} = i_b, \quad \begin{bmatrix} v_1 \\ v_2 \\ v_b \end{bmatrix} = v_b$$

$$i_b^T v_b^a - i_b^{aT} v_b = 0$$

$$\rightarrow i_1 v_1^a + i_2 v_2^a + i_b^T v_b^a - i_1^a v_1 - i_2^a v_2 - i_b^{aT} v_b = 0$$

assume $T(a) = v_2/v_1^{(a)}$

keep v_1 fixed but v_2 will change when change circuit & keep v_1^a fixed

$$i_b = Y v_b, \quad i_b^a = Y^a v_b^a$$

$$\Delta i_b = \Delta Y \cdot v_b + Y \cdot \Delta v_b, \quad \Delta i_b^a = 0, \quad \Delta Y^a = 0, \quad \Delta v_b^a = 0$$

after Δv_2 , as $\Delta T(a) = \Delta v_2/v_1$

only changes to

$$\Delta i_1 \cdot v_1^a + i_1 \Delta v_1^a + \Delta i_2 \cdot v_2^a + i_2 \Delta v_2^a + \Delta i_b^T \cdot v_b^a + i_b^T \cdot \Delta v_b^a - \Delta i_1^a v_1 - i_1^a \Delta v_1 - \Delta i_2^a v_2 - i_2^a \Delta v_2 - \Delta i_b^{aT} \cdot v_b - i_b^{aT} \Delta v_b = 0$$

$$(\Delta i_1 v_1^a + \Delta i_2 v_2^a + \Delta i_b^T v_b^a) - i_2^a \Delta v_2 - i_b^{aT} \Delta v_b$$

$$\Delta i_b = \Delta Y \cdot v_b + Y \cdot \Delta v_b$$

$$i_b^a = Y^a v_b^a$$

$$(\Delta i_1 v_1^a + \Delta i_2 v_2^a - i_2^a \Delta v_2) + [v_b^T \Delta Y v_b^a + \Delta v_b^T Y^T v_b^a]$$

external changes \uparrow interested in $- [v_b^{aT} Y^{aT} \Delta v_b] = 0$

$$v_b^{aT} Y \Delta v_b - v_b^{aT} Y^{aT} \Delta v_b = v_b^{aT} [Y - Y^{aT}] \Delta v_b$$



set this to zero choose N^R by $Y = Y^{aT} \Rightarrow Y^a = Y^T$

choose $v_1^a = 0 \Rightarrow$ a short, $i_2^a = -1$ (a current source)

$\Delta i_2 = 0$ (an open on port 2 of N)

$$\Delta v_2 = v_b^T \Delta Y v_b^a = v_b^{aT} \Delta Y v_b$$
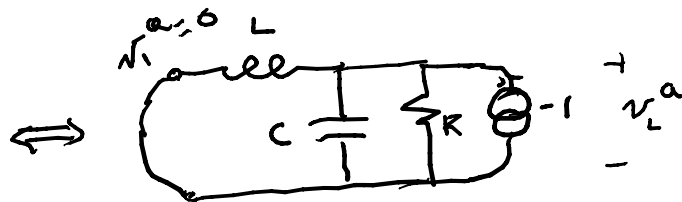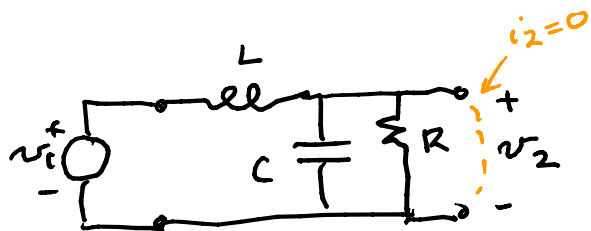
$$\therefore \frac{\Delta v_2}{\Delta x} = v_b^{aT} \frac{\Delta Y}{\Delta x} v_b$$



$$Y = \begin{bmatrix} \frac{1}{sL} & -\frac{1}{sL} \\ -\frac{1}{sL} & \frac{1}{sL} + Cs + G \end{bmatrix}; \quad Y^a = Y$$

$$v_b^T = [v_L \ v_C \ v_R], \quad v_b^a = \begin{bmatrix} \frac{1}{sL} & 0 & 0 \\ 0 & Cs & 0 \\ 0 & 0 & G \end{bmatrix} v_b; \quad Y = \begin{bmatrix} \frac{1}{sL} & 0 & 0 \\ 0 & Cs & 0 \\ 0 & 0 & G \end{bmatrix}$$

if S_L then $\frac{\Delta Y}{\Delta L} = \begin{bmatrix} -\frac{1}{L^2} \frac{\Delta L}{L} & \frac{1}{sL} & 0 & 0 \\ 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 \end{bmatrix} = \begin{bmatrix} -\frac{1}{L^2} & 0 & 0 \\ 0 & 0 & 0 \\ 0 & 0 & 0 \end{bmatrix}$

$$\therefore \frac{\Delta v_2}{\Delta L} = -\frac{1}{L^2} v_L \cdot v_L^a \Rightarrow S_L = \frac{v_2}{v_1} = \frac{L}{L^2} v_L v_L^a$$

$$v_L^a = \frac{1}{\frac{1}{sL} + Cs + G} \cdot (-1)$$

$$v_L = \frac{sL}{sL + \frac{1}{Cs + G}}, \quad v_1 = 1$$

$$\frac{v_2}{v_1} = \frac{\frac{1}{C+G}}{AL + \frac{1}{C+G}} = \frac{1}{A^2LC + GLA + 1} \quad ; \quad \frac{d(v_2/v_1)}{dL} = \frac{-1(C+G)}{(A^2LC + GLA + 1)^2}$$

by direct differentiation

$$\frac{\Delta v_2}{\Delta L} = -\frac{1}{L^2} \left(\frac{AL}{AL + \frac{1}{C+G}} \right) \cdot \frac{1}{\frac{1}{AL} + C+G} \quad \text{from NBN}^a$$

$$= \frac{-1(C+G)}{AL(C+G)+1} \times \frac{1}{1 + A^2LC + GLA} = \frac{-A(C+G)}{(CLA^2 + GLA + 1)^2}$$

$$\sum_L^{TCR} = \frac{\frac{1}{L^2}}{\frac{1}{A^2LC + GLA + 1}} \cdot \frac{-AL}{A^2LC + GLA + 1} \cdot \frac{AL(C+G)}{(A^2LC + GLA + 1)} = \frac{AL(C+G)}{LCA^2 + LGA + 1}$$

varies with $\alpha = \sigma + j\omega$