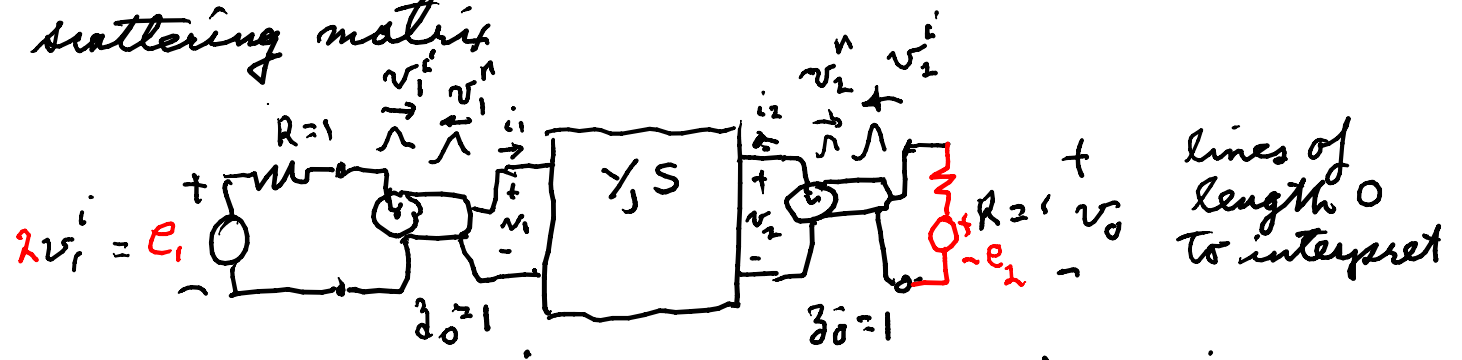


p. 406 = adjoint

scattering matrix



$$v^n = S v^i$$

S = scattering matrix

$$2v^i + 2v^n = 2v \Rightarrow v = v^i + v^n$$

$$2v^i - 2v^n = 2i \Rightarrow i = v^i - v^n$$

$$2v^i = v + \beta_0 i = v + i$$

$$2v^n = v - \beta_0 i = v - i$$

$$v^i = \begin{bmatrix} v_1^i \\ v_2^i \end{bmatrix} \quad i \Rightarrow \text{incident} \quad v = \begin{bmatrix} v_1 \\ v_2 \end{bmatrix}$$

$$v^n = \begin{bmatrix} v_1^n \\ v_2^n \end{bmatrix} \quad n \Rightarrow \text{reflected}, \quad i = \begin{bmatrix} i_1 \\ i_2 \end{bmatrix}$$

$$\frac{1}{2}(v - i) = S \frac{1}{2}(v + i)$$

$$\frac{1}{2}i + \frac{1}{2}Si = \frac{1}{2}(v - Sv)$$

$$(1_2 + S)i = (1_2 - S)v \Rightarrow i = Yv = (1_2 + S)^{-1}(1_2 - S)v$$

$$Y = (1_2 + S)^{-1}(1_2 - S)$$


$$S_{11} = \left. \frac{v_1^n}{v_1^i} \right|_{v_2^i=0} \quad ; \quad v_1^i = \frac{v_2 + i_2}{2} \Rightarrow v_2 = -i_2 \text{ if } v_2^i = 0 \Rightarrow e_2 = 0$$

always $e_2 = v_2 + Ri_2 = v_2 + i_2 = 2v_2^i$

$$e_1 = v_1 + Ri_1 = v + i_1 = 2v_1^i$$


S_{11} = input S at port 1 when load in port 2 by $\beta_0 = 1$
= reflection coefficient @ port with 1Ω on port 2

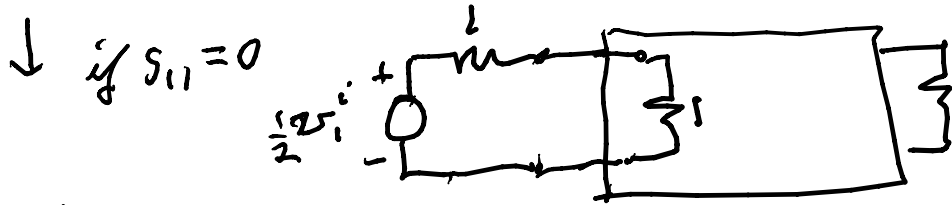if $S_{11} = 0 \Rightarrow v_1^n = 0$ when $v_2^i = 0$
 $= \frac{1}{2}(v_1 - i_1) \Rightarrow v_1 = i_1 \Rightarrow$ input @ port 1 = 1Ω
when load port 2 is 1Ω



$$S_{21} = \left. \frac{v_2}{v_1^i} \right|_{v_2^i = 0} \Rightarrow v_2 = -Ri_2 = -i_2 ; v_2^i = \frac{1}{2}(v_2 - i_2) = v_2$$

$$v_1^i = \frac{1}{2}e_1$$

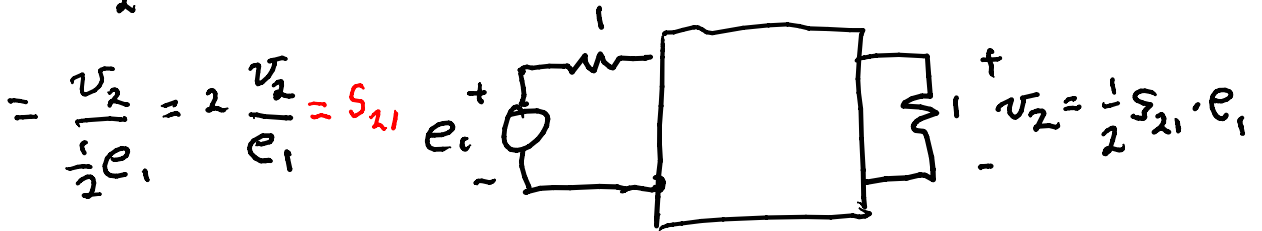

\Rightarrow called transmission coefficient

Note: $(\frac{1}{2} + S)^{-1} (1_2 - S) = (1_2 - S)(\frac{1}{2} + S)^{-1}$

to see $\times (\frac{1}{2} + S)$ on left & right; $(1_2 - S)(\frac{1}{2} + S)$, $(\frac{1}{2} + S)(1_2 - S)$

$$\frac{1}{2} - S^2 \quad \longleftrightarrow \quad 1_2 - S^2$$

are =

For a 1-port $1_2 \rightarrow 1$

Note $Y = (\frac{1}{2} + S)^{-1} (1_2 - S) \Rightarrow (\frac{1}{2} + S)Y = (1_2 - S)$

$$Y + SY = 1_2 - S$$

$$Y - 1_2 = (-S - SY) = S(-1 - Y)$$

$$S = (\frac{1}{2} - Y)(1_2 + Y)^{-1}$$

Ex:

$1_2 \rightarrow 1$, $y(s) = aC$ pole @ ∞

$$S(s) = \frac{(1 - y(s))}{(1 + y(s))} = \frac{1 - aC}{1 + aC} \quad \text{no pole @ } \infty \quad (= -1/C)$$

Ex

$$y(s) = \frac{2a}{s^2 + 3} \quad \begin{matrix} L = 1/2 \\ C = 2/3 \end{matrix} ; S(s) = \frac{1 - \frac{2a}{s^2 + 3}}{1 + \frac{2a}{s^2 + 3}} = \frac{s^2 + 3 - 2a}{s^2 + 3 + 2a}$$

Hurwitz

$$s_{1,2} = -\frac{2}{2} \pm \frac{1}{2} \sqrt{4 - 4 \times 3} = -1 \pm j\sqrt{2} \text{ in LHP}$$

For passive circuits S is bounded-real
 & if rational called BR

conditions

1) $S(s)$ is real for real $s = \sigma > 0$

2) $S(s)$ is analytic in $\sigma > 0$

3) $\mathbf{I}_2 - S^T(s) \cdot S(s)$ is positive semi-definite in $\sigma > 0$
 (bounded norm by 1)

For lossless: $Y(s) + Y(-s)^T = \mathbf{O}_2$

$\times (\mathbf{I}_2 + S(s))$ on left $\left\{ \begin{array}{l} (\mathbf{I}_2 + S(s))^{-1} (\mathbf{I}_2 - S(s)) + (\mathbf{I}_2 - S^T(-s)) (\mathbf{I}_2 + S^T(-s))^{-1} \end{array} \right.$

$\times (\mathbf{I}_2 + S^T(-s))$ on right $\left\{ \begin{array}{l} (\mathbf{I}_2 - S(s)) (\mathbf{I}_2 + S^T(-s)) + (\mathbf{I}_2 + S(s)) (\mathbf{I}_2 - S^T(-s)) = \mathbf{O}_2 \end{array} \right.$

$$\mathbf{I}_2 - S(s) + S^T(-s) - S(s)S^T(-s) + \mathbf{I}_2 - S^T(-s) + S(s) - S(s)S^T(-s) = \mathbf{O}_2$$

$$2\mathbf{I}_2 - 2S(s)S^T(-s) = \mathbf{O}_2 \Rightarrow S(s) \cdot S^T(-s) = \mathbf{I}_2$$

$$\Rightarrow S(s)^{-1} = S^T(-s) \Leftrightarrow \text{lossless condition}$$