

Lossless for $S(s) \Rightarrow \frac{1}{2} = S(-s)S(s)$
2 in for n port

Power: $P(j\omega) = \text{Re } v(j\omega) i(j\omega)$
 $2P(j\omega) = i^{TX}(j\omega) v(j\omega) + v^{TX}(j\omega) i(j\omega)$

$v = v^i + v^r$
 $i = v^i - v^r$

$$2P(j\omega) = (v^i - v^r)^{TX} (v^i + v^r) + (v^i + v^r)^{TX} (v^i - v^r)$$

$$= v^{iTX} v^i - v^{rTX} v^r + v^{iTX} v^r - v^{rTX} v^i + v^{iTX} v^i - v^{rTX} v^r + v^{iTX} v^r - v^{rTX} v^i$$

$P(j\omega) = v^{iTX} v^i - (v^{iTX} S^{TX})(S v^i) = v^{iTX} [1_2 - S^{TX}(j\omega) S(j\omega)] v^i$

for passive want this > 0

$v^i = \text{incident voltage}, 2v^i = v + i = v + Z_0 i$
 $v^r = \text{reflected voltage}, 2v^r = v - i = v - Z_0 i$
 Z_0 normalized = 1_2

$v^r = S v^i$; $S(s)$ is rational in s for a finite circuit

For passive $\frac{1}{2} - S^{TX}(j\omega) S(j\omega) = \frac{1}{2} - \|S(j\omega)\|^2 \geq 0$

also $S(s)$ has no poles in $\sigma \geq 0$

Lossless $\Leftrightarrow P(j\omega) = 0 \Rightarrow \frac{1}{2} = S^{TX}(j\omega) S(j\omega) = S^{TX}(-j\omega) S(j\omega)$

\Downarrow
 $\frac{1}{2} = S^{TX}(-s) S(s)$
(lossless)
rational real coefficients by analytic continuation


Ex: $Av = Bi \Rightarrow A(v^i + v^r) = B(v^i - v^r)$
 $(A - B)v^i = -(A + B)v^r$
 $\Rightarrow v^r = S v^i \Rightarrow (B + A)^{-1} (B - A) v^i = v^r$

$$S = (B+A)^{-1}(B-A)$$

For transformer:

$$v_2 = T v_1 \quad v_1^T i_1 + v_2^T i_2 = 0$$
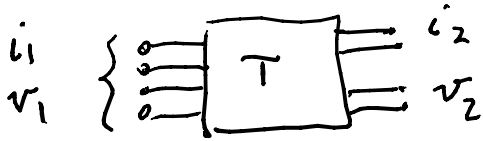
$$i_1 = -T^T i_2 \quad v_1^T i_1 + v_1^T T^T i_2 = 0$$



$$Av = Bi$$


$$\begin{bmatrix} -T & 1 \\ 0 & 0 \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix} = \begin{bmatrix} 0 & 0 \\ 1 & T^T \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix}$$

$$Y \Rightarrow i = Yv = B^{-1}Av$$

$$B+A = \begin{bmatrix} -T & 1 \\ 1 & T^T \end{bmatrix}; \text{ if } n=1 \quad -TT^T - 1$$

no B^{-1} for the transformer.

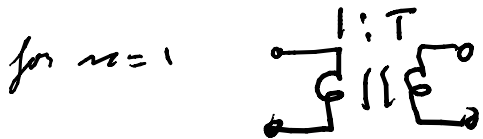here $(B+A)^{-1}$ always exists if T is real



$$\text{then } (B+A)^{-1} = \frac{-1}{1+T^2} \begin{bmatrix} T & -1 \\ -1 & -T \end{bmatrix}$$

$$(B-A) = \begin{bmatrix} T & -1 \\ 1 & T^T \end{bmatrix}$$

$$S = \frac{-1}{1+T^2} \begin{bmatrix} T & -1 \\ -1 & -T \end{bmatrix} \begin{bmatrix} T & -1 \\ 1 & T^T \end{bmatrix} = \frac{-1}{1+T^2} \begin{bmatrix} T^2-1 & -2T \\ -2T & 1-T^2 \end{bmatrix}$$


$$S^{-1} = S^T?$$

$$S^T = S$$

$$\text{for } S^{-1}, \det S = \frac{(T^2-1)(1-T^2) - 4T^2}{(1+T^2)^2} = \frac{T^2 - T^4 - 1 + T^2 - 4T^2}{1+2T^2+T^4}$$

$$= \frac{-(T^4 + 2T^2 + 1)}{1+2T^2+T^4} = -1$$
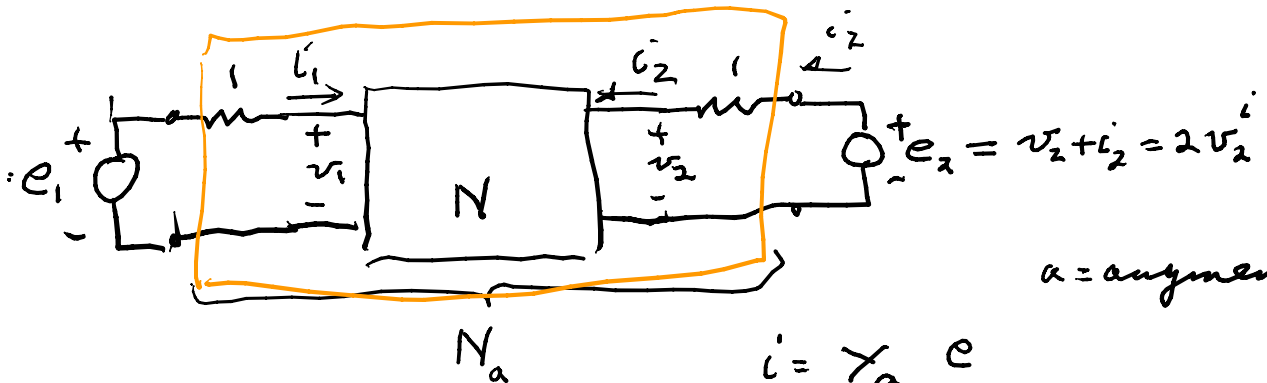
$$S^{-1} = \frac{-1}{-1} \begin{bmatrix} \frac{1-T^2}{-(1+T^2)} & \frac{2T}{-(1+T^2)} \\ \frac{+2T}{-(1+T^2)} & \frac{(T^2-1)}{-(1+T^2)} \end{bmatrix} = S^T \Rightarrow \text{lossless}$$



$$i = Y_a e = 2 Y_a v^i \quad 2v^i = v - i$$

$$v = e - i = e - Y_a e$$

$$= (\mathbb{1}_2 - Y_a) e$$

$$\Rightarrow (\mathbb{1}_2 - Y_a) i = (\mathbb{1}_2 - Y_a) Y_a e = (Y_a - Y_a^2) e$$

$$Y_a v = Y_a (\mathbb{1}_2 - Y_a) e = (Y_a - Y_a^2) e$$

$$A v = B i$$

$$Y_a v = (\mathbb{1}_2 - Y_a) i \Rightarrow A = Y_a, B = \mathbb{1}_2 - Y_a$$

$$S = (B + A)^{-1} (B - A) = \mathbb{1}_2 \times (\mathbb{1}_2 - 2Y_a) = \mathbb{1}_2 - 2Y_a$$

Y_a does not exist if we see -1Ω @ any port
essentially every passive circuit has an S