

ENEE 303H Final Exam – Fall 2014


Take Home; due 10am M 12/15; classroom – Signature certifies that all the work is your own 150 points, 2 hours, open book, open notes. Notebooks are due at the end of the exam.

Good luck and have a good semester break

1. (50 points, 30 minutes)

The following circuit uses the Wilamowski resistor, on the left, with its complement, on the right, to make a bilateral resistor.

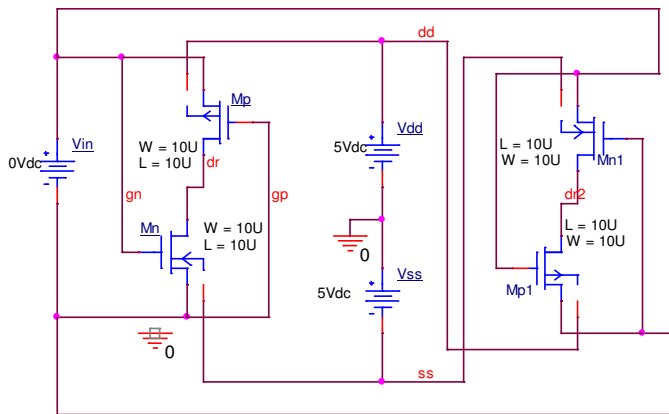- a) Make an analytic analysis of the DC behavior of the resistor on the left (made of Mn and Mp with leads fed by Vin) to give its Iin as a function of Vin, $I_{in}=f(V_{in})=-I(V_{in})$, for $0 \leq V_{in} \leq V_{dd}$. Assume that Mp is completely complementary to Mn.
- b) Obtain Spice curves for the following circuit using MNMOSIS and MPMOSIS transistors. Run for $-V_{dd} \leq V_{in} \leq V_{dd}$.
- c) Compare the Spice results with the theoretical $I_{in}=f(v_{in})$.
- d) Attach the floating ground to the source of Mn and discuss the problem that occurs.



Reference: Y. Ota and B. M. Wilamowski, "CMOS Implementation of a Voltage-Mode Fuzzy Min-Max Controller," Journal of Circuits, Systems, and Computers, Vol. 6, No. 2, pp. 171-184, April, 1996.

2. (50 points, 30 minutes)

This problem uses the standard CMOS working between ground and Vdd.

- a) The formula for the value, V_M , of V_{in} when $V_{out}=V_{in}$ ($=V_M$) as given on the web by Professor Paul A. Morton at Michigan State for ECE 410 Lecture note 7.5 is

$$V_M = \frac{V_{dd} - |V_{tp}| + V_{tn} \sqrt{\frac{\beta_n}{\beta_p}}}{1 + \sqrt{\frac{\beta_n}{\beta_p}}}$$

Give the conditions under which this is true.

- b) If the Early effect is considered, the above formula changes and requires solution of a cubic equation. But when the Early voltage is large, $\lambda \ll 1$, solving the cubic can be avoided by simply modifying the above equation using the approximations $1/(1+x)=1-x$ and $\sqrt{1+x}=1+x/2$. Use these approximations to give an improved equation for V_M .
- c) Evaluate V_M for the CMOS 4007 transistors using $V_{dd}=6V$ first when $\lambda=0$ and then when $\lambda \neq 0$ and compare. The Spice models for these are on the course web page.

3. (50 points, 20 minutes)

The following NMOS transistor works in sub-threshold for which the law is

$$I_D = I_S e^{V_{GS}/nV_T} (1 - e^{-V_{DS}/V_T})$$

where V_T =thermal voltage=0.026V, $n=3$, I_S =saturation current=20E-18 (includes other factors such as VTO).

- a) Find the small signal conductance $g=dI/dV$ when biased at $V_b > 0$.
- b) This circuit is claimed to give very large resistance for small signals. Determine if this is the case when it is biased at $V_b=0.6V$.
- c) What happens if $V < 0$?

