


b) slope =  $-\frac{1}{R} = \frac{-3 \times 10^{-3}}{5-1} = \frac{-3}{4} \times 10^{-3} \Rightarrow R = \frac{4}{3} \times 10^3 = 1.33 \text{ k}\Omega$

c)  $I_{i_{in}} = \left. \frac{di}{dv} \right|_{v=1} = [3 + 4 \times 0] \times 10^{-3} = 3 \text{ mA}$


d)  $V_{out} = R I_{i_{in}} = \frac{4}{3} \times 10^3 \times 3 \times 10^{-3} = 4 \text{ V} \equiv E - V_{i_{in}} = 5 - 1$

e)  $g'_d = \left. \frac{\partial i}{\partial v} \right|_{v=V_{bias}} = 4 \times 10^{-3} \left[ (v-0)(v-\frac{3}{2}) + (v-\frac{1}{2})(v-\frac{3}{2}) + (v-\frac{1}{2})(v-1) \right] \Big|_{v=1}$   
 $= 4 \times 10^{-3} \left[ (1-\frac{1}{2})(1-\frac{3}{2}) \right] \Big|_{v=1} = 4 \times 10^{-3} \left[ \frac{1}{2}(-\frac{1}{2}) \right]$   
 $= -1 \times 10^{-3} \text{ S}$

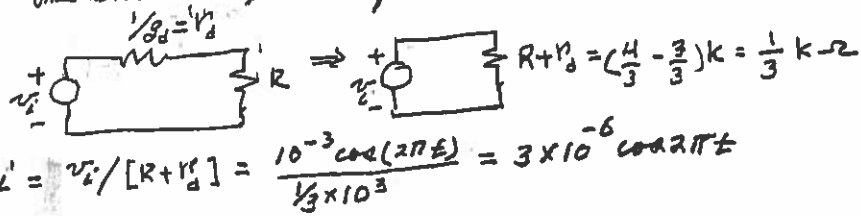5) The small signal equivalent circuit is



#2. see attached  
#3.

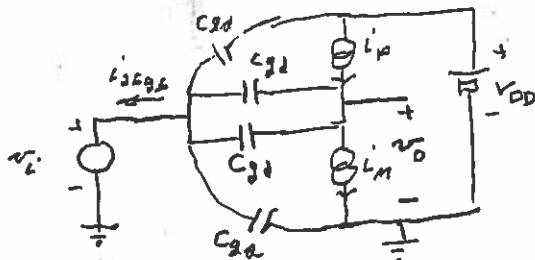

at  $v_i = V_{DD}/2$  both  $M_n$  &  $M_p$  are in saturation  
 as  $|V_{GS}| - |V_{TO}| < V_{DD} = |V_{DS}|$

then  
 $i_p = k_p (V_{DD} - v_i - |V_{TO}|)^2$   
 $i_n = k_n (v_i - V_{TO})^2$   
 $k_p = \frac{k_p}{2} \frac{W}{L}$   
 assume  $V_{TO} > 0$

assume  $v_i = (1.001) V_{DD}/2$  is near enough to  $V_{DD}/2$  to keep  $M_n$  &  $M_p$  in saturation

$$i_p - i_n = i_{c_{gd}} = 2C_{gd} \frac{d(v_o - v_i)}{dt} = k_p [(V_{DD} - V_{TO})^2 - 2(V_{DD} - V_{TO})v_i + v_i^2] - k_n [v_i^2 - 2V_{TO}v_i + V_{TO}^2]$$

$$= k_p [(V_{DD}^2 - 2V_{TO}V_{DD}) - 2(V_{DD} - 2V_{TO})v_i]$$


$$= k_p (V_{DD} - 2V_{TO}) [V_{DD} - 2v_i]$$

$$\therefore 2C_{gd} \frac{dv_o}{dt} = 2C_{gd} \frac{dv_i}{dt} + 2k_p (V_{DD} - 2V_{TO}) v_i + k_p (V_{DD} - 2V_{TO}) V_{DD}, \quad t > 0$$

for  $t > 0$ ,  $v_i = 1.001 V_{DD}/2$ ,  $dv_i/dt = 0$

$$\Rightarrow \frac{dv_o}{dt} = -\frac{k_p}{C_{gd}} (V_{DD} - 2V_{TO}) (1.001) \frac{V_{DD}}{2} + \frac{k_p}{C_{gd}} (V_{DD} - 2V_{TO}) \frac{V_{DD}}{2} = -\frac{(0.001)k_p}{C_{gd}} (V_{DD} - 2V_{TO}) \frac{V_{DD}}{2}$$
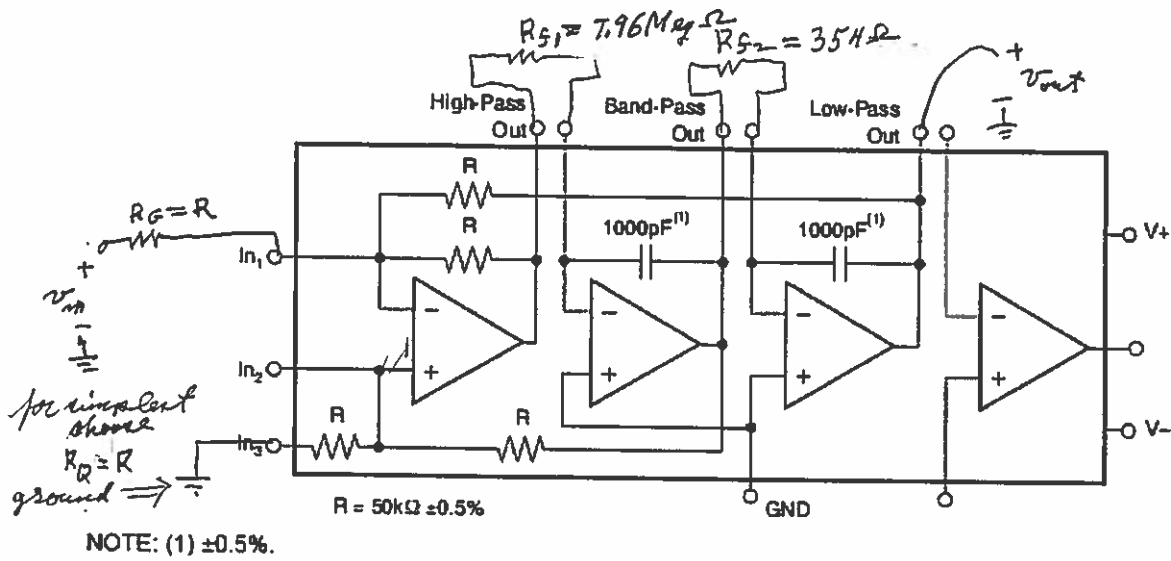
$$= -0.001 \frac{k_p}{C_{gd}} (V_{DD} - 2V_{TO}) \frac{V_{DD}}{2}, \quad t > 0, \quad v_o(0) = V_{DD}/2$$



#1. Let  $A_0 = -1 = -\frac{R_1}{R_2} = -\frac{R}{R_G} \Rightarrow R_G = R = 50k\Omega$

for  $\omega_m^2 = (6\pi \times 10^3)^2 = \frac{R_2}{R_1 R_{S1} R_{S2} C_1 C_2} = \frac{R}{R R_{S1} R_{S2} C^2} \Rightarrow R_{S1} R_{S2} = \frac{1}{\omega_m^2 \times (10^3 \times 10^{-12})^2}$

$$= \frac{10^{18}}{36\pi^2 \times 10^6} = \frac{10^{12}}{36\pi^2} \approx 28.4 \times 10^8$$

for  $Q = 100 = \left[1 + \frac{R_4}{R_Q}\right] \left[\frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_G}}\right] \left[\frac{1}{R_2} \frac{R_{S1} C_1}{R_{S2} C_2}\right]^{1/2}$

$$= \left[1 + \frac{R}{R_Q}\right] \left[\frac{R}{3} \cdot \frac{1}{R}\right] \left[\frac{R_{S1}}{R_{S2}}\right]^{1/2} \Rightarrow \frac{R_{S1}}{R_{S2}} = \frac{10^4 \cdot 3^2}{(1 + R/R_Q)^2} = \frac{9 \times 10^4}{(1 + R/R_Q)^2}$$

$$\therefore R_{S1} = \frac{10^{12}}{36\pi^2} \cdot \frac{1}{R_{S2}} \Rightarrow \frac{R_{S1}}{R_{S2}} = \frac{10^{12}}{36\pi^2} \cdot \frac{1}{R_{S2}} = \frac{9 \times 10^4}{(1 + R/R_Q)^2}$$

$$\Rightarrow R_{S2}^2 = \frac{10^{12}}{36\pi^2} \times \frac{1}{9} \times \frac{1}{10^4} \times (1 + R/R_Q)^2 = 10^8 \times \frac{1}{9 \times 36\pi^2} \cdot (1 + R/R_Q)^2$$

$$\Rightarrow R_{S2} = \frac{1}{3 \times 6\pi} \times 10^4 (1 + R/R_Q)$$

for simplified choice  $R_Q = R \Rightarrow R_{S2} = \frac{1 \times 2}{3 \times 6\pi} \times 10^4 = \frac{1}{9\pi} \times 10^4$  ;  $R_{S1} = \frac{10^{12}}{36\pi^2} \times \frac{1}{\frac{1}{9\pi} \times 10^4} = \frac{10^8}{4\pi} = \frac{25 \times 10^6}{\pi}$

$$\approx 0.03537 \times 10^7 \qquad \approx 7.958 \times 10^6$$

$$\approx 354\Omega \qquad \approx 7.96M\Omega$$