
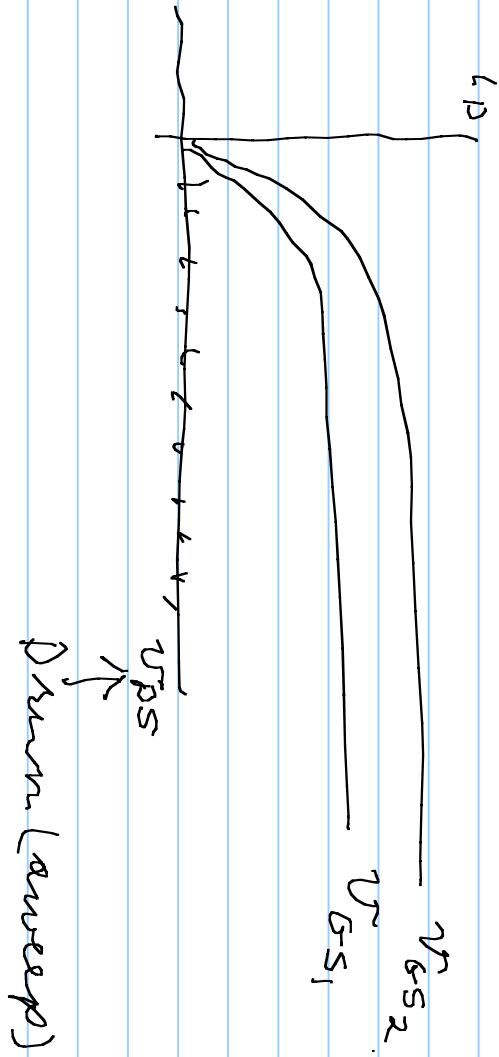


Sketch Approx  $l_D$  vs  $U_{DS}$  &  $U_{GS}$  curves

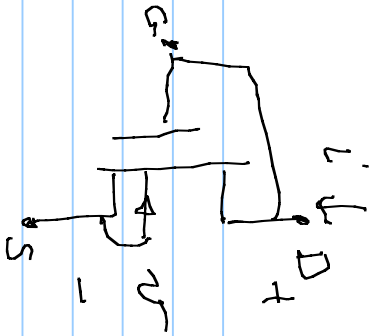

EE303H  
09/11/14



$$V_{GG} = V_{DS} > V_{T0}$$

$0 < V_{GG} - V_{T0} < V_{DS} = V_{GS}$   
 Turn on  
 $> 0 =$  enhancement  
 N channel


NMOS



for  $V_{DS} < V_{T0}$ ,  $i_D = 0$  as off

for  $V_{DS} > V_{T0}$  are in saturation


$$i_D = \frac{k_p}{2} \frac{W}{L} (V_{DS} - V_{T0})^2 (1 + \lambda V_{DS})$$
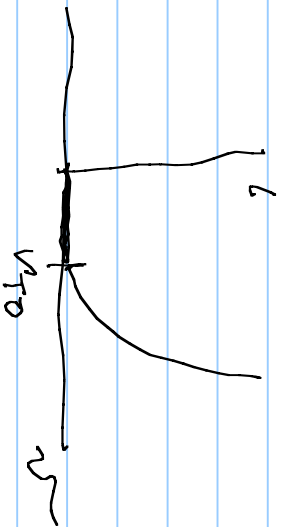
$$\approx \frac{k_p}{2} \frac{W}{L} (V_{DS} - V_{T0})^2$$




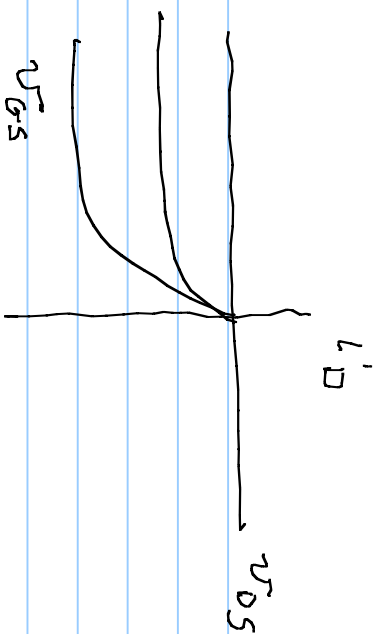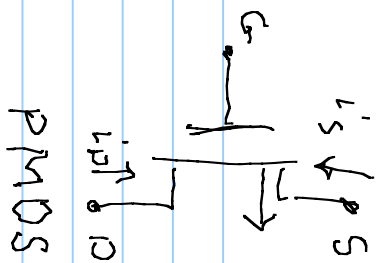


All signs  
reversed from  
NMOS

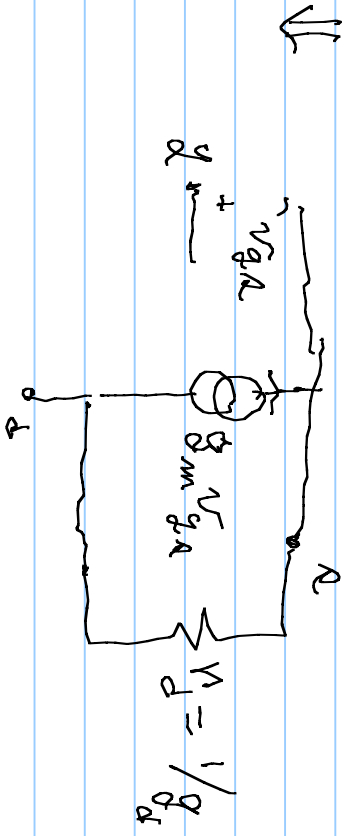

CMOS

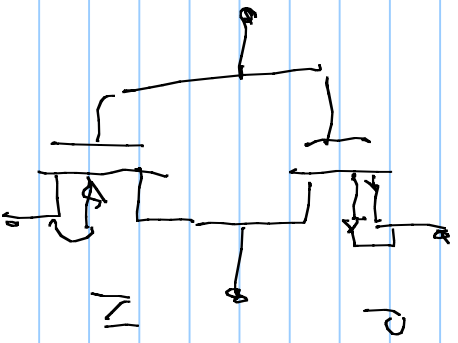


draining

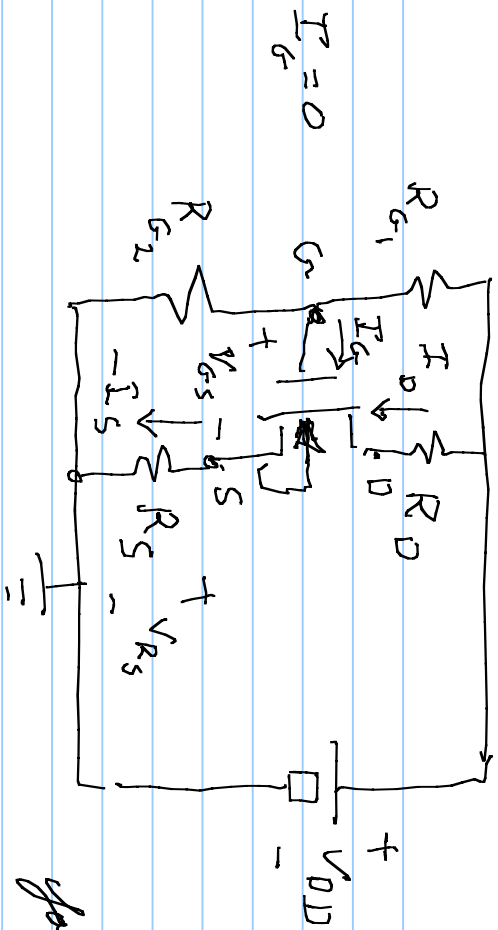

$$V_{RS} = R_S I_D$$

$$V_{GS} = V_{RG2} - V_{RS}$$

you can find the operating point

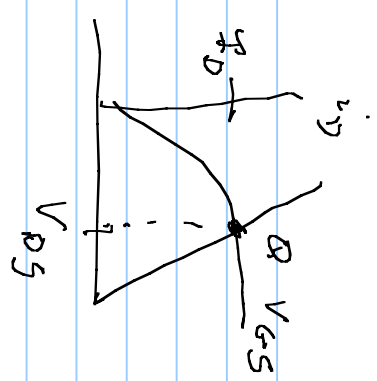

$$V_{RG2} = V_G = \frac{R_{G2}}{R_{G1} + R_{G2}} V$$

as a voltage divider when  $I_G = 0$

Ex: if  $I_D \approx 2 \text{ mA}$ ,  $R_D = 1 \text{ k}\Omega$ ,  $R_S = 1 \text{ k}\Omega$

$$V_{DS} = V - I_D (R_S + R_D) = V - 2 \times 10^{-3} \times 2 \times 10^3 = V - 4$$

$\Rightarrow$  given  $V_{DS} = 3 \text{ V} \Rightarrow V = 7 \text{ V}$

if  $V_{GS} = 1.5 \text{ V}$  Then  $\Rightarrow V_{R_{G2}} = V_{GS} + V_{RS} = 1.5 + 2 \times 10^{-3} \times 1 \times 10^3 = 3.5 \text{ V}$

$$V_{R_{G2}} = \frac{R_{G2}/R_{G1}}{1 + R_{G2}/R_{G1}} \times V \Rightarrow \frac{3.5}{7} = \frac{1}{1 + R_{G1}/R_{G2}} \Rightarrow$$

$$\Rightarrow \frac{R_{G1}}{R_{G2}} = \frac{1}{3.5} - 1 = 2 - 1 = 1 \Rightarrow R_{G1} = R_{G2} \text{ choose } R_{G1} = 1 \text{ Meg}$$

$$g_m = \frac{\partial I_D}{\partial V_{GS}} \Big|_Q = \frac{2 I_D}{(V_{GS} - V_{T0})}$$

$$g_d = \frac{\partial I_D}{\partial V_{DS}} \Big|_Q = \lambda I_D = \lambda \times 2 \times 10^{-3}$$

$$= \frac{d}{dV_{DS}} \left( \frac{k_n^2 W}{2L} (V_{GS} - V_{T0})^2 (1 + \lambda V_{DS}) \right)$$

$$\text{if } V_{T0} \approx 1/2 \text{ V} \quad \lambda = \frac{1}{10}$$

$$\text{then } g_m = 4 \times 10^{-3} \text{ V}$$

$$g_D = \frac{1}{10} \times 2 \times 10^{-3} = 2 \times 10^{-4}$$

$$r_D = \frac{10^4}{2} = 5 \times 10^3 \Omega$$

$$\text{if } \text{may } \frac{v_o}{v_i} = -g_m R_L = -4 \times 10^{-3} \times 1 \times 10^3 = -4$$

but  $R_L$  seems in parallel with  $g_D \Rightarrow g_{m \text{ eff}} = \frac{5}{6} g_m$