
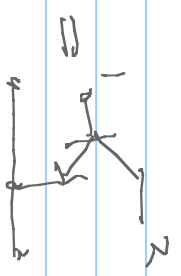


Y matrix

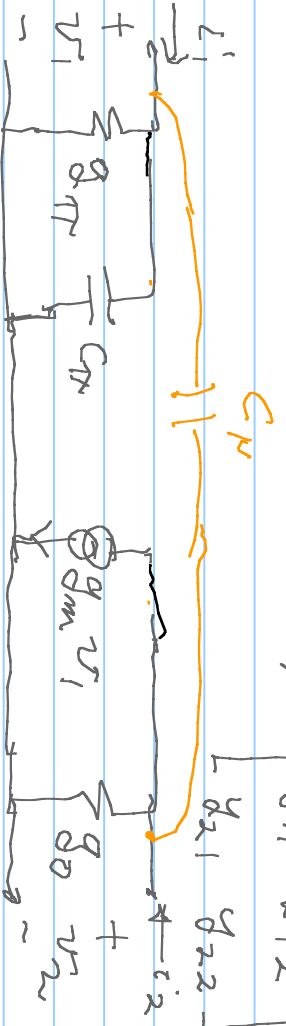

$$\begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = Y \begin{bmatrix} v_1 \\ v_2 \end{bmatrix}$$

$$Y = \begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix}$$




$$i_1 = g_{m1} v_1 + s C_x v_1 = y_{11}(s) v_1 + 0 \cdot v_2$$

$$i_2 = g_{m2} v_1 + g_o v_2$$


$$\begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} g_{m1} + s C_x & 0 \\ g_{m2} & g_o \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix}$$
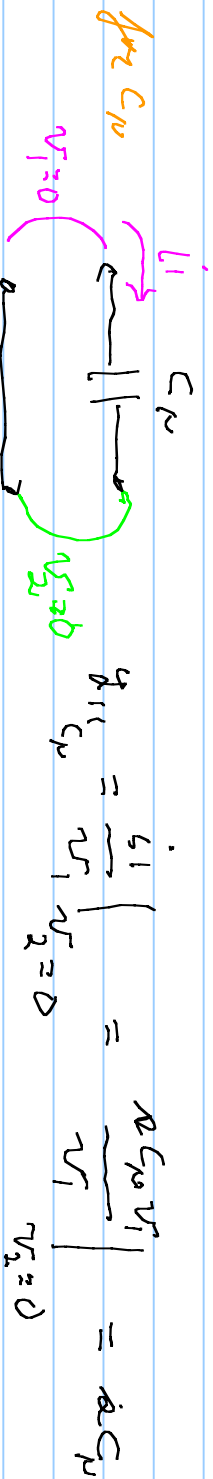
$$Y_{BJT} = \begin{bmatrix} g_m + a_{CP} & 0 \\ g_m & g_D \end{bmatrix}$$



$$-a_{CP} = y_{12, C_P} = \frac{i_1}{v_2} \Big|_{v_1=0} = \frac{-a_{CP} v_2}{v_2} \Big|_{v_1=0} \quad \text{apply } v_2 \text{ & find } i_1!$$
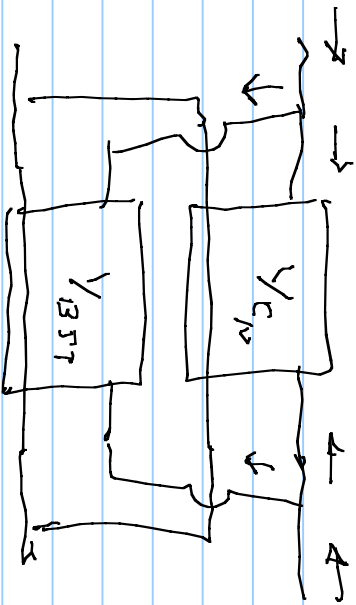
$$Y_{C_P} = \begin{bmatrix} a_{CP} & -a_{CP} \\ -a_{CP} & a_{CP} \end{bmatrix} = a_{CP} \begin{bmatrix} 1 & -1 \\ -1 & 1 \end{bmatrix}$$



$$I = Y_{Cp} V + Y_{B5T} V = (Y_{Cp} + Y_{B5T}) V$$


$$Y_{\text{total}} = Y_{Cp} + Y_{B5T}$$

$$Y_{\text{total}} = \left[ g_{\pi} + a (g_{\pi} + c_{\mu}) \right. \\ \left. g_o - a c_{\mu} \right]$$

$$\left[ -a c_{\mu} \right. \\ \left. g_o + a c_{\mu} \right]$$

( $Y$  for  $T$  equivalent  
high frequency  
analysis of the BJT)


# Biasing for BJT

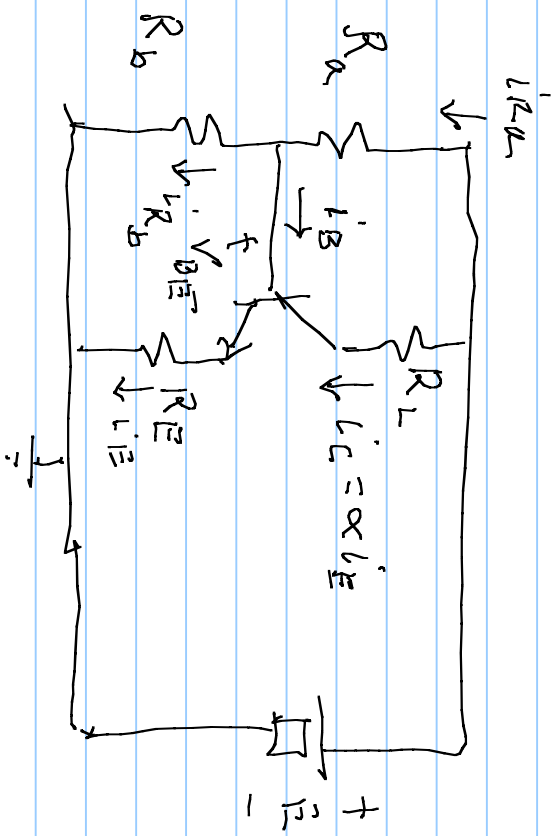

given  $A_{v} = -g_m R_L$ ,  $V_E$ ,  $\beta$ ,  $I_B$ ,  $V_{CE}$  &  $V_{BE} \approx 0.7$   
 derive to choose  $R_a, R_b, R_E, R_L$

max KVi, KCL & Laws of components to

more part of E to left

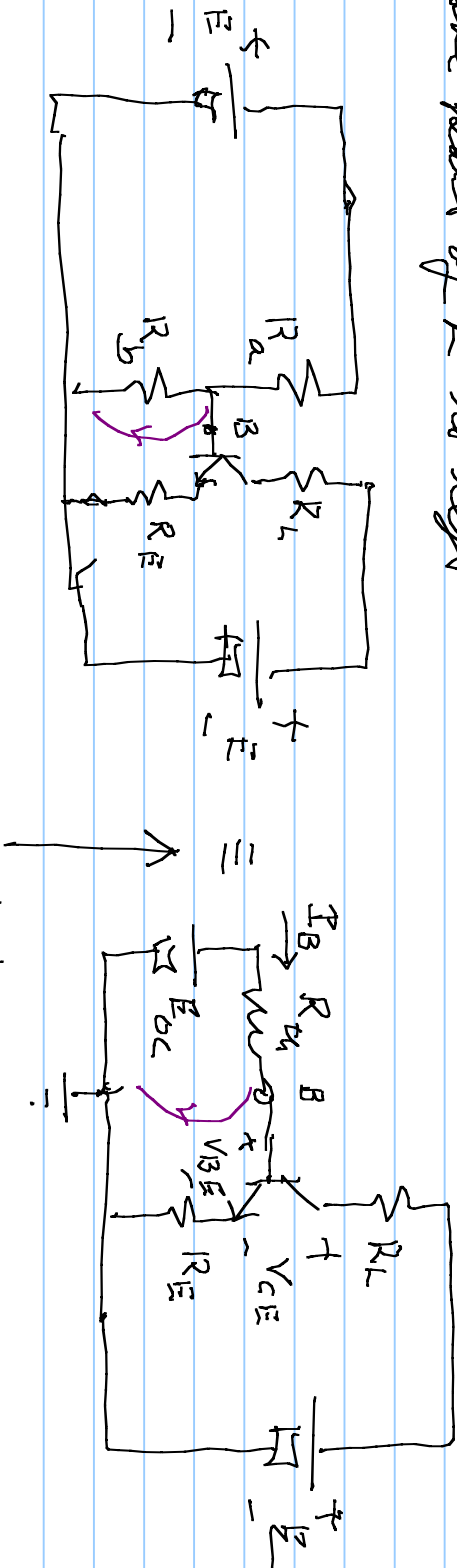

Shortening  
Thevenin

$$E_0 = \frac{R_a}{R_a + R_b} \cdot E$$

$$I_{SC} \text{ left} = \frac{E}{R_a} = \frac{E_{OC}}{R_{th}} \Rightarrow R_{th} = \frac{E_{OC}}{E} \cdot R_a = \frac{R_a}{R_a + R_b} \cdot R_a$$

$$R_{th} = \frac{R_a}{1 + R_b/R_a}, \quad E_0 = \frac{1}{1 + R_b/R_a} E$$

KVL input loop:  $0 = -E_0 + R_a I_B + V_{BE} + R_E (-I_E)$

(3rd KVL loop)  $\Rightarrow 0 = -\frac{1}{1 + R_b/R_a} E + \frac{R_a}{1 + R_b/R_a} I_B + 0,7 + R_E \frac{\beta}{\alpha} I_B$  1)

KVL output loop  $\Rightarrow 0 = -E + R_L \beta I_B + V_{CE} + R_E \frac{\beta}{\alpha} I_B$

( $R_L, R_E$  free of known  $V_{CE}$ )  $\Rightarrow E = (R_L + \frac{R_E}{\alpha}) \beta I_B + V_{CE}$  2)

And  $I_E \approx -I_{em} R_L \approx -\frac{\beta I_B}{V_T} R_L$  gives  $R_E$

1) gives  $R_a$  and  $R_b/R_a$  once  $R_E$  is given by 2)

