

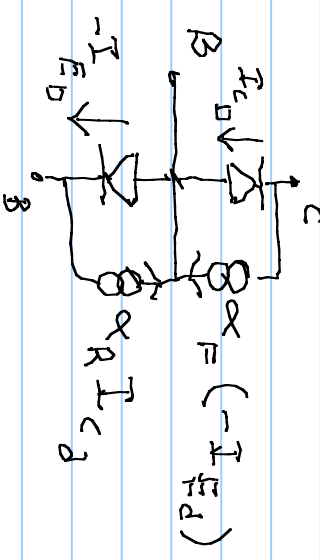



Ebers-Moll model of BJT

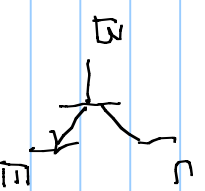

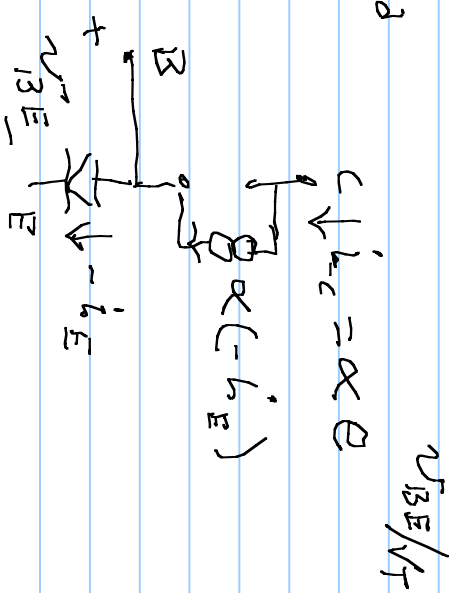in forward active region
(large signal model)




How to make a capacitor

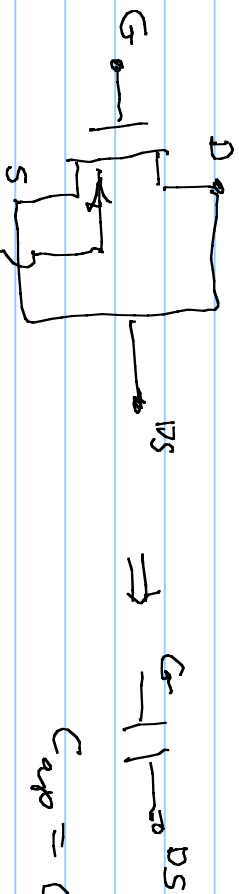

lowest potential in circuit

$$C_{ap} = C_{GS} + C_{GD}$$

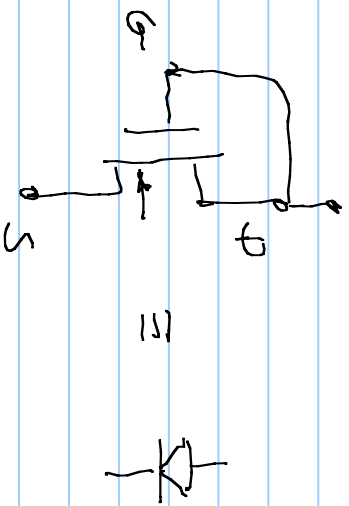

$$V_{GS} = V_{DS}$$


$$V_{GS} - V_{th} \leq V_{DS} \text{ are in saturation}$$

holds for this diode


$$i_D = \frac{1}{2} \mu_p C_{ox} \frac{W}{L} (v_{DS} - V_{T0})^2 (1 + \lambda v_{DS})$$

if $v_{DS} > V_{T0}$


$$= 0 \text{ if } v_{DS} < V_{T0}$$

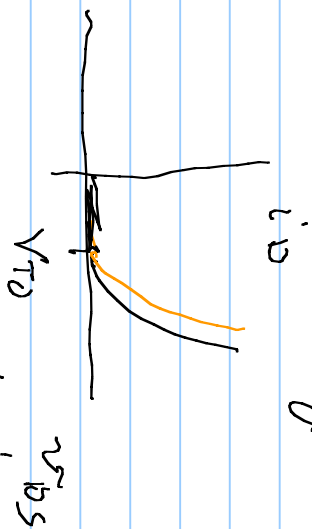


Current mirror MOS

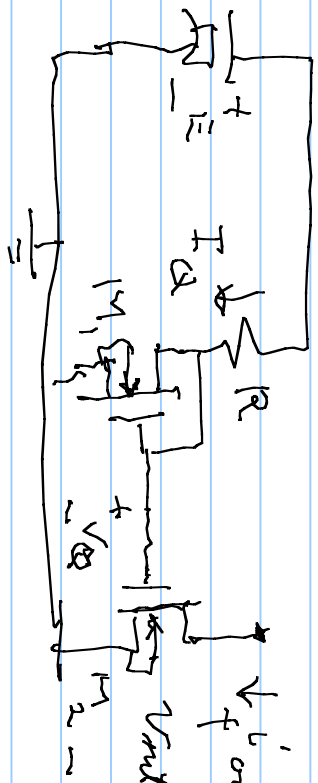

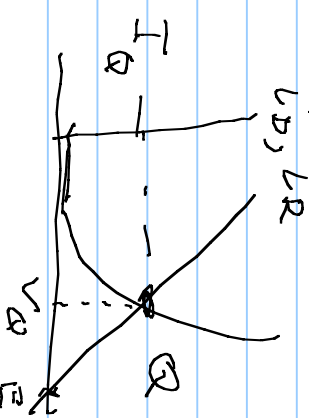$v_{out} = V_Q - I_Q R$
 if M_2 is in saturation
 $\Rightarrow v_{out} > V_Q - V_{T0}$



can make R with an MOS diodes

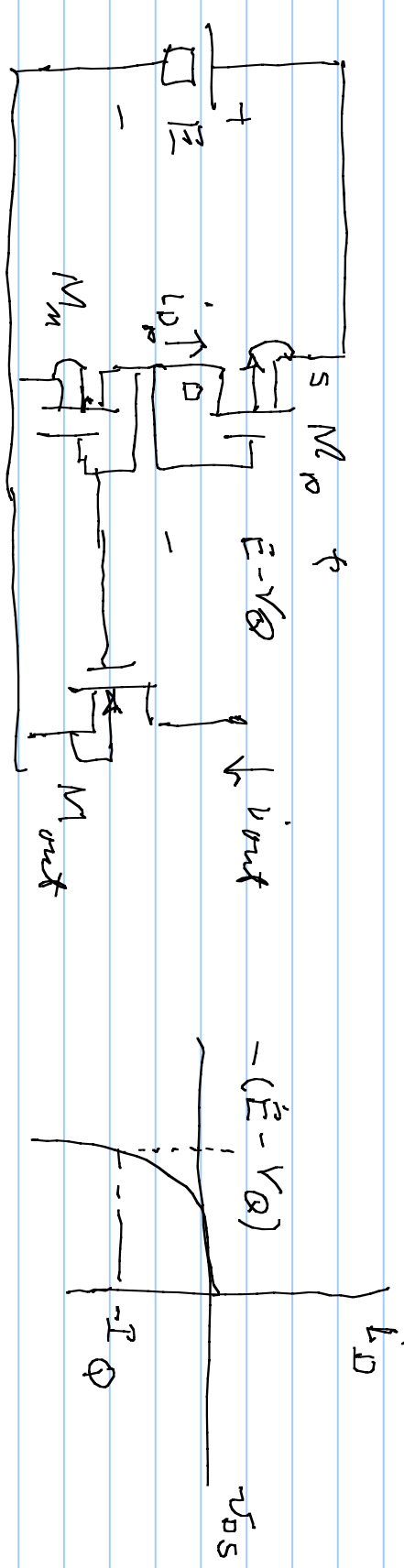


$$-I_{DQ} = \frac{K_P}{2} \frac{W}{L} (-v_{DS} - |V_{TQ}|)^2 = -I_Q$$



$$\Rightarrow I_Q = \frac{K_P}{2} \frac{W}{L} (E - V_Q - |V_{TQ}|)^2 \Rightarrow \text{gives } \frac{W}{L} \text{ for } M_P$$

$$\frac{w}{L} = \frac{2I_D Q}{K_P ((E - V_Q) - (V_{DQ1}))^2}$$


But things vary with output voltage

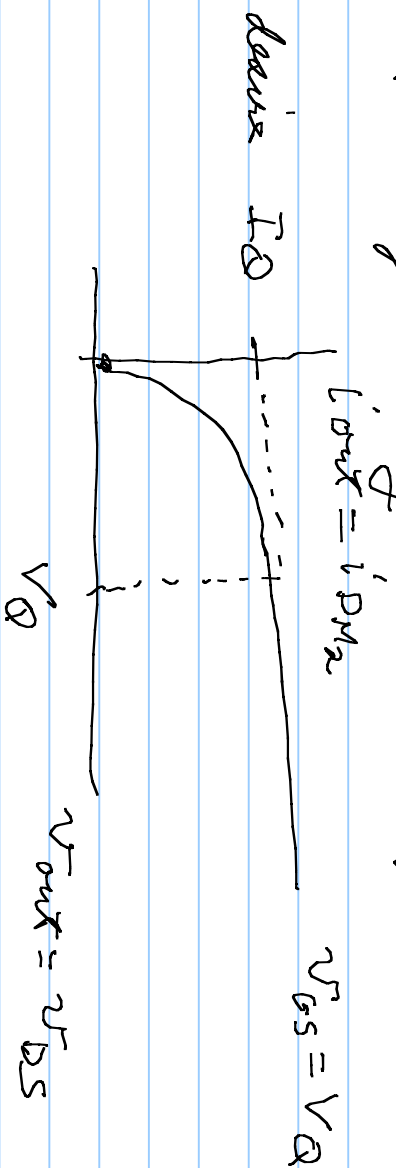

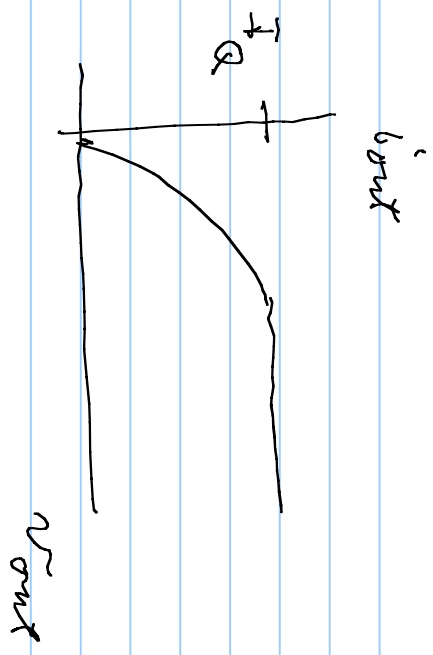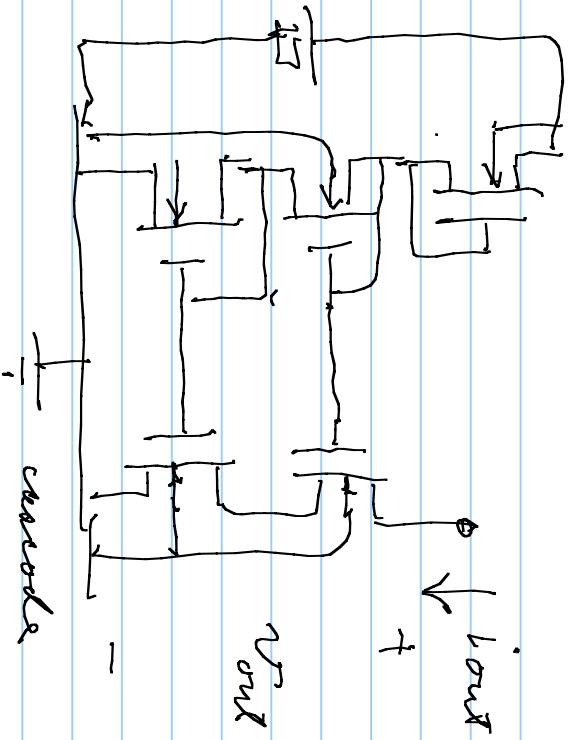as I_{out} changes if
the load V_{out}
changes




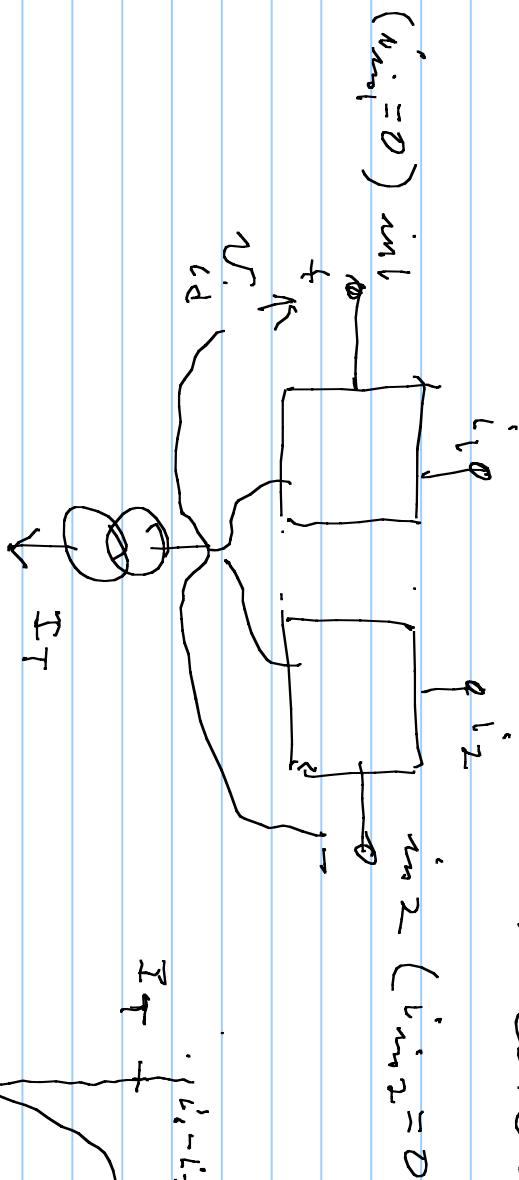
Differential pair (used for OTA = operational transconductance amplifiers)





$$i_1 + i_2 = I_T$$

$$i_1 - i_2 = S(v_{1d})$$

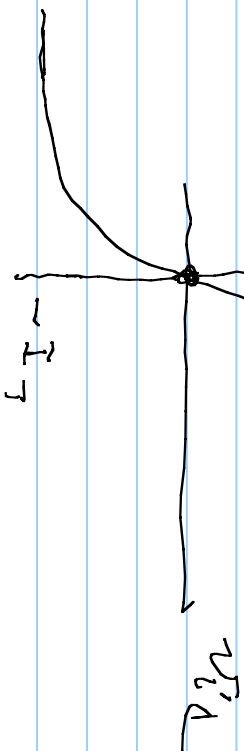

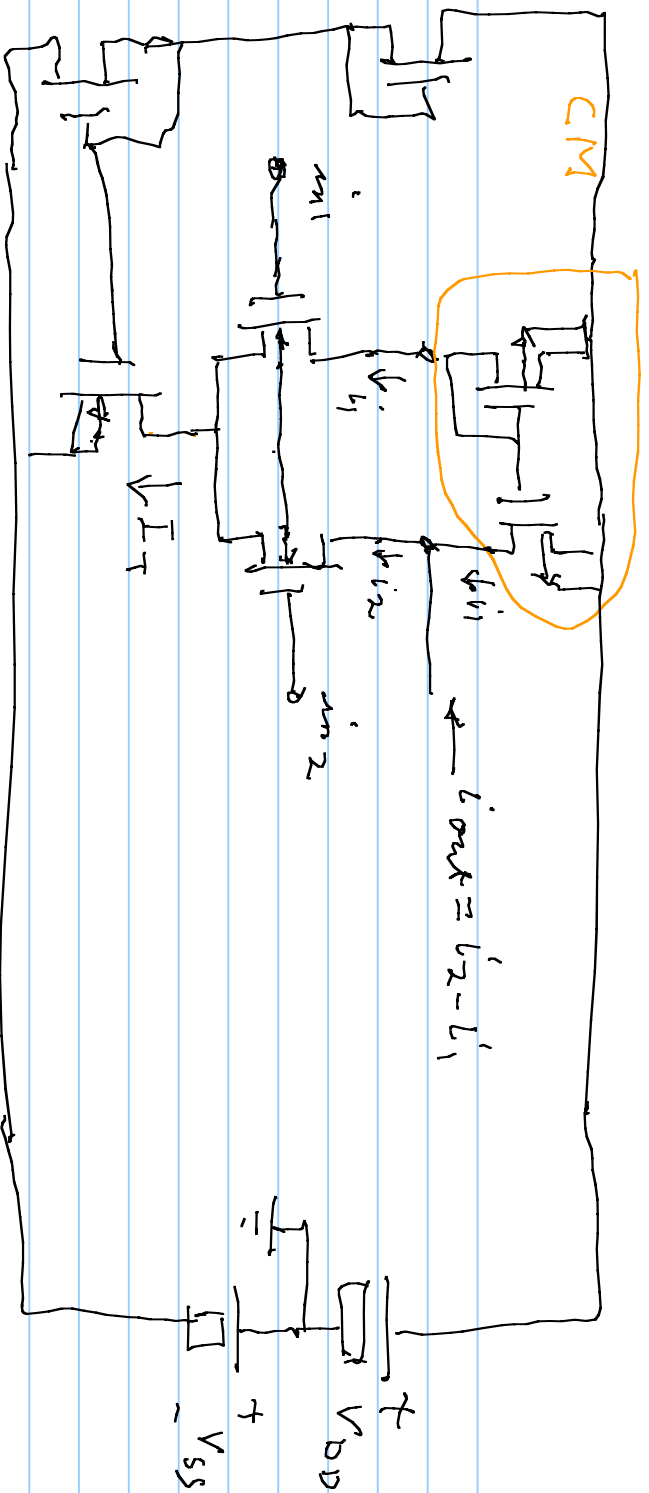

\Rightarrow an OTA

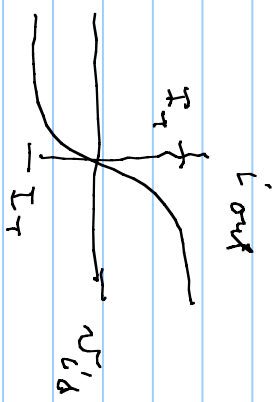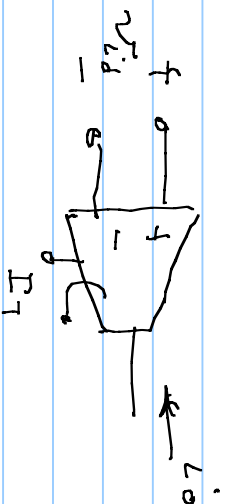

Small signal

$$L_o = g_m r_{id}$$

$$\text{Slope} = g_m$$

if made with BJTs $i_0 = I_T \tanh(\nu_{id}/2V_T)$

assume for MOS that all transistors are in saturation

$$\nu_{i1} = \nu_{G1} - \nu_{G2} \quad ; \quad i_1 = i_{D1} \quad , \quad i_2 = i_{D2}$$

$$i_D = k(\nu_{GS} - V_{T0})^2$$

$$k = \frac{1}{2} \mu_n^2 \frac{W}{L}$$

$$\nu_{GS1} = V_{T0} + \sqrt{\frac{i_D}{k}} \quad , \quad \nu_{GS2} = V_{T0} + \sqrt{i_D/k}$$

$$\nu_{iD} = \nu_{GS1} - \nu_{GS2} = \sqrt{\frac{i_D}{k}} - \sqrt{\frac{i_D}{k}}$$