

Differential pairs

MOS p. 595 \Rightarrow 637 Fig. 8.32I_{D1a} p. 596, eqn. (8.23 & 24)

curvts p. 598, Fig. 8.7

BJT p. 615

I_{E1a}, p. 616, eqn. (8.73 & 74)curvts, p. 617 \Rightarrow p. 658, Fig. 8.43

Other Top - amps, p. 1003, Fig. 12.13

$$v_{Ld} = v_{G51} - v_{G52} = \sqrt{\frac{L_1}{R}} - \sqrt{\frac{L_2}{R}}$$

$$L_0 = L_1 - L_2 \quad ; \quad L_1 + L_2 = I_T$$

$$L_2 = L_1 - L_0 = I_T - L_1 \Rightarrow L_0 = 2L_1 - I_T$$

$$v_{Ld}^2 = \frac{L_1}{R} + \frac{L_2}{R} - 2\sqrt{\frac{L_1 L_2}{R}}$$

$$= \frac{L_1}{R} + \frac{L_0 - L_1}{R} - 2\sqrt{\frac{L_1^2 - L_1 L_0}{R}} = \frac{2L_1 - L_0}{R} - 2\sqrt{\frac{L_1^2 - L_1 L_0}{R}}$$

$$R v_{Ld}^2 - I_T^2 = -2\sqrt{L_1^2 - L_1 L_0} \Rightarrow 4(L_1^2 - L_1 L_0) = (I_T - R v_{Ld}^2)^2$$

$$L_1^2 - L_1 L_0 - \frac{1}{4}(I_T - R v_{Ld}^2)^2 = 0 \Rightarrow \text{ma } L_0 = 2L_1 - I_T$$

$$\Rightarrow L_1^2 - 2L_1^2 + L_1 I_T - \frac{1}{4}(I_T - R v_{Ld}^2)^2 = 0 \Rightarrow L_1^2 - I_T L_1 + \frac{1}{4}(I_T - R v_{Ld}^2)^2 = 0$$

$$i_1 = \frac{1}{2} I_T \pm \frac{1}{2} \sqrt{I_T^2 - (I_T - k v_{iD}^2)^2} = \frac{1}{2} I_T \pm \frac{1}{2} I_T \sqrt{1 - (1 - k \frac{v_{iD}^2}{I_T})^2}$$

$$i_2 = I_T - i_1 = \frac{1}{2} I_T \mp \frac{1}{2} I_T \sqrt{1 - 1 + 2 \frac{k v_{iD}^2}{I_T} - (k \frac{v_{iD}^2}{I_T})^2} = \frac{1}{2} I_T \left(1 \mp \sqrt{\frac{2k}{I_T}} v_{iD} \left(1 - \frac{k v_{iD}^2}{2 I_T} \right) \right)$$

$$\Rightarrow i_1 = \frac{I_T}{2} \left(1 \pm \sqrt{\frac{2k}{I_T}} v_{iD} \sqrt{1 - \left(\frac{k}{2 I_T} v_{iD}^2 \right)^2} \right)$$

$$i_2 = \frac{I_T}{2} \left(1 \mp \sqrt{\frac{2k}{I_T}} v_{iD} \sqrt{1 - \left(\frac{k}{2 I_T} v_{iD}^2 \right)^2} \right)$$

should be (by book)


$$i_{D1} = \frac{I_T}{2} + \left(\sqrt{k I_T} \right) \frac{v_{iD}}{2} \left[1 - \underbrace{\left(\frac{v_{iD}^2}{2} \right)^2}_{\text{negligible } (v_{iD}^2/2)^2 < I_T/k} \right]$$

$$i_{D2} = \frac{I_T}{2} - \left(\sqrt{k I_T} \right) \frac{v_{iD}}{2} \left[1 - \frac{\left(v_{iD}^2/2 \right)^2}{I_T/k} \right]$$

$$l_0 = l_0' - l_0'' = 2 \cdot \sqrt{k I_T} \cdot \frac{v_{id}}{2} \sqrt{1 - \frac{k}{I_T} (v_{id}/2)^2}$$

$$= f(x); \quad x = \sqrt{\frac{k}{I_T}} (v_{id}/2)$$
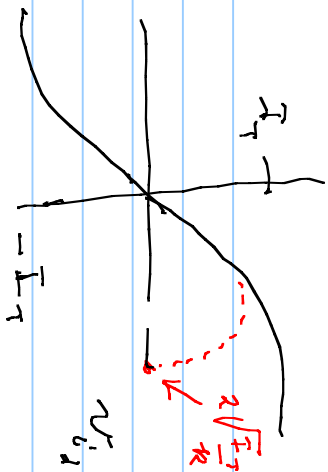
$$l_0 = 2 \sqrt{I_T} \sqrt{\frac{k}{I_T}} \cdot \frac{v_{id}}{2} \sqrt{1 - \left(\sqrt{\frac{k}{I_T}} \cdot \frac{v_{id}}{2} \right)^2} = 2 \sqrt{I_T} \cdot x \sqrt{1-x^2}$$



$$l_0 = l_0' - l_0''$$


$l_0 = f(x) \Rightarrow$ max: $\frac{d f(x)}{d x} = 0$ gives maximum x

$$\frac{d}{d x} \left[\sqrt{I_T} \cdot x \sqrt{1-x^2} \right] = \sqrt{I_T} \left[\sqrt{1-x^2} + I_T x \cdot \frac{1}{\sqrt{1-x^2}} \cdot (-2x) \cdot \frac{1}{2} \right]$$

$$x^2 \neq 1 \quad = \sqrt{I_T} \left\{ \frac{1-x^2 + x(-x)}{\sqrt{1-x^2}} \right\} = \sqrt{I_T} \frac{(1-2x^2)}{1-x^2}$$

max of $x^2 = 1/2 \Rightarrow x = 1/\sqrt{2} =$
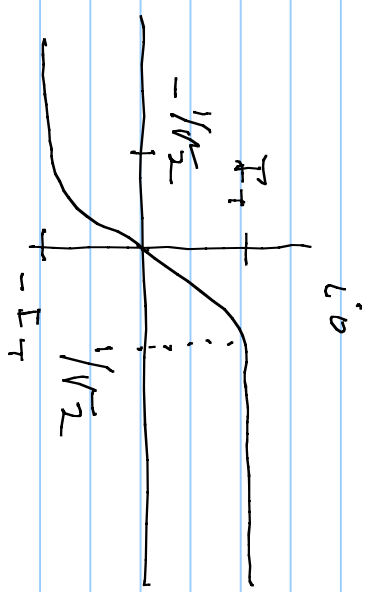
$$i_o = 2I_T \cdot \chi \sqrt{1-x^2} \Rightarrow i_o \text{ max} = 2I_T \cdot \frac{1}{\sqrt{2}} \sqrt{1-\frac{1}{2}} = \sqrt{2} I_T \cdot \frac{1}{\sqrt{2}} = I_T$$




note: $\frac{di_o}{dx} = \frac{di_o}{dx} \cdot \frac{dx}{dy} ; \frac{di_o}{dx} = 2I_T \left(\sqrt{1-x^2} - \frac{x(-2x)}{2} \right) \frac{1}{(1-x^2)}$


at $x=0, \frac{di_o}{dy} = 2I_T$

$\Rightarrow g_m = 2I_T \cdot \sqrt{\frac{R_e}{I_T}} \cdot \frac{1}{\sqrt{2}} = \sqrt{R_e I_T}$

with BJT we use similar arguments

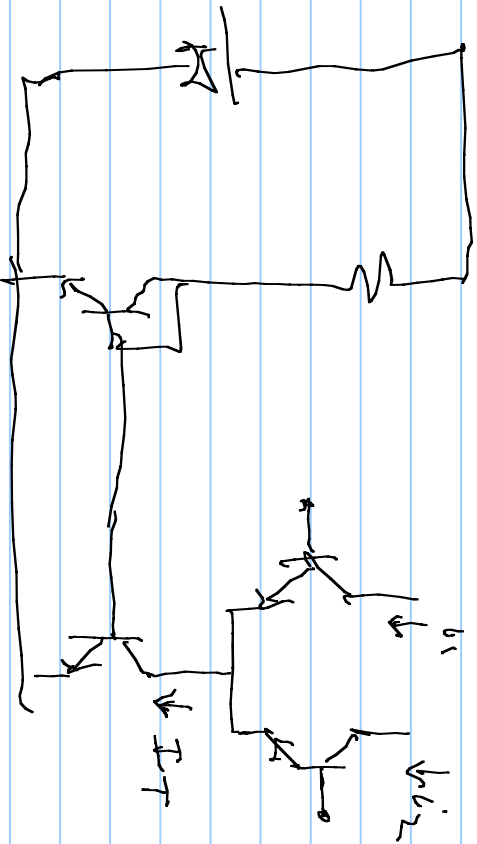
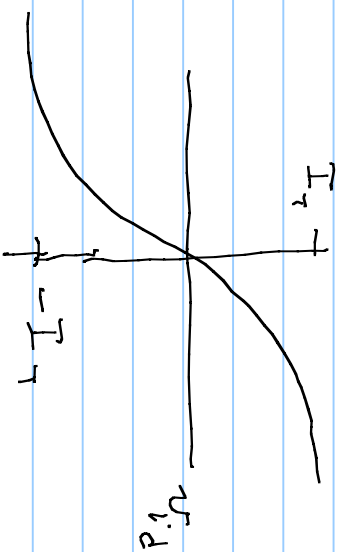
$$i_o = i_{c1} - i_{c2} = \alpha I_T \tanh\left(\frac{v_{id}}{2V_T}\right)$$



in linear mode, near $v_{id} = 0$

$$v_o = g_m v_{id} \approx 0 + \frac{di_o}{dv_{id}} \bigg|_{v_{id}=0} (v_{id} - 0) + \dots$$

$$\frac{dI_D}{dV_{GS}} \approx \alpha I_T \frac{d \tanh\left(\frac{V_{GS}}{2V_T}\right)}{dV_{GS}}$$

$$\tanh x = \frac{e^x - e^{-x}}{e^x + e^{-x}}$$

$$= \alpha I_T \cdot \left(1 - \tanh^2\left(\frac{V_{GS}}{2V_T}\right)\right) \cdot \frac{1}{2V_T}$$


$$\frac{d \tanh x}{dx} = \frac{e^x + e^{-x}}{e^{2x} + e^{-2x}} \cdot \frac{(e^x - e^{-x})^2}{(e^x + e^{-x})^2} = 1 - \tanh^2 x$$

$$\Rightarrow I_D = 0 + I_T \left(1 - \tanh^2\left(\frac{V_{GS}}{2V_T}\right)\right) \cdot \frac{1}{2V_T} \left(V_{GS} - 0\right) + \dots$$

$$= \frac{1}{2} \cdot \frac{1}{2V_T} \cdot \alpha I_T \cdot V_{GS} \quad V_{GS} = 0$$

$$\Rightarrow g_m = \alpha \frac{I_T}{2V_T}$$

also holds for MOS @ subthreshold

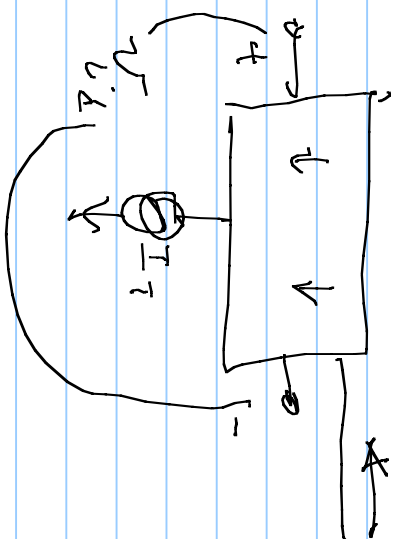



$$i_b = I_T \tan h \left(\frac{v_i}{2V_T} \right)$$


if I_T varies with another voltage then this

term becomes a

multiplier

requires $I_T > 0$

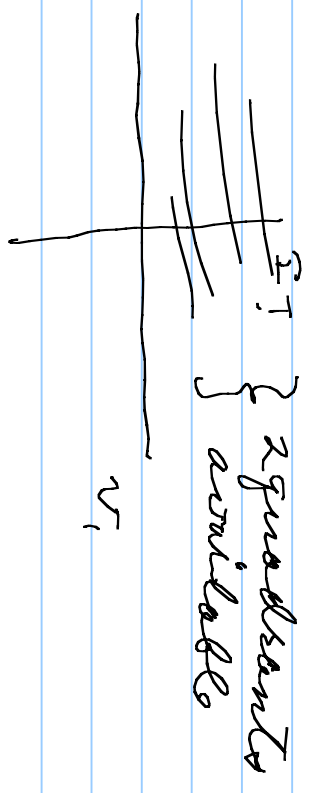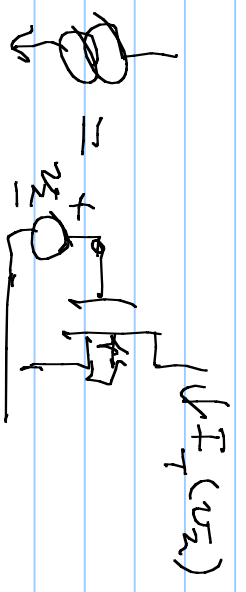

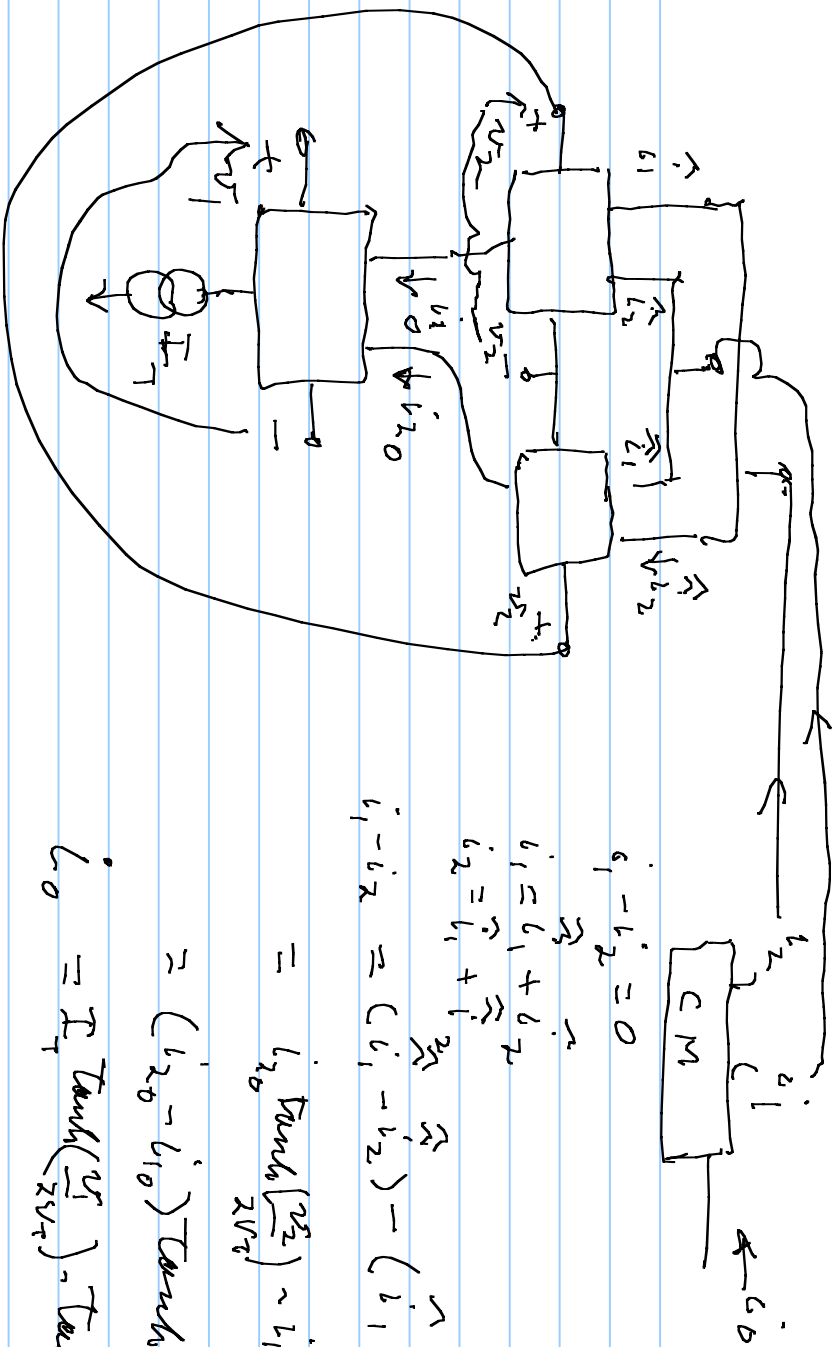

$$i_1 - i_2 = 0$$

$$i_1 = i_1 + i_2$$

$$i_2 = i_1 + i_1$$

$$i_1 - i_2 = (i_1 - i_2) - (i_1 - i_2)$$

$$= i_2 \tanh\left(\frac{v_2}{2V_T}\right) - i_1 \tanh\left(\frac{v_2}{2V_T}\right)$$

$$= (i_2 - i_1) \tanh\left(\frac{v_2}{2V_T}\right)$$

$$i_0 = I_T \tanh\left(\frac{v_2}{2V_T}\right) - \tanh\left(\frac{v_2}{2V_T}\right)$$

for v_1 & v_2 small $i_0 = \frac{I_T}{2V_T} \cdot \frac{1}{2V_T} \cdot v_1 \times v_2$