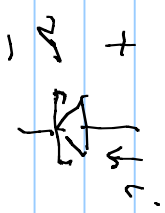


EE303H

10/07/14

Esaki diodes = tunnel diodes





negative differential resistance

$h_{fe}$  a BJT parameters  $\approx h_{21}$

when  $e \approx$  ground forward

$$\begin{bmatrix} V_1 \\ I_2 \end{bmatrix} = H \begin{bmatrix} I_1 \\ V_2 \end{bmatrix}$$
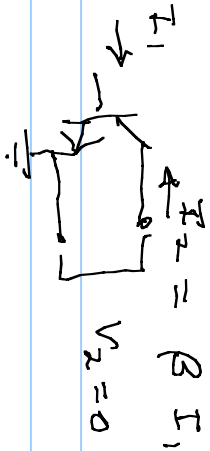
$$h_{21} = I_2 / I_1 \quad | \quad v_2 = 0$$

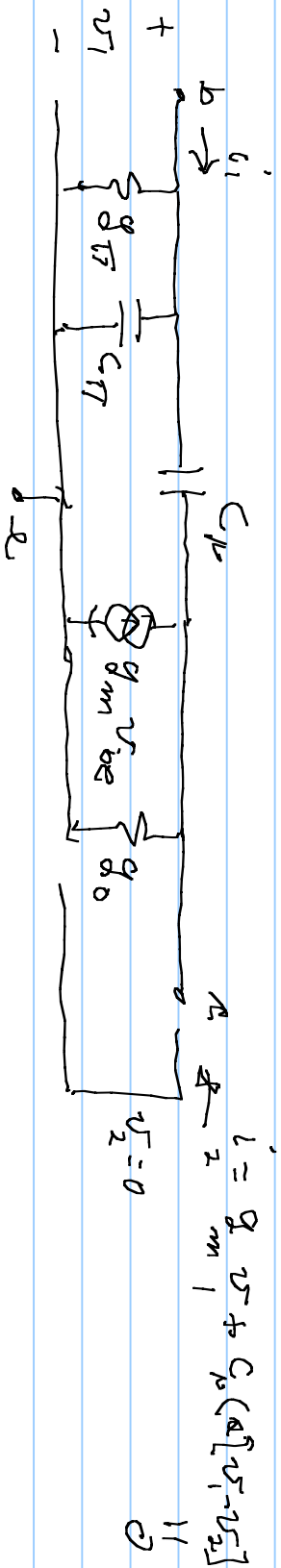


$$i_2 = (g_m + \alpha C_p) v_1 ; \quad L_1 = (g_m + \alpha C_p) v_1 + \alpha C_p v_1$$

$$= (g_m + \alpha [C_\pi + C_\mu]) v_1$$

$$\Rightarrow v_1 = \frac{i_1}{(g_m + \alpha [C_\pi + C_\mu])} \Rightarrow \frac{i_2}{i_1} = \frac{g_m + \alpha C_p}{g_m + \alpha [C_\pi + C_\mu]}$$

$$|B(\omega)| = \frac{g_m}{g_{\pi}} \left( \frac{1 + R C_p / g_m}{1 + R \left[ \frac{C_M + C_D}{g_{\pi}} \right]} \right) = \beta_0 \cdot \frac{1 + R C_p / g_m}{1 + R \left[ \frac{C_M + C_D}{g_{\pi}} \right]}$$



if  $C_p$  is small

$$\Rightarrow \beta = \beta_0 \frac{1}{1 + R/\omega} \quad \omega \approx 1/C_M \frac{3dB}{g_{\pi}}$$

$$|B(j\omega)| = \frac{\beta_0}{1 + j\omega/\omega} \quad @ \omega = \omega, \quad |B(j\omega)| = \frac{\beta_0}{\sqrt{2}}$$

$$\omega_{3dB} = 3dB \quad \text{frequency}$$

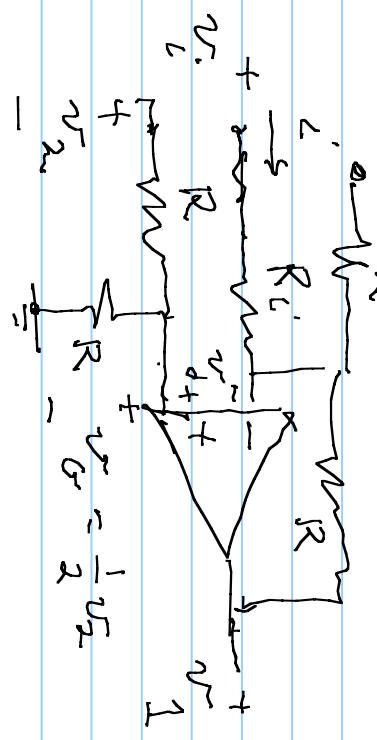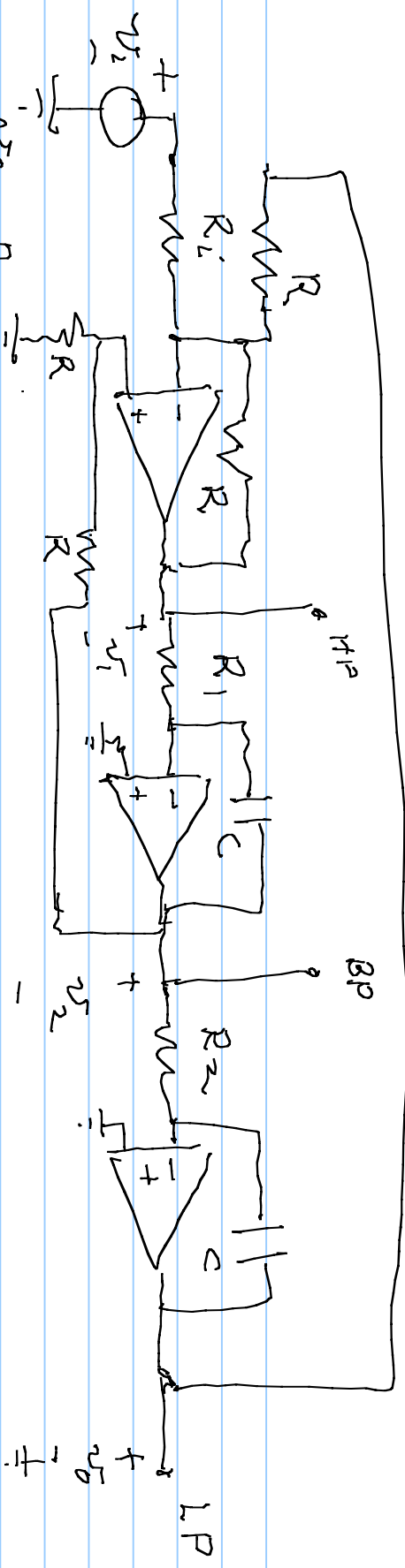TI design by VFF = universal analog filter




$$v_2 = 0, \quad \text{Cap-amp in } + \text{ or } - = 0$$

$$v_1 = -R_L' + \frac{1}{2} v_2, \quad \text{Cap-amp in } + \text{ or } - = G_L (v_1 - v_0)$$

$$+ (-\frac{R}{R}) (v_0 - v_1)$$

$$v_1 = -R G_L' v_1 + R G_L' \frac{1}{2} v_2 + \frac{R}{2} v_2 - v_0$$
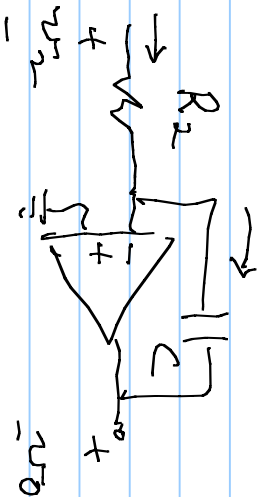
$$v_1 = -R_1 g_1 v_2 + \left(\frac{1}{2}\right)(R_2 + R_1 g_1) v_2 \sim v_0$$



$$L' = -sC v_0 = +G_2 v_2$$

$$\frac{v_0}{v_2} = \frac{G_2}{sC} = \frac{1}{R_2 C s} = \text{integrator}$$

$$\frac{v_2}{v_1} = -\frac{1}{R_1 C s} \Rightarrow v_2 = -\frac{1}{R_1 C s} \cdot v_1 \Rightarrow v_0 = -\frac{1}{R_2 C s} \cdot \frac{1}{R_1 C s} v_1$$

$$v_0 = \frac{1}{R_1 R_2 C^2 s^2} v_1 = \frac{1}{R_1 R_2 C^2 s^2} \left[ -R_2 R_1 v_1 + \frac{1}{2} (R_2 + R_1 g_1) (-R_2 C s) v_0 \sim v_0 \right]$$


$$\left[ 1 + \frac{(2+R/G_i)}{2} \left( \frac{R_2 C a}{R_1 R_2 C^2 a^2} \right) + \frac{1}{R_1 R_2 C^2 a^2} \right] = \frac{-R R_L'}{R_1 R_2 C^2 a^2} \omega_L'$$

$$\left[ a^2 + \frac{(2+R/G_i)}{2} \frac{1}{R_1 C} a + \frac{1}{R_1 R_2 C^2} \right] \omega_0 = - \frac{R R_L'}{R_1 R_2 C^2} \omega_L'$$

$$\frac{\omega_0}{\omega_L'} = T(a) = \frac{-R R_L'}{R_1 R_2 C^2} \frac{a^2 + \frac{(2+R/G_i)}{2} \frac{1}{R_1 C} a + \frac{1}{R_1 R_2 C^2}}{a^2 + \frac{\omega_0}{Q} a + \omega_0^2}$$

$$\omega_0 = \frac{1}{R_1 R_2 C^2} \Rightarrow \omega_0 = \frac{1}{\sqrt{R_1 R_2}}$$
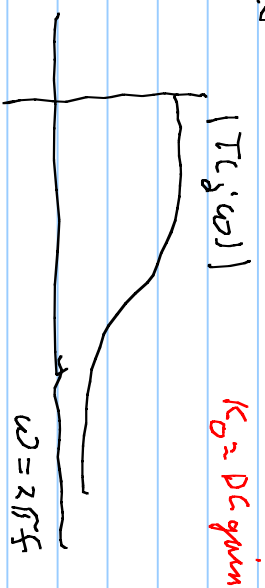
$$\frac{\omega_0}{Q} \Rightarrow Q = \frac{\omega_0 R}{(2+R/G_i)} \times R_1 C = \frac{R \sqrt{R_1}}{R_2 (2+R/G_i)}$$



$$\text{all-pass} = T(s) = \frac{s^2 - \omega_0^2}{s^2 + \omega_0^2} ; |T(j\omega)| = 1$$