



CMOS inverters p. 1089 fig 13.17


Kalsh p. 1205

BST transition frequency, p. 710 \Rightarrow low gain = 1

$$eq. 9.43 \quad f_T = \frac{g_m}{2\pi(C_D + C_G)}$$

CMOS inverters

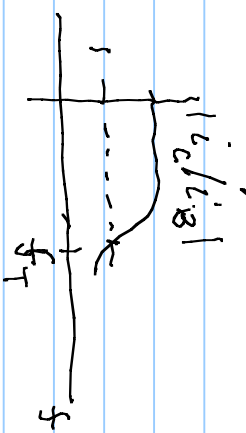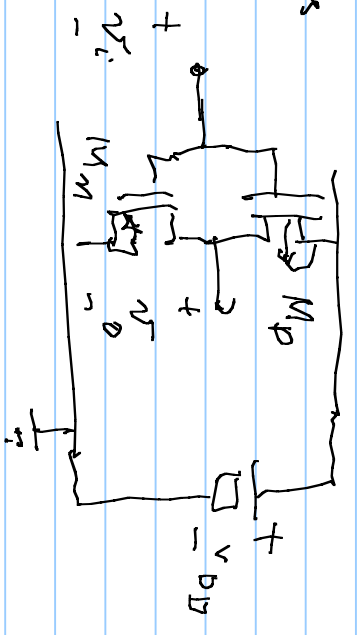


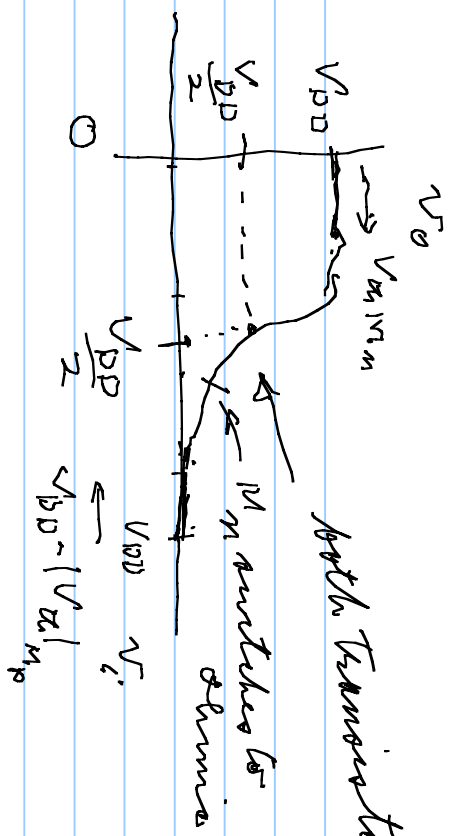

both Transistors in saturation

@ $v_i = 0$, $v_{GS,NM} = 0$

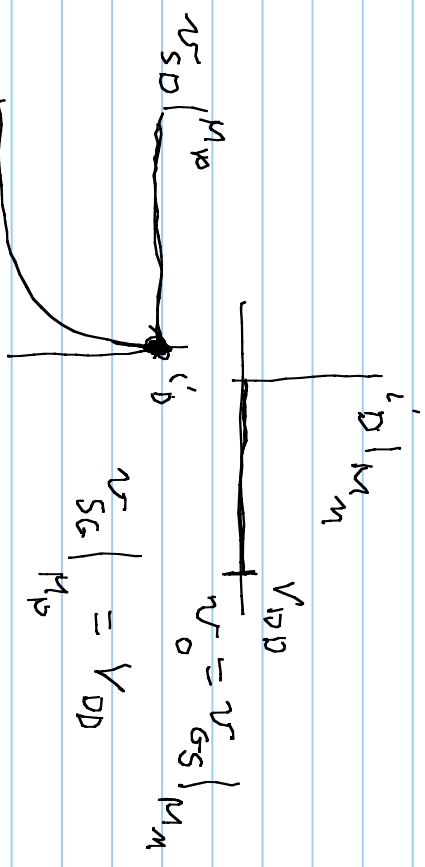when both in saturation, @ $v_i = v_o$
 $= V_{DD}/2$




$i_{D,N} = -i_{D,P}$ if $|v_{GS}|$ turns transistor bulk diodes off
 (does in standard connection)

$$i_{D_M} = \frac{K_{D_M}}{2} \left(\frac{W}{L} \right)_M \left(\frac{V_{DD}}{2} - V_{T0_M} \right)^2 \left(1 + \lambda_n \frac{V_{DD}}{2} \right)$$




$$\approx \frac{K_{D_P}}{2} \left(\frac{W}{L} \right)_P \left(\frac{V_{DD}}{2} - |V_{T0_P}| \right)^2 \left(1 + \lambda_p \frac{V_{DD}}{2} \right)$$

allows choice of $(W/L)_P$ for fixed everything else.

Ring oscillators

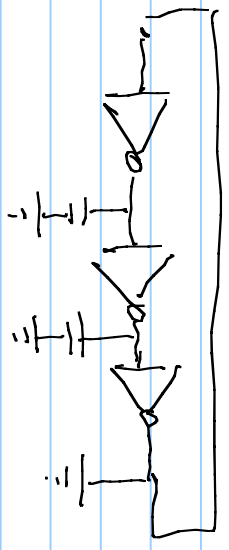

P. 1100, Fig 13.22 dischargeing

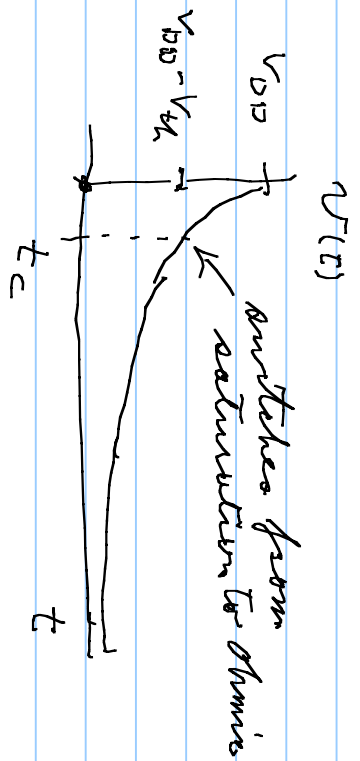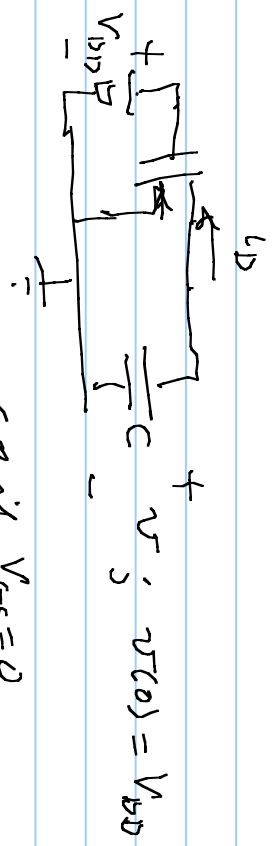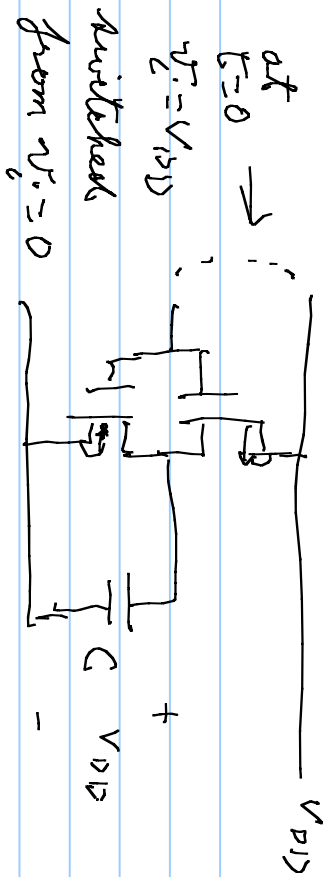

$$-C \frac{dv_o}{dt} = I_D(v_i, v_o) = \begin{cases} 0 & \text{if } v_{GS} = 0 \\ \text{saturation value if } v_i > V_{DD} - V_{th} \\ \text{ohmic value if } v_i < V_{DD} - V_{th} \end{cases}$$

ignores linear DDE


Agner's Lemma

for $0 \leq t \leq t_{change} = t_c \Rightarrow$ time for switch from saturation

$$\rightarrow C \frac{dv}{dt} = k (V_{DD} - V_{T0})^2 \quad ; \quad v(0) = V_{DD}$$

$$v = -\frac{k}{C} \int_0^t (V_{DD} - V_{T0})^2 dt + v(0)$$
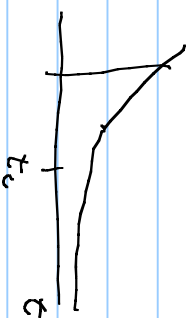
$$= V_{DD} - \frac{k}{C} (V_{DD} - V_{T0})^2 \cdot t$$



$$-t_c = \frac{(V_{DD} - V_{T0}) - V_{DD}}{\frac{k}{C} (V_{DD} - V_{T0})^2} = -\frac{V_{T0} \times C}{k (V_{DD} - V_{T0})^2}$$

then arrives to

$$-C \frac{dv}{dt} = k [2(V_{DD} - V_{T0})v - v^2] \quad ; \quad v(t_c) = V_{DD} - V_{T0}, \quad t_c < t < \infty$$

$$\frac{dv}{dt} = \frac{k}{C} v^2 + \frac{2k}{C} (V_{DD} - V_{T0})v = 0 \quad \text{a Riccati equation}$$

$$\frac{dx}{v^2 - 2(V_{p0} - V_T) v} = \frac{R_0 dt}{C} \Rightarrow \int_{v(t_0)}^{v(t)} \frac{dx}{x - 2(V_{p0} - V_T)} = \int_{t_0}^t \frac{R_0}{C} dx$$

partial fraction expansion of , $a = 2(V_{p0} - V_T)$

$$\frac{1}{x(x-a)} = \frac{R_0}{x} + \frac{R_1}{x-a} = \frac{-1/a}{x} + \frac{1/a}{x-a}$$

$$R_0 = \frac{1}{x-a} \Big|_{x=0} = -1/a$$

$$R_1 = \frac{1}{x} \Big|_{x=a} = 1/a$$

$$\int_{v(t_0)}^{v(t)} \left[\frac{-1/a}{x} dx + \frac{1/a}{x-a} dx \right] = -\frac{1}{a} \ln x \Big|_{v(t_0)}^{v(t)} + \frac{1}{a} \ln(x-a) \Big|_{v(t_0)}^{v(t)}$$

$$= \frac{1}{a} \left[-\ln v(t) + \ln v(t_0) + \ln(v(t)-a) - \ln(v(t_0)-a) \right]$$

$$= \frac{1}{a} \left[\ln(v(t)/v(t_0)) + \ln\left(\frac{v(t)-a}{v(t_0)-a}\right) \right]$$

$$= \frac{1}{a} \lim_{\epsilon \rightarrow 0} \left[\frac{v(t_0 + \epsilon) \times (v(t) - a)}{v(t) \times (v(t_0) - a)} \right] = \frac{K}{C} (t - t_0)$$

\Rightarrow take $e^{Kt} = x \Rightarrow$

$$\frac{v(t_0) \times (v(t) - a)}{v(t) \times (v(t_0) - a)} = e^{\frac{aK}{C} (t - t_0)}$$

$$\Rightarrow v(t_0) v(t) = a \cdot v(t_0) + v(t) [v(t_0) - a] e^{\frac{aK}{C} (t - t_0)}$$

$$v(t) = \frac{a v(t_0)}{(v(t_0) - [v(t_0) - a] e^{\frac{aK}{C} (t - t_0)})}, \quad t_0 \leq t, \quad v(t_0) = v(t_0)$$

denominator to 0 as $t \rightarrow \infty$ somewhat like e^{-aKt} .

