

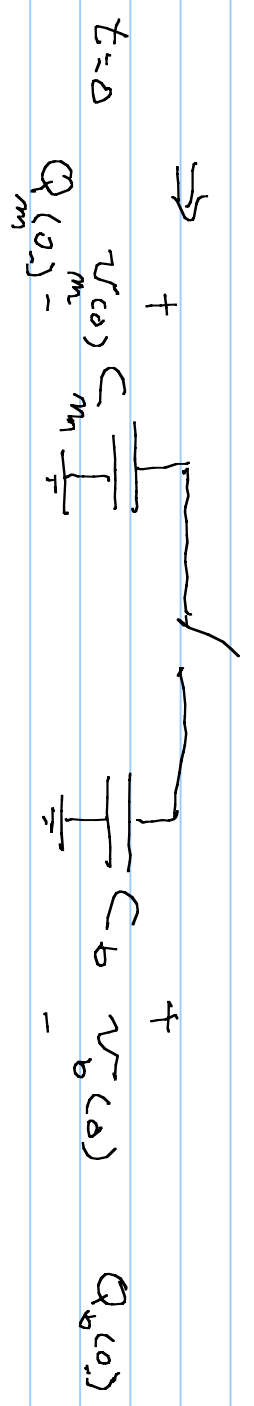


# Dynamic RAM R1K1 R0.1225

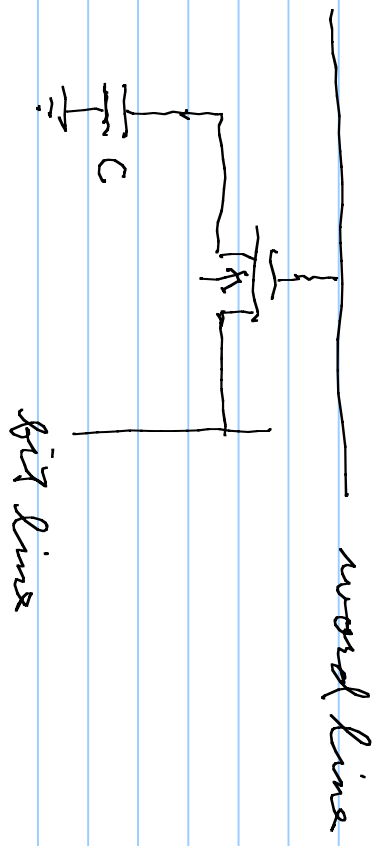

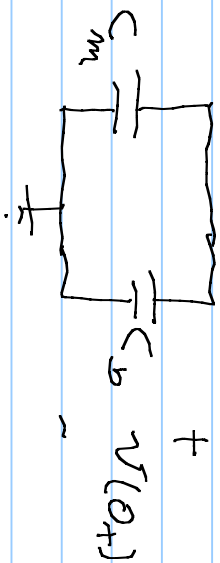

$$Q_{(0+)} \approx Q_{(0-)} + Q_b(0-)$$

$$C = C_m + C_b$$

$$(C_m + C_b) \mathcal{V}(0+) \approx Q_m(0-) + Q_b(0-) = C_m \mathcal{V}_m(0-) + C_b \mathcal{V}_b(0-)$$

if  $C_m$  stores a 1 then  $\mathcal{V}_m(0-) = V_{DD}$  &  $\mathcal{V}_b(0-) = \frac{V_{DD}}{2}$  by precharge

$$(C_m + C_b) \mathcal{V}(0+) \approx C_m \cdot V_{DD} + C_b \frac{V_{DD}}{2} \Rightarrow \mathcal{V}(0+) = \frac{(C_m + C_b/2) \cdot V_{DD}}{(C_m + C_b)}$$


$$\approx \frac{2C_m + C_b}{C_m + C_b} \cdot \frac{V_{DD}}{2}$$

will have  $V_{DD}/2 + \Delta, V_{DD} = \mathcal{V}(0+)$


if  $C_m$  stores a zero then  $\mathcal{N}(0+) = \frac{0 \cdot C_m + C_b}{C_m + C_b} \frac{V_{DD}}{2}$

will have  $\frac{V_{DD}}{2} \rightarrow \Delta_0 V_{DD} = \mathcal{N}(0+)$

Hysteresis


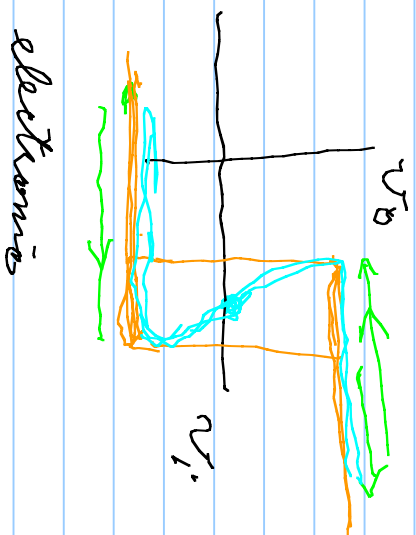


electronic

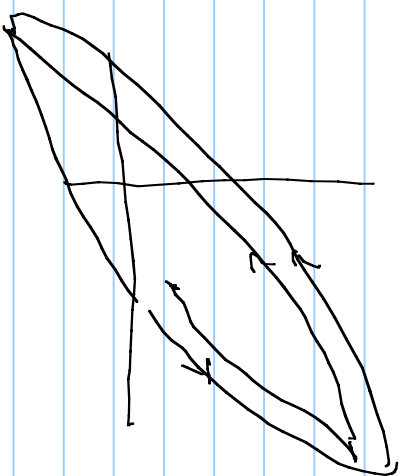


magnetic

How to make

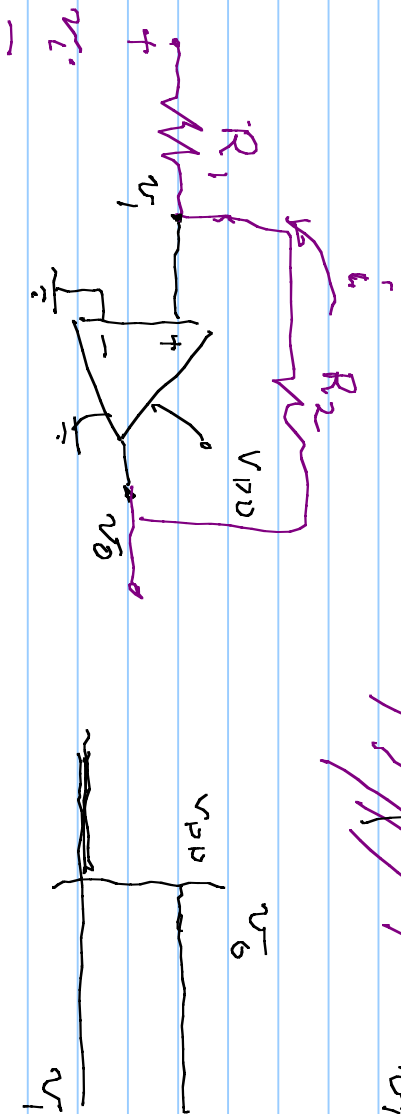
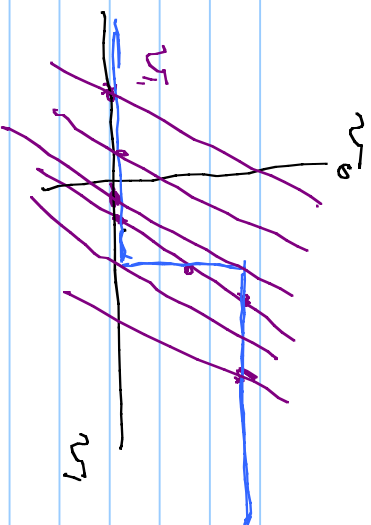


$$v_o = R_2 i + v_i, \quad v_i - v_i = R_1 i \Rightarrow i = G_1 (v_i - v_i)$$
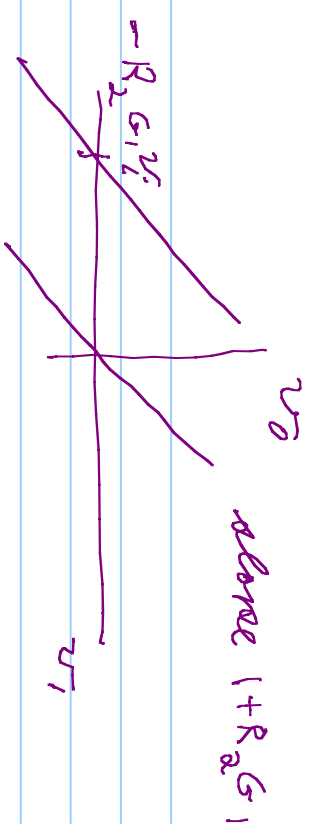
$$v_o = R_2 G_1 v_i + (1 + R_2 G_1) v_i - R_2 G_1 v_i$$



→ more right if decreases  $v_i$

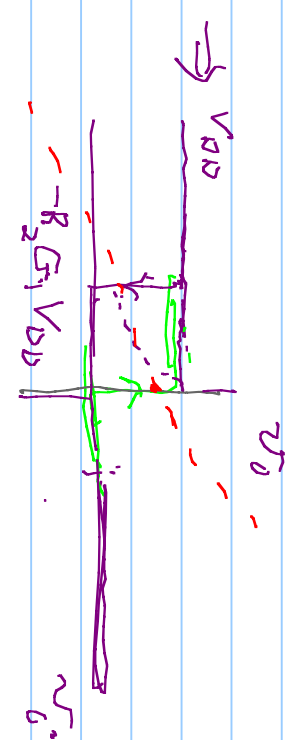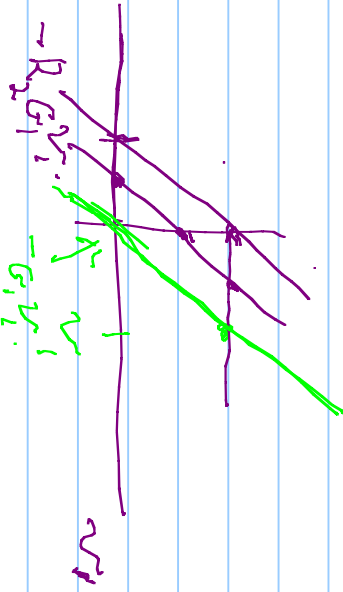

find  $v_i$ : such that  $v_o = V_{DD}$  @  $v_i = 0 \Rightarrow V_{DD} = -R_2 G_1 v_i \Rightarrow v_i = -\frac{V_{DD}}{R_2 G_1}$

