

EE 303H

11/06/14

Note Title

11/6/2014

van der Pol

$$\frac{d^2 x}{dt^2} + \nu(x^2 - 1) \frac{dx}{dt} + \omega_0^2 x = 0 \quad x(0), \dot{x}(0)$$

$$\nu \gg 0$$

$$f(x) = \frac{\nu}{3} x^3 - \nu x$$

$$\frac{df(x)}{dx} = \nu(x^2 - 1) \frac{dx}{dx}$$


$$\frac{d(y)}{dt} + \omega_0^2 x = 0, \quad y = \frac{dx}{dt} + f(x)$$

$$\frac{dx}{dt} = y - f(x), \quad \frac{dy}{dt} = -\omega_0^2 x \quad \text{state variables eqs.}$$

plot in  $y$  vs  $x$  for the reduction

$$\frac{dy}{dx} = \frac{dx/dt}{y - f(x)} = \frac{-\omega_0^2 x}{y - f(x)}$$

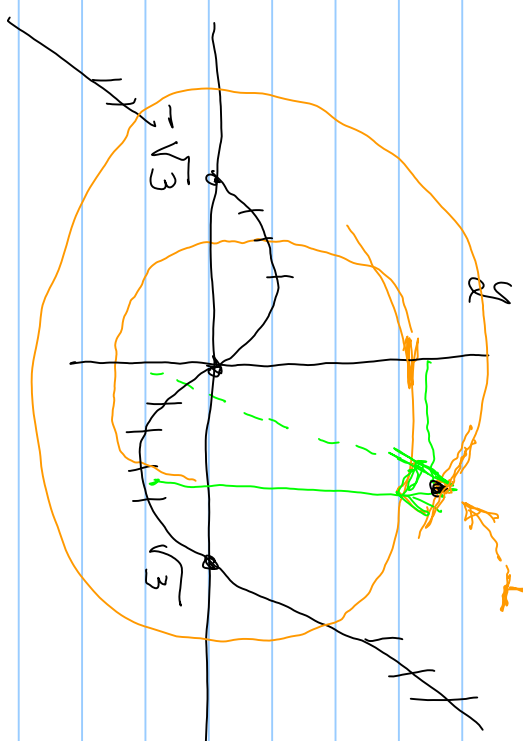
$$y = f(x) = \frac{\mu}{3}(x^3 - 3x) = \frac{\mu}{3}x(x^2 - 3)$$



← goes to a limit cycle

$x$  if normalizing  $\omega_0 = 1$

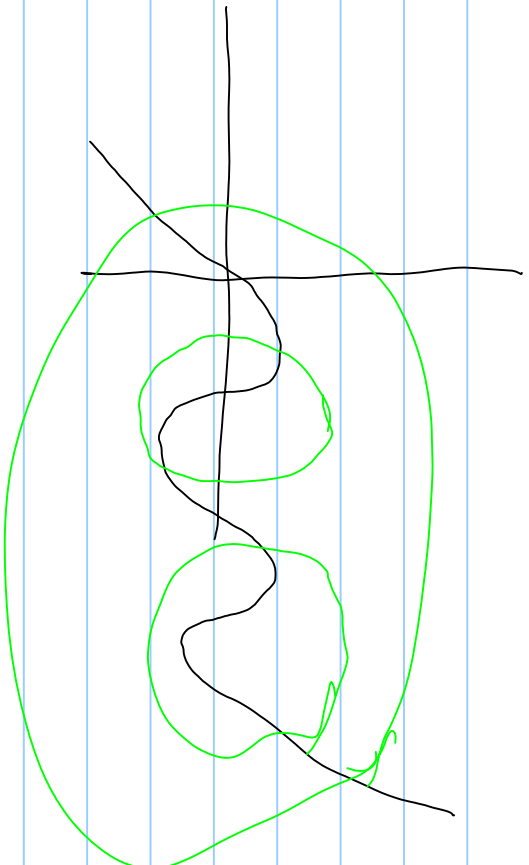for multiple limit cycles are an  $f(x)$   
with two negative slopes




Synthesis of passive circuits

$$E(t) \geq 0 \text{ for all } t$$

Energy into circuit  $E(t) = \int_{-\infty}^t p(\tau) d\tau$
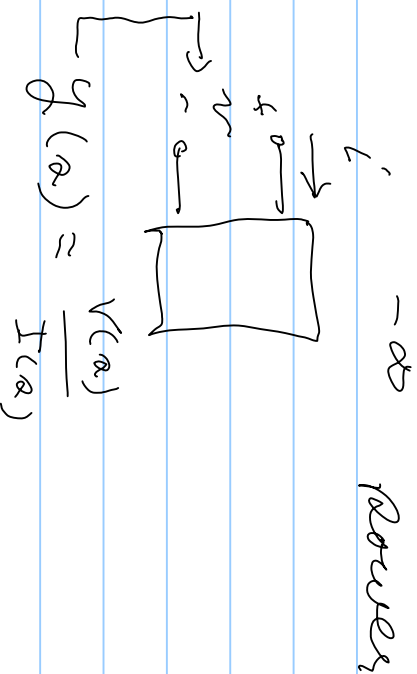
$$E(t) = \int_{-\infty}^t v(\tau) i(\tau) d\tau$$



$$V(a) = \int_{-\infty}^{\infty} v(t) e^{-at} dt = \text{Laplace transform}$$

$q(a)$  will come from a passive circuit if it is positive real; can synthesize

if  $g(a)$  is rational & positive real  $\Rightarrow$  PR

$f(a)$  by definition is positive real  
if and only if

1.  $f(a)$  is if  $R$  is real &  $\text{Re } R = \sigma > 0$   
(a real number)
2.  $f(a)$  is analytic in  $\sigma > 0$  (stable)
3.  $\text{Re } g(a) \geq 0$  in  $\sigma > 0$

Ex:  $\int_R ; g(a) = 1/R \Rightarrow$  PR if  $R > 0$

$\int_C ; g(a) = c ; \text{Re } g(a) = c(\sigma + j\omega) = c\sigma$  real  
if  $c$  is real

$$\mathcal{I} \left( \frac{1}{s^2 + 2s + 1} \right) = \frac{1}{s^2 + 2s + 1} = \frac{1}{(s+1)^2} = \frac{1}{s+1} - \frac{1}{(s+1)^2}$$

$\Rightarrow$  Real poles at  $s = -1/LC$


$$s = \pm j/\sqrt{LC}$$

if  $k > 0$  is stable

Re  $g(s)$  in  $R = \sigma + j\omega$ ,  $\sigma > 0$

$$g(s) = \frac{(s+j\omega)C}{1 + LC(\sigma^2 + 2j\omega\sigma - \omega^2)}$$
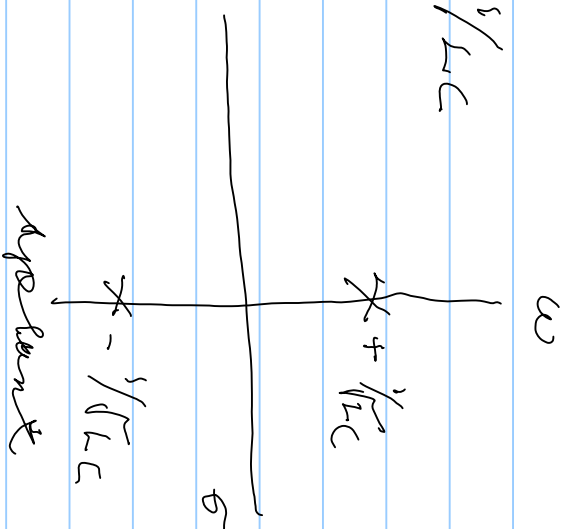
$$= \frac{(s+j\omega)C(1 + LC\sigma^2 - LC\omega^2 - 2j\omega LC\sigma)}{[1 + LC\sigma^2 - LC\omega^2 + 2j\omega LC\sigma][1 + LC\sigma^2 - LC\omega^2 - 2j\omega LC\sigma]}$$



$$\operatorname{Re} y(\alpha) \times D(\alpha) D(\alpha^*) = \sigma \left[ 1 + LC\sigma^2 - LC\omega^2 \right] + 2\omega^2 LC\sigma$$

$$\Rightarrow \sigma \text{ in } \sigma > 0$$

$$\Rightarrow y(\alpha) = \frac{C\alpha}{LC\alpha^2 + 1} \quad \text{is PR}$$

How to make a minimum

lowpass  $\Rightarrow$  Pass (jw) = 0

complex

$$V(\alpha) I(\alpha) + V(\alpha) I(\alpha^*) = 2 \operatorname{Pass}(j\omega) = 0$$

$$\alpha = j\omega \quad \alpha = j\omega$$


$$V^*(\alpha) y(\alpha) + V(\alpha^*) y(\alpha^*) = V^* [y(\alpha) + y(\alpha^*)] V = 0$$

$$\Rightarrow V^* [y(\alpha) + y(\alpha^*)] \Big|_{\alpha=j\omega} V = 0 \quad \text{for all } V$$

$$\alpha = j\omega \quad \text{for all } V$$

$$\Rightarrow y(\alpha) + y(\alpha^*) = 0 \quad \text{for } \alpha = j\omega \leftarrow \text{Lowpass}$$

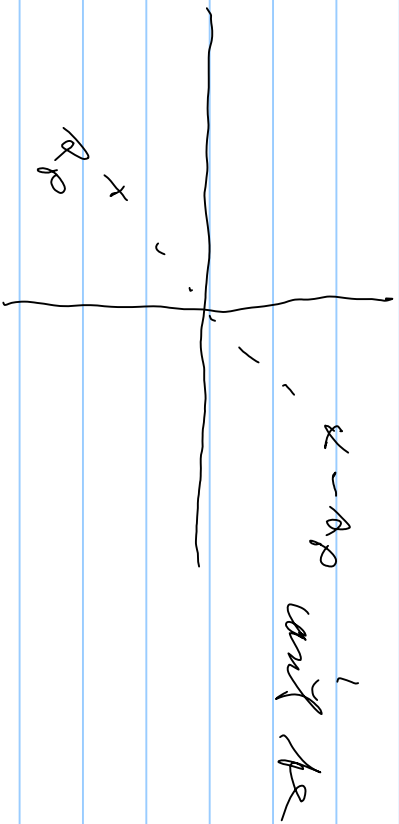holds for all  $\alpha = \sigma + j\omega \Rightarrow g(\alpha) = -g(-\alpha)$  for a  
lossless PR function



all poles are on  $j\omega$   
axis



$$T(A) = \frac{N(A)}{D(A)} = \frac{a_m A^m + \dots + a_1 A + a_0}{A^d + b_{d-1} A^{d-1} + \dots + b_0}$$

$a_i, b_j$  real

$A = \sigma + j\omega$

$$A^k = (j\omega)^k = j^k \omega^k = \begin{cases} (-1)^{k/2} \omega^k & k \text{ even} \\ j(-1)^{(k-1)/2} \omega^k & k \text{ odd} \end{cases}$$

$A = j\omega$

$e^{j\omega t}$  if  $A = j\omega$ ,  $e = \cos \omega t + j \sin \omega t$

$$T(A) = \frac{N(A) D(-A)}{D(A) D(-A)} = \text{Ev} T(A) + \text{Od} T(A)$$

$a \rightarrow -a$        $n \rightarrow n$

$$T(j\omega) = \text{Ev} T(j\omega) + \text{Od} T(j\omega) = R(\omega) + jX(\omega)$$