

610 Fall 2014 – Homework 6 Due Th 10/16/14

1. (60 points, maximally flat transfer functions)  
Consider again the degree 4 low pass maximally flat transfer function,  $T(s)$ , normalized so that the gain is 1 at dc and the lead denominator coefficient is also 1
  - a) Factor  $T(s)$  into two degree two transfer functions. Give the  $Q$ 's and  $\omega_o$ 's of the two sections.
  - b) Denormalize so that the normalized  $\omega=1$  becomes  $\omega=2\pi 10^4$ . Use the TI UAF42 to realize the resulting LP  $V_o(s)/V_i(s)$  transfer function. Submit the Spice circuit with element values and an AC magnitude run using AD741 op-amps (in the OPAMP library of PSpice)..
  
2. (40 points, PR property)  
For the degree 2 rational input admittance
$$y(s) = [s^2 + as + 1]/[s^2 + 2s + b]$$
  - a) Determine for which values of the real constants  $a$  and  $b$  this admittance is PR. Is there a relationship between  $a$  and  $b$ ?
  - b) For each PR  $y(s)$  give the zeros and poles. Can any be on the  $j\omega$  axis?