
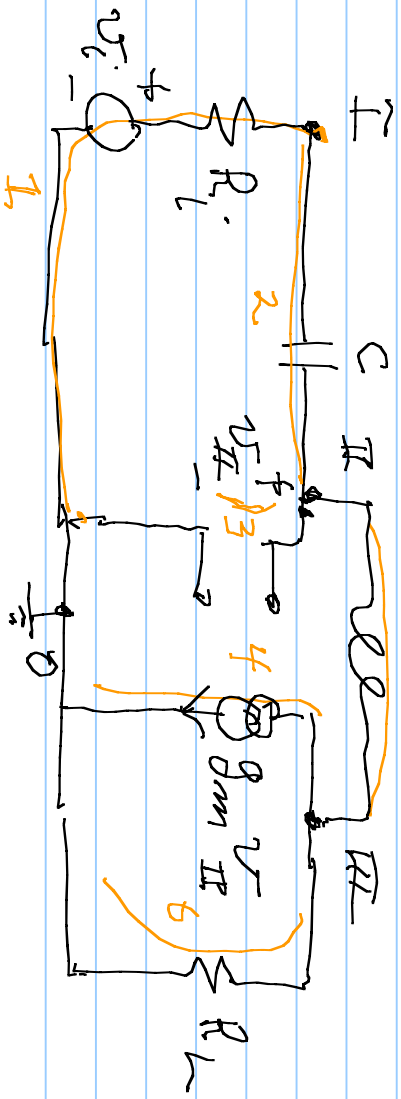


Mesh Theory for KCL, KVL

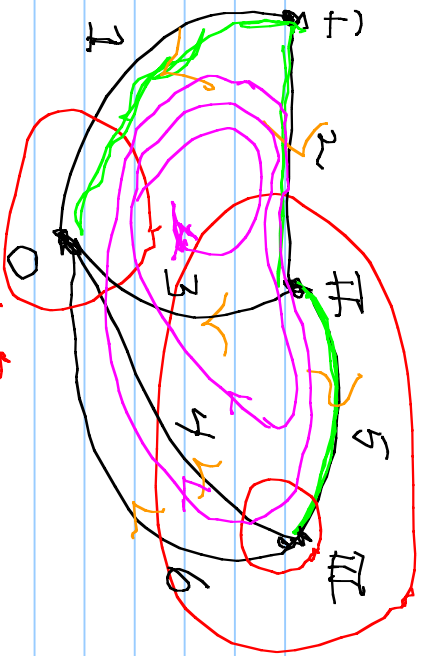



2nd cut set = b_2, b_3, b_4, b_6

$m = \# \text{ of nodes} = 4$

$b = \# \text{ of branches} = 6$


$t = \# \text{ of tree branches} = 3$

$l = \# \text{ of links} = 3$

$$T = m - 1 \quad A = \# \text{ dependent paths}$$

$$L = b - t = 1 \quad (T = m - a)$$

cut set = b_1, b_3, b_4, b_6

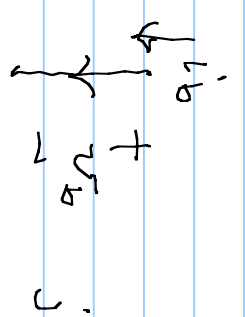

Power into branch = $v_b i_b \Rightarrow v_b^T i_b = \text{total power into the circuit}$
 $V = \text{transpose}$

$$\Rightarrow i_p \quad p_2 \quad p_3 \quad p_4 \quad p_5 \quad p_6$$

$$i_b = [i_{b1}, i_{b2}, i_{b3}, i_{b4}, i_{b5}, i_{b6}]$$

KCL: Σ currents into a closed sphere = 0
 do for each tree branch \Rightarrow 3 KCL's

$$0 = i_{b_1} + i_{b_3} + i_{b_4} + i_{b_6}$$

$$0 = i_{b_2} - i_{b_3} - i_{b_4} - i_{b_6}$$

$$0 = -i_4 + i_{b_5} - i_{b_6}$$

$$= \begin{bmatrix} 0 \\ 0 \\ 0 \end{bmatrix} \geq \begin{bmatrix} 1 & 0 & 1 & 1 & 0 & 1 \\ 0 & 1 & -1 & -1 & 0 & -1 \\ 0 & 0 & 0 & -1 & 1 & -1 \end{bmatrix}$$

$$\begin{bmatrix} i_{b_1} \\ i_{b_2} \\ i_{b_3} \\ i_{b_4} \\ i_{b_5} \\ i_{b_6} \end{bmatrix}$$

$\Rightarrow \underline{0} = \underline{C} \cdot \underline{i_b}$ } \underline{C} = cut set matrix
 } independent as 1 per tree branch

KVL: Σ voltages around a closed path = 0
 do one for each link

$$\begin{aligned}
 b_3 \cdot 0 &= -v_6 + v_2 + v_3 \\
 b_4 \cdot 0 &= -v_6 + v_2 + v_4 + v_5 \\
 b_6 \cdot 0 &= -v_4 + v_2 + v_5 + v_6
 \end{aligned}
 = \begin{bmatrix} 0 \\ 0 \\ 0 \end{bmatrix} = \underbrace{\begin{bmatrix} -1 & 1 & 1 & 0 & 0 & 0 \\ -1 & 1 & 0 & 1 & 1 & 0 \\ -1 & 1 & 0 & 0 & 1 & 1 \end{bmatrix}}_{Q} v_5$$

have 3 independent equations

$$Q = Q^{-1} v_5$$

Q^{-1} is the adj matrix

if number trees first can get equations

$$Q = \begin{bmatrix} 1 & 1 & 1 \\ 1 & 1 & 0 \\ 1 & 1 & 0 \end{bmatrix} \Rightarrow 1_T = \begin{bmatrix} 1 & 0 & 0 \\ 0 & 1 & 0 \\ 0 & 0 & 1 \end{bmatrix} \text{ for } T=3$$

$$\Rightarrow -1_T = K' L_Q$$

is for links $Q_x = \begin{bmatrix} K_{x1} & 1 \\ 1 & K_{x2} \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix} \Rightarrow -v_x = K_{x1} v_1$

$$\begin{bmatrix} v_t^T \\ v_R^T \end{bmatrix} = v_b = \begin{bmatrix} 1_t \\ -K_{v^T} \end{bmatrix} \cdot \begin{bmatrix} v_t^T \\ v_R^T \end{bmatrix} = \begin{bmatrix} 1_t \\ -K_{v^T} \end{bmatrix} \cdot \begin{bmatrix} 1_R \\ 1_R \end{bmatrix}$$

or $P_{in} \equiv 0$ if a finite graph for a circuit then

$$v_b^T \cdot v_b = \sum_{k=1}^R v_b^T \cdot v_b = 0 \Rightarrow v_t^T \underbrace{\begin{bmatrix} 1_t \\ -K_{v^T} \end{bmatrix}}_{v_b^T} \cdot \begin{bmatrix} 1_R \\ 1_R \end{bmatrix} v_R$$

$$\Rightarrow v_t^T \underbrace{\begin{bmatrix} -K_{v^T} & -K_{v^T} \end{bmatrix}}_{t \times R} v_R = 0_{1 \times 1}$$

or $v_t^T v_R$ can be for any circuit with this graph then this means $-K_{v^T} - K_{v^T}^T = 0_{t \times R}$

$$\Rightarrow K_{L'} = -K_{R'}^T$$

$$\Rightarrow C = [1_{L'}, K_{L'}] \cdot C^T =$$

$$\begin{bmatrix} 1_{L'} \\ -K_{R'} \end{bmatrix} = \begin{bmatrix} 1_{L'} \\ K_{L'}^T \end{bmatrix}$$

$$C^T = [K_{R'}, 1_{R'}]$$

$$C^T = \begin{bmatrix} K_{R'}^T \\ 1_{R'} \end{bmatrix} = \begin{bmatrix} -K_{L'} \\ 1_{R'} \end{bmatrix}$$

$$u_b = \begin{bmatrix} 1_{L'} \\ -K_{R'} \end{bmatrix} u_f = \begin{bmatrix} 1_{L'} \\ K_{L'}^T \end{bmatrix} u_f$$

$$\Rightarrow u_b \approx C^T u_f \quad (KVL)$$

$$\Rightarrow u_b' \approx C^T u_r' \quad (KCL)$$

need source of branches

$$\begin{aligned}
 Y_{b1} &\equiv \sum_{i=1}^n R_{ci} \\
 Y_{b2} &\equiv \frac{1}{C} \\
 Y_{b3} &= Y_{b4} = 0 \\
 Y_{b5} &= 0 \\
 Y_{b6} &\equiv \sum_{i=1}^n R_{ci}
 \end{aligned}$$

max admittance \Rightarrow Y_{b5} do have an open circuit branch on VCSS