

Assume: $\text{Re } y(s) = 0 \Rightarrow \text{Im } z(s) = 0 =$

$$2\text{Re}(z(s)) = z(s) + z(-s) = \frac{1}{y(s)} + \frac{1}{y(-s)}$$

write if PR \downarrow
 $= \frac{y(-s) + y(s)}{y(s)y(-s)} = 0$


$$y(s) = \frac{k_0}{s} + k_{\infty} s + \sum_{l=1}^N \frac{2k_l s}{s^2 + \omega_l^2}, \quad k_l \geq 0$$

$y(s)/s = B(s)$


$$y(s) = -j \frac{k_0}{\omega} + j k_{\infty} \omega + \sum_{l=1}^N \frac{2k_l j \omega}{-\omega^2 + \omega_l^2}$$

$$\frac{\partial y(s)/s}{\partial \omega} = -\frac{k_0(-1)}{\omega^2} + k_{\infty} + 2 \sum_{l=1}^N \frac{k_l}{(-\omega^2 + \omega_l^2)^2} + \frac{(-2\omega) k_l(s) \omega}{(-\omega^2 + \omega_l^2)^2}$$
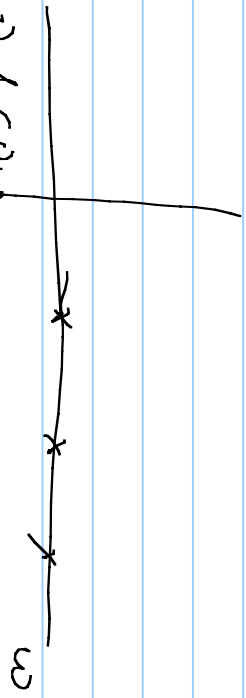
$$= \frac{k_0}{\omega^2} + k_{\infty} + 2 \sum_{l=1}^N k_l \frac{[-\omega^2 + \omega_l^2 + 2\omega^2]}{(-\omega^2 + \omega_l^2)^2} \geq 0$$



$B(u)$

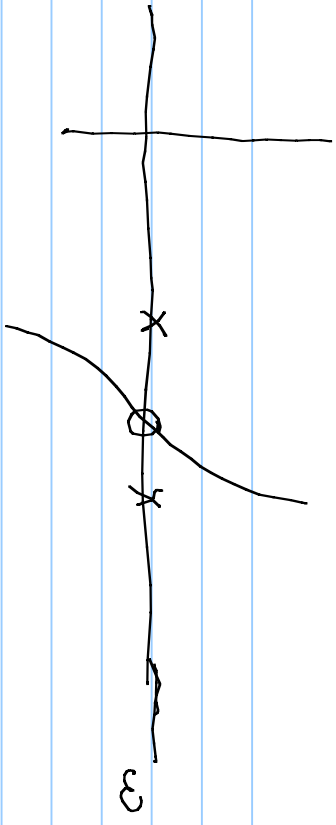


\Rightarrow a zero between poles

\therefore poles of $z(a)$ are zeros of $y(a)$ between poles of $y(a)$

Ex: $y(a) = -y(-a)$ for lossless PR & poles & zeros alternate
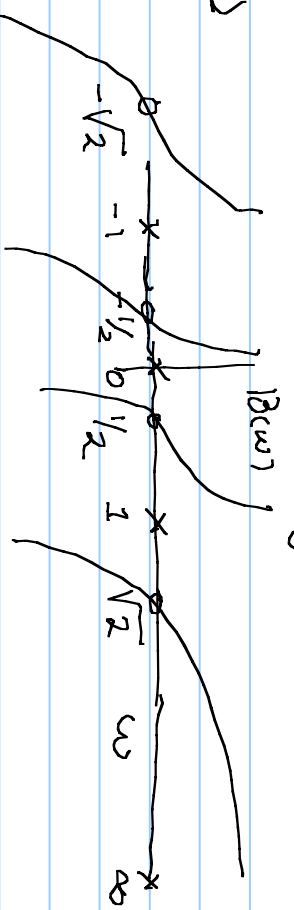
$$= \frac{(a^2 + 1/4)(a^2 + 2)}{a(a^2 + 1)}$$



and $\tilde{y}(a) \Rightarrow$ partial fraction expansion of $y(a)$

$$y(s) = \frac{K_0}{s} + K_1 s + \frac{2K_1 s}{s^2+1} = \frac{(s^2+1/4)(s^2+2)}{s(s^2+1)}$$

$K_0 \rightarrow$ x R on both sides, cancel on right & set $s=0$ (kills K_0 & K_1)


$$K_0 = \frac{(s^2+1/4)(s^2+2)}{(s^2+1)} \Big|_{s=0} = \frac{1/4 \times 2}{1} = 1/2$$

terms

$$K_1 s = \frac{s^4}{s^3} \times \frac{1}{s} = 1$$

$$2K_1 = \frac{\cancel{s^3+1}}{s} \left[\frac{(s^2+1/4)(s^2+2)}{\cancel{s(s^2+1)}} \right] = \frac{(-1+1/4)(-1+2)}{-1} = \frac{-3/4 \times 1}{-1} = 3/4$$
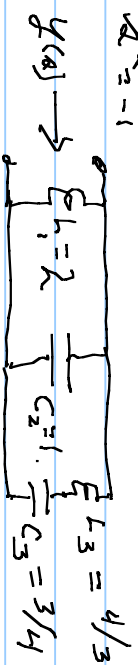
$$y(s) = \frac{1/2}{s} + 1 + \frac{3/4 s}{s^2+1}$$




$$y_3 = \frac{3/4 R}{R^2 + 1} \Rightarrow z = \frac{1}{y_3} = \frac{R^2 + 1}{3/4 R} = \frac{4}{3} R + \frac{1}{3/4 R}$$

let z total \Rightarrow partial fraction expansion of $z(s)$

$$z(s) = \frac{1}{y(s)} = \frac{1}{\underbrace{(R^2 + 1/4)(R^2 + 2)}} = \frac{R(R^2 + 1)}{(R^2 + 1/4)(R^2 + 2)} = \frac{2R_3 R}{R^2 + 1/4} + \frac{2R_4 R}{R^2 + 2}$$

$$2R_3 = \frac{R^2 + 1}{R^2 + 2} \Big|_{R^2 = -1/4} = \frac{3/4}{7/4} = 3/7 \quad ; \quad 2R_4 = \frac{R^2 + 1}{R^2 + 1/4} \Big|_{R^2 = -2} = \frac{-1}{-7/4} = 4/7$$

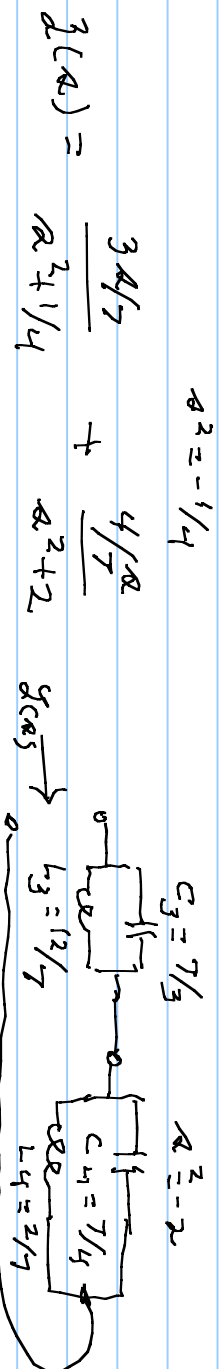

$$z(s) = \frac{3R/7}{R^2 + 1/4} + \frac{4R/7}{R^2 + 2}$$


$$y_3 = \frac{R^2 + 1/4}{\frac{3}{7}R} = \frac{7}{3}R + \frac{7}{12R} \quad y_4 = \frac{R^2 + 2}{4R} = \frac{7}{4}R + \frac{1}{2R}$$

1st Cases: Continued fractions expansion about ∞
 (That is, remove poles at ∞ of y_3)

y_3 has a pole @ ∞ ; divide highest power of R

$$y_3(s) = \frac{(R^2 + 1/4)(R^2 + 2)}{R(R^2 + 1)} \approx \frac{R^4 + \frac{9}{4}R^2 + 1/2}{R^3 + R}$$
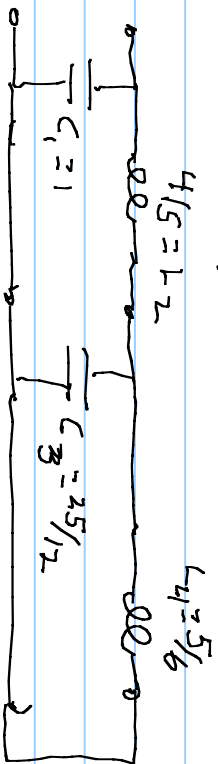
$$\begin{aligned} &= R + \frac{1}{R} \\ &\quad + \frac{4}{5}R + \frac{1}{12} \\ &\quad + \frac{25}{12}R + \frac{1}{5R} \end{aligned}$$



at $R = \infty$ an open } stop signals
 at $R = \infty$ getting through
 at $R = \infty$

$$\begin{array}{r}
 \frac{3}{a^3 + a} \left\{ \frac{a}{a^4 + \frac{a}{4}a^2 + \frac{1}{2}} \right. \\
 \left. \frac{a^4 + a^2}{5/4} \right\} \\
 \frac{a^3 + a}{5} \\
 \frac{a^3 + \frac{2}{5}a}{\frac{3}{5}a} \\
 \frac{a^3 + a}{\frac{5}{4}} \left\{ \frac{a^2 + \frac{1}{2}}{\frac{5}{4}} \right\} \\
 \frac{a^2 + \frac{1}{2}}{\frac{5}{4}} \\
 \frac{1}{2} \sqrt{\frac{3}{5}a}
 \end{array}$$


2nd case \Rightarrow continued fraction expansion about $a = 0$

$$y(s) = \frac{\frac{1}{2} + \frac{9}{4}s^2 + s^4}{s + s^3} = \frac{1}{2s} + \frac{1}{\frac{7}{4}s} + \frac{1}{\frac{12}{49}s} + \frac{1}{\frac{3}{7}s^3}$$

$$\frac{s + s^3}{\frac{1}{2} + \frac{9}{4}s^2 + s^4} = \frac{\frac{1}{2} + \frac{1}{2}s^2}{\frac{7}{4}s^2 + s^4} = \frac{\frac{1}{2} + \frac{1}{2}s^2}{\frac{7}{4}(s^2 + s^4)} = \frac{\frac{1}{2} + \frac{1}{2}s^2}{\frac{7}{4}(s^2 + s^4)}$$


$$= \frac{\frac{1}{2} + \frac{1}{2}s^2}{\frac{7}{4}(s^2 + s^4)} = \frac{\frac{1}{2} + \frac{1}{2}s^2}{\frac{7}{4}(s^2 + s^4)} = \frac{\frac{1}{2} + \frac{1}{2}s^2}{\frac{7}{4}(s^2 + s^4)}$$
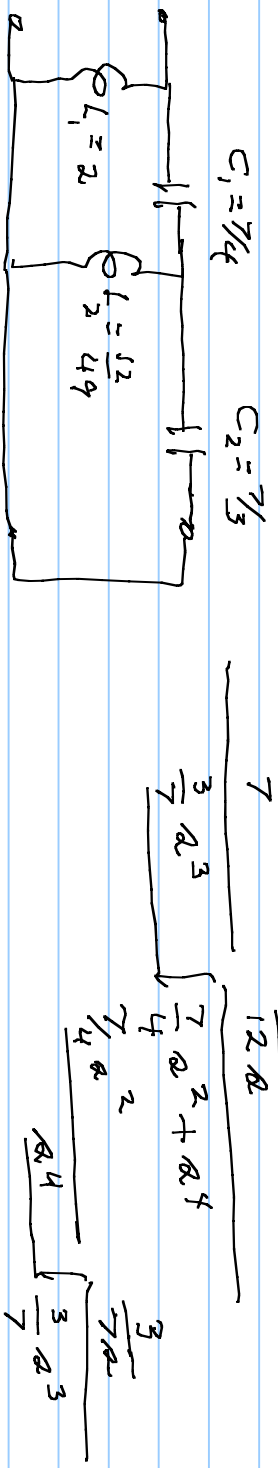
$$= \frac{\frac{1}{2} + \frac{1}{2}s^2}{\frac{7}{4}(s^2 + s^4)} = \frac{\frac{1}{2} + \frac{1}{2}s^2}{\frac{7}{4}(s^2 + s^4)}$$



useful for high pass
 open @ $s=0$ closed @ $s=0$

Use for v_2/v_1 synthesis

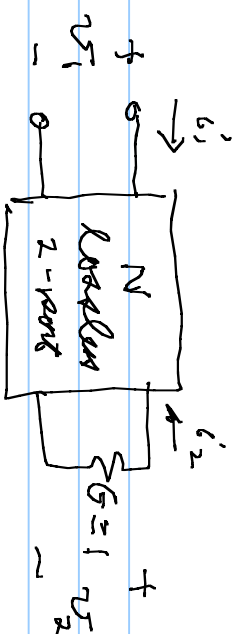

$$-v_2 = \begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix}$$

$$-v_2 = y_{21} v_1 + y_{22} v_2$$

$$\frac{v_2}{v_1} = \frac{-y_{21}}{1 + y_{22}} \Rightarrow \text{given } y_{21}(s) \text{ is constant, } y_{22} = \frac{N(s)}{D(s)} \text{ is odd}$$

y_{22} is even/odd or odd/even

$$= -k(\text{polynomial}) = -k(\text{odd or even})$$

polynomial Even + odd \Rightarrow should be Hurwitz

if numerator is odd divide out even & (vice versa)

$$\begin{aligned}
 Y_K: \frac{U'_2(a)}{U'_1} &= \frac{-K R^2}{R^4 + 2R^3 + 4R^2 + 2R + 2} = \frac{-K R^2 \frac{R^2}{R^3 + 2R}}{1 + \frac{R^4 + 4R^2 + 2}{R^3 + 2R}} = \frac{-Y_{21}}{1 + Y_{22}}
 \end{aligned}$$

$$Y_{22} = \frac{R^4 + 4R^2 + 2}{R^3 + 2R} \quad \text{symmetrisieren, um } Y_{21} = -K \frac{R^2}{R^3 + 2R}$$