

#1. a) $V_{GS} = V_{DD} - V_D \geq V_{GS} + V_i - V_D - V_{T0} \Rightarrow V_{DD} \geq 2V_{GS} - V_{T0} = 6 - 1 = 5 \Rightarrow V_{DDmin} = 5V$


b) $V_{GS} = V_{GS} - R i_D = 3 - 1 \times 10^3 \times 1 \times 10^{-3} = 3 - 1 = 2V$, $i_D = 10^{-3} = k (V_{GS} - V_{T0})^2 = k(2-1)^2 = k \Rightarrow k = 10^{-3}$

c) $i_D = k (V_{GS} - V_{T0})^2 = \frac{1}{R} v_D + C \frac{dv_D}{dt}$ with $v_{GS} = V_i + V_{GS} - v_D = 4 - v_D$ for $t > 0$
 $\Rightarrow 10^{-3} (3 - v_D)^2 = 10^{-3} v_D + 10^{-6} \dot{v}_D \Rightarrow 10^3 (9 - 6v_D + v_D^2) = 10^3 v_D + \dot{v}_D \Rightarrow 9 \times 10^3 = 7 \times 10^3 + 10^3 v_D^2 + \dot{v}_D$
 for $t < 0$, $v_D = R i_D = 1V$

#2. a) as the transistors are complementary $g_{m_n} = g_{m_p}$ & $g_{o_n} = g_{o_p}$

@ $v_i = V_{DD}/2$ both transistors are in saturation $[V_{GS_n} - V_{T0} = V_{DD}/2 - V_{T0} < V_{DD} = V_{DD}/2]$

so $i_{D_n} = k (V_{GS_n} - V_{T0})^2 (1 + \lambda V_{DS_n}) \Rightarrow g_{m_n} = 2k (V_{GS_n} - V_{T0}) (1 + \lambda V_{DS_n}) \Big|_Q = 2k (V_{DD}/2 - V_{T0}) (1 + \lambda V_{DD}/2)$
 $= \frac{2I_{Dn}}{(V_{DD}/2 - V_{T0})}$
 $g_{o_n} = \lambda [k (V_{GS_n} - V_{T0})^2] \Big|_Q = \lambda k (V_{DD}/2 - V_{T0})^2 = \frac{\lambda I_{Dn}}{(1 + \lambda V_{DD}/2)}$

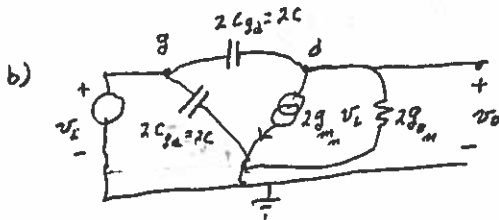

c) KCL @ d: $2C_{gd} \cdot \dot{v}_i (s) - V_o(s) = 2g_{m_n} V_i(s) + 2g_{o_n} V_o(s)$
 $\Rightarrow (2C_{gd} - 2g_{o_n}) V_i = (2C_{gd} + 2g_{o_n}) V_o \Rightarrow \frac{V_o(s)}{V_i(s)} = \frac{C_{gd} - g_{o_n}}{C_{gd} + g_{o_n}}$ zero: $\omega_z = g_{o_n}/C$ pole: $\omega_p = -g_{o_n}/C$

#3. a) $I_{R_1} = \frac{1}{R_1} [V_{CC} - V_{EB_{Q1}}] \Rightarrow R_1 = \frac{V_{CC} - V_{EB_{Q1}}}{I_{R_1}} = \frac{5 - 0.7}{10^{-3}} = 4.3 \times 10^3 \Omega = R_1$

b) $I_{out_{Q2}} = -I_{C_{Q2}} = \alpha I_{E_{Q2}} = \alpha I_{E_{Q1}}$, but $I_{R_1} = -I_{C_{Q1}} - 2I_{B_{Q1}} = -(I_{C_{Q1}})(1 + \frac{2}{\beta}) = \alpha I_{E_{Q1}} (1 + \frac{2}{\beta})$
 $= I_{out_{Q2}} = \frac{\beta}{1+\beta} I_{E_{Q1}} = \frac{\beta}{1+\beta} \cdot \frac{1+\beta}{2+\beta} I_{R_1} = \frac{\beta}{\beta+2} I_{R_1} = \frac{100}{102} \times 10^{-3} = I_{out_{Q2}} = 0.98 \text{ milliA}$

c) $v_o(t)|_{t=0} = 0$, as v_o cannot jump $v_o(0+) = 0$ and rises to $v_o(\infty) = R I_{out_{Q2}}$ with RC time const.

$I_{out_{Q2}} = C \frac{dv_o}{dt} + \frac{1}{R} v_o \Rightarrow \frac{dv_o}{dt} + \frac{1}{RC} v_o = \frac{0.98 \times 10^{-3}}{C}$ } $v_o(\infty) = 0$

$\Rightarrow v_o = 0.98 \times 10^{-3} R (1 - e^{-t/RC})$ for $t > 0$ & $v_o(t) = 0$ for $t < 0$

