

Open book open notes but not open computers; 100 points total (75 minutes); if stuck go on to the next problem. Good luck

1. (35 points, 20 min)

Assume an organic Thin Film Transistor (=TFT) is characterized by

$$i_D = \begin{cases} 0 & \text{for } v_{GS} \leq V_{th} \\ k(v_{GS} - V_{th})^2 (1 - e^{-v_{DS}/V_o}) & \text{for } V_{th} \leq v_{GS} \end{cases}$$

where k , V_o , and V_{th} are positive material constants.

- Give an expression for g_m at a bias point I_D , V_{GS} , V_{DS} simplified as much as possible in terms of I_D and the overdrive voltage $V_{OV} = V_{GS} - V_{th}$.
- For $V_{th} = 3V$, $V_o = 60V$, $I_D = 10\mu A$, $V_{GS} = 23V$ and $V_{DS} = 120V$ determine k and give its units.


2. (35 points, 20 min)

Attached are (expanded) curves for the ALD1101 NMOS transistor for which the data sheet also gives $V_{TO} = 0.7V$ and the output conductance g_o as $200\mu Mho$ at $I_D = 10mA$.

- Give the range of output resistance available for $0 \leq V_{GS} \leq 12V$ over $0 \leq V_{DS} \leq 160mV$ (using the low voltage output characteristics).
- Design a current sinking current source giving $I_{source} = 80mA$ using two ALD1101s, a resistor and a 9V power supply ($V_{DD} = 9V$, $V_{SS} = 0$).
- What is the lowest voltage on the drain of the output transistor needed to maintain 80mA (ignore g_o)

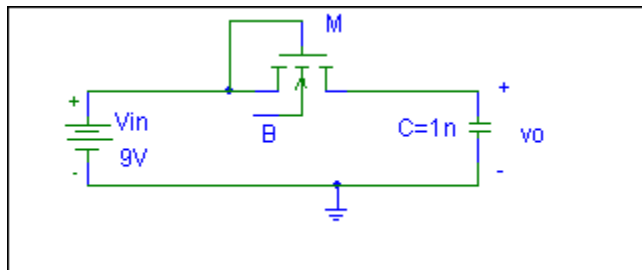3. (30 points, 20 minutes)

For the following circuit assume the capacitor is uncharged at $t=0$. Assume the transistor has the Spice parameters $V_{TO} = 1V$, $KP/2 = 2 \times 10^{-5} A/V^2$, $W=L$, $LAMBDA = \lambda = 0$, $GAMMA = \gamma = 0.1$, $2PHI_f = 2\phi_f = 0.6$ (the latter two for V_{th})



- Give the connection of the bulk terminal, B, to insure that $V_{th} = V_{TO}$.
- Using that bulk connection set up the differential equation for the capacitor voltage, v_o , for $t > 0$, first symbolically using all the Spice parameters and then numerically using the above values of the Spice parameters.
- Give the final value of the output voltage, v_o at $t = \infty$.
- Discuss what changes with the other two possible connections of the bulk terminal.