


303H Fall 2015 – Homework 1 Due Th 09/10/15

The PARAM part is in the SPECIAL library and Dbreak is in the BREAKOUT library

1. (60 points, Diode bias & Spice transient analysis)

Set up the following circuit in Spice. Then do a DC run on  $V_{in}$  (about 0 to 3V) along with a Parametric run to find  $R_L$  to give a diode current of 1mA.

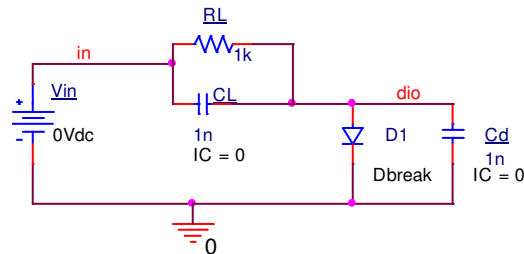- a) Record 1) the resistance  $R_d$  of the resistor  $R_L$  for the diode current to be 1mA, 2) the diode voltage,  $V_{dio}$ , at this diode current Q point, 3) the value of  $V_{in}$  for this Q point and 4) the conductance (slope),  $g_d$ , of the diode current vs diode voltage at this Q point.



- b) Change the model for the diode via Edit PSpice Model using the model for the 1N4007 from the course web page and repeat part a). Comment on any differences.
- c) Make  $R_L = R_d$ , the value found for the above Q point. Set up the small signal differential equation when the initial value of the capacitor  $C_d$  is 1mV greater than the Q point voltage. Do a transient analysis for about 50uSec in PSpice with that capacitor IC value. Submit your transient analysis curves of anode voltage and diode current.

2. (40 points, RLC circuits)

- a) Show that with the Spice G component one can obtain a negative resistance. Draw the resulting circuit, including a ground on both sides of the G component, and give the value of the negative resistance.

