

303H Fall 2015 – Homework 2 Due Th 09/17/15


1. (50 points, Q points and load lines)

The following circuit has the 1-port diode described by the piecewise linear curve shown



- Assume $E > V_0 > 0$ and $R > 0$. Give a range of R to the Q point is in the positive slope region; repeat for the Q point in the constant current $= I_0$ region. Draw separate graphs for typical load lines on the diode curve for each of the two cases.
- Give the small signal conductance in the above two regions. Explain what happens if Q is at the two break points, $v_D = 0$ & V_0 .
- Next assume that $E < 0$ and $R < 0$. Pictorially with three different graphs show that there are one, two or three (that is, multivalued) Q points and discuss what you think this means.
- As the diode characteristic is piece-wise linear it can be written in one formula as a sum of unit-step functions with coefficients. Obtain such a representation.

2. (50 points, Spice G and load line)

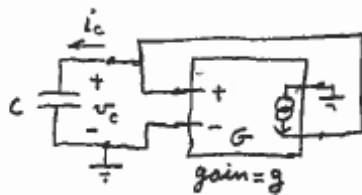

- Set up the differential equation for the above circuit which uses the G ($=VCCS$) component of Spice. Solve the differential equation for $t > 0$ when the capacitor initial condition is $v_C(0) > 0$ and again when $v_C(0) < 0$. Assume that $C > 0$ and $g > 0$. But note even though the G component gain may be positive its input resistance can be negative. G components can though have negative gains,
- Chose some reasonable values and run Spice for this circuit submitting your results.