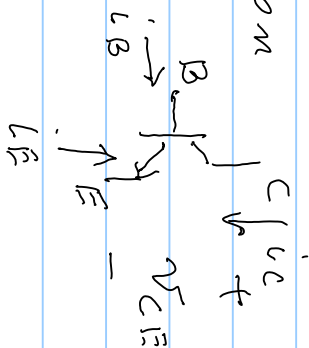


EE303H
09/10/15

mpm



$$i_B + i_C + i_E = 0 \quad \text{KCL}$$



$$i_B = -i_C - i_E = -i_C + \frac{1}{\alpha} i_C$$

Law of mpm $i_C = -\alpha i_E$

$$i_E = -\frac{1}{\alpha} i_C$$






$$i_C = \frac{\alpha}{1-\alpha} i_B$$
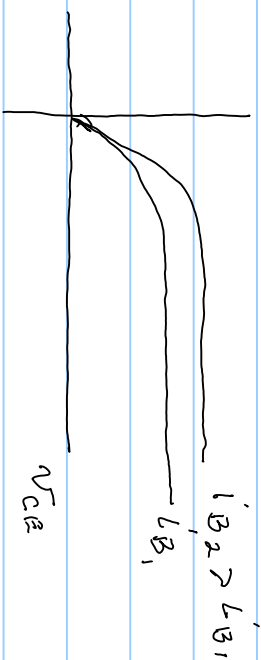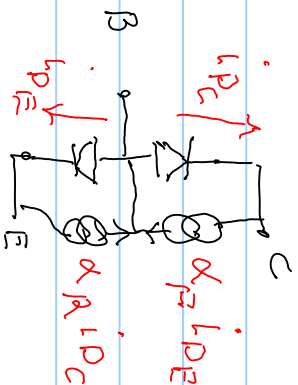
$$\beta = \frac{\alpha}{1-\alpha} \approx 50 - 500$$




if $\beta = 100, i_B = 10^{-6}, i_C = 10^{-4} = 0.1 \text{ mA}$

NPN

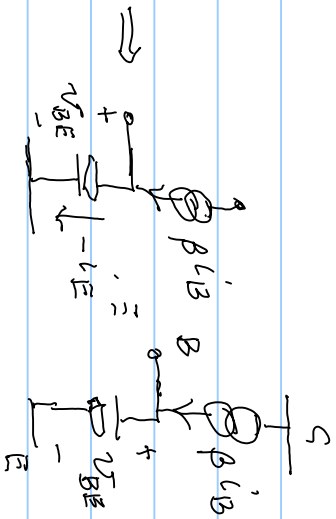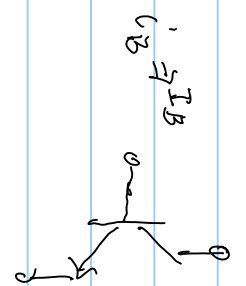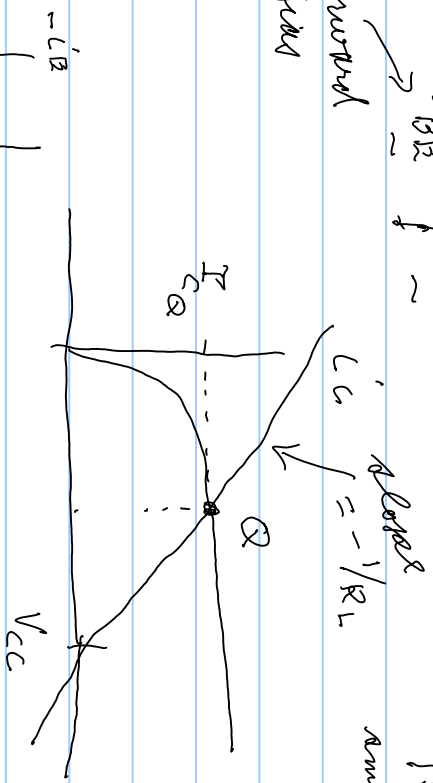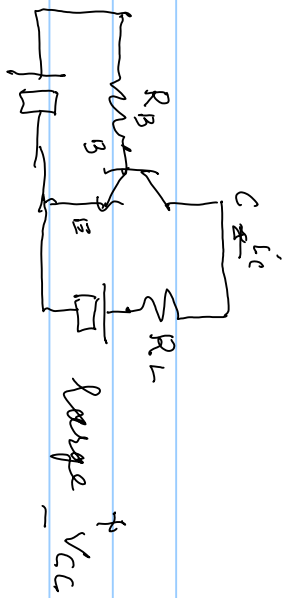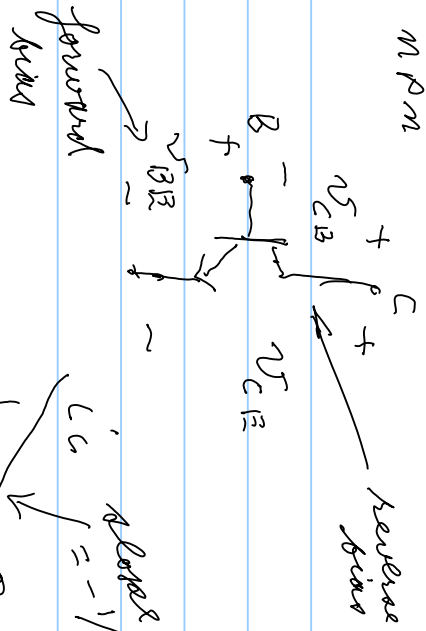

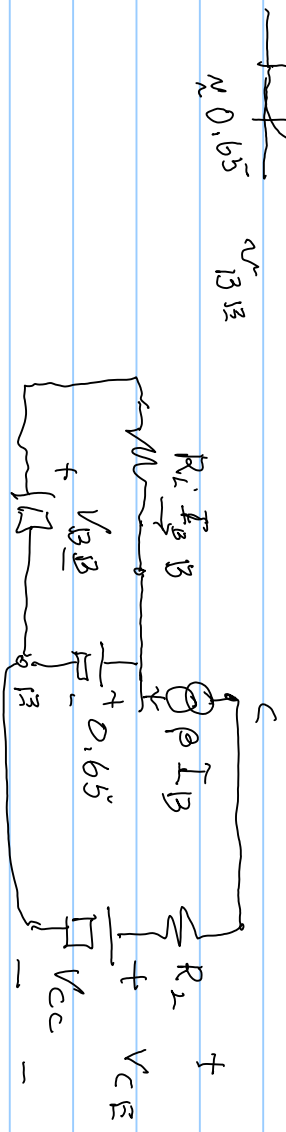for bias
 $i_B \rightarrow I_B$
 $V_{BE} \rightarrow V_{B1}$



KVL B-E $V_{BE} = R_i I_B + 0.65 \Rightarrow I_B = \frac{V_{BE} - 0.65}{R_i}$ } across the base

Ex: $V_{BE} = 1.65 \Rightarrow I_B = 1/R_i$ if $I_B \approx 1 \times 10^{-6}$, $R_i = 1 \text{ Meg } \Omega$

Bias at the collector: β given; βI_B is known; $\beta I_B = I_C$

KVL $V_{CE} = -R_L I_C + V_{CC}$



know V_{CE} as a function, say

$V_{CE} = 6V, -R_L \beta I_B$


know $V_{CE} \Rightarrow \frac{V_{CE} - V_{CE}}{\beta I_B} = R_L = \frac{6-3}{\beta \times 10^{-6}} = \frac{3}{10^{-4}} = 0.3 \times 10^3 \Rightarrow 300 \Omega_m$

$\beta = 100$



$I_C = 0.1 \text{ mA}$

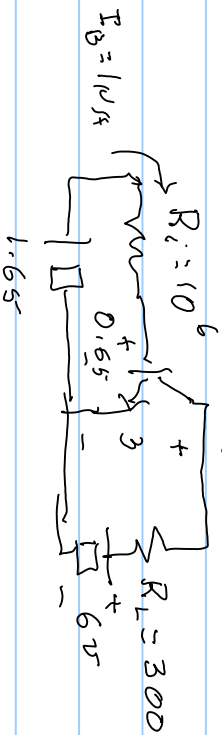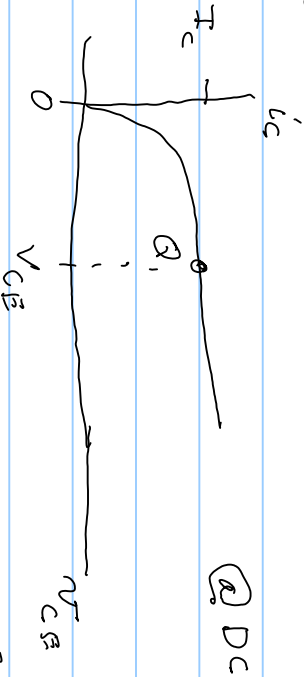

Signal gain

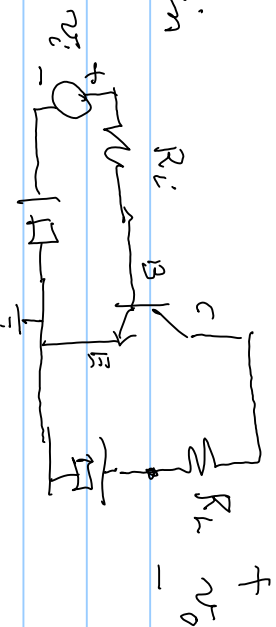

Small signal
equivalent
circuit

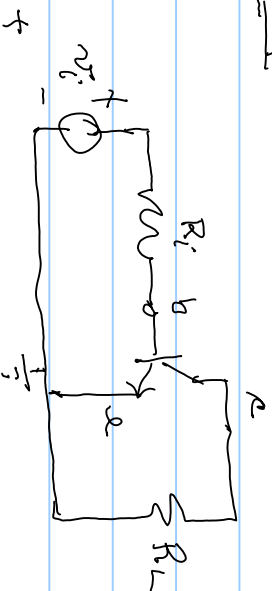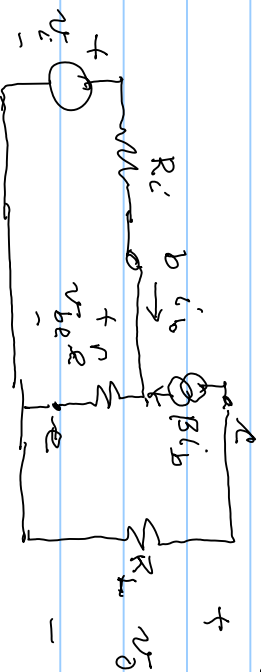




$$r_e = \frac{1}{g_m} = \frac{V_T}{I_E}$$

$$v_o = -\beta i_b \cdot R_L \quad ; \quad v_{be} = V_E \cdot (r_{\pi} + \beta r_e) = V_E \cdot (-r_e)$$

$$v_o = R_L i_b + v_{be} \approx [R_L + V_E (1 + \beta)] i_b \Rightarrow i_b = \frac{v_i}{R_L + (1 + \beta) r_e}$$

$$v_D = - \frac{\beta R_L}{R_L + (1+\beta)R_E} v_i \implies \frac{v_D}{v_i} = - \frac{\beta}{R_L + (1+\beta)R_E} \cdot R_L \approx - \frac{\beta R_L}{R_L}$$

MOS Transistors = metal oxide silicon

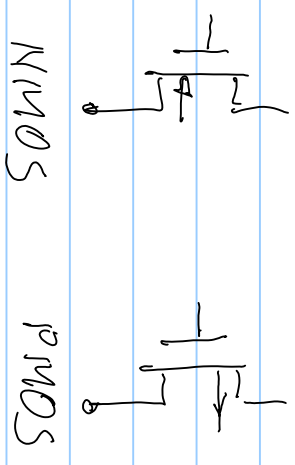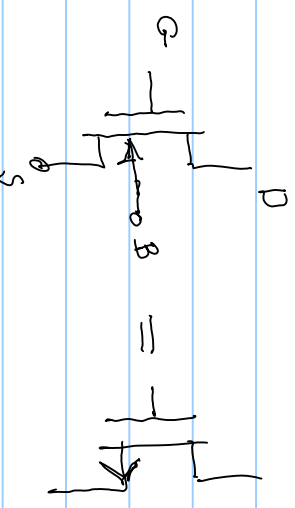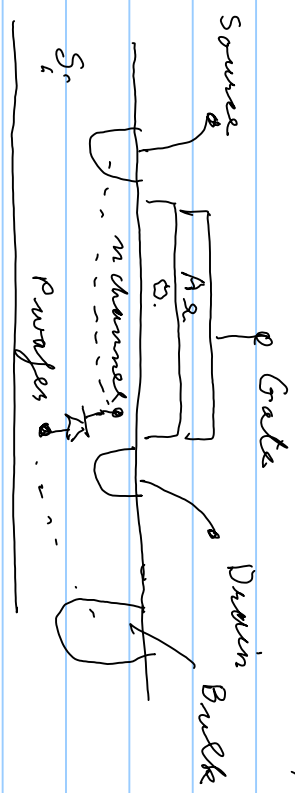

NMOS

PMOS

