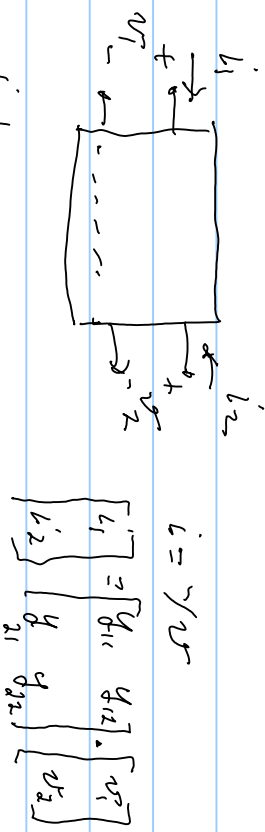


EE 303H

09/17/15


TI EZ 430 - Character Development Tool

Y matrix linear operation 2 -port $Y \Rightarrow$





$$i'_1 = y_{11} v'_1 + y_{12} v'_2 \Rightarrow y_{11} = \frac{i'_1}{v'_1} \Big|_{v'_2=0}$$

$$y_{12} = \frac{i'_1}{v'_2} \Big|_{v'_1=0} = y_{21}$$

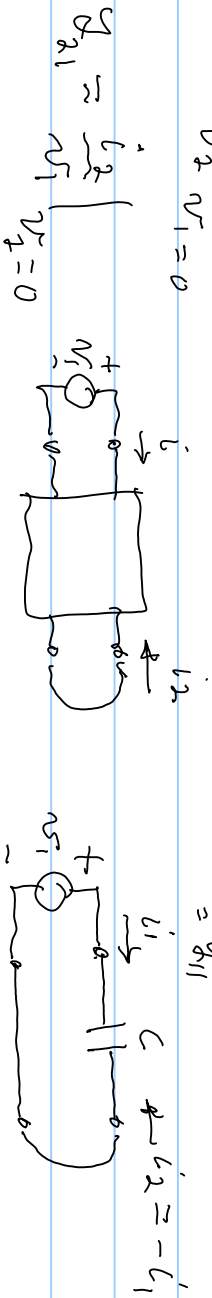
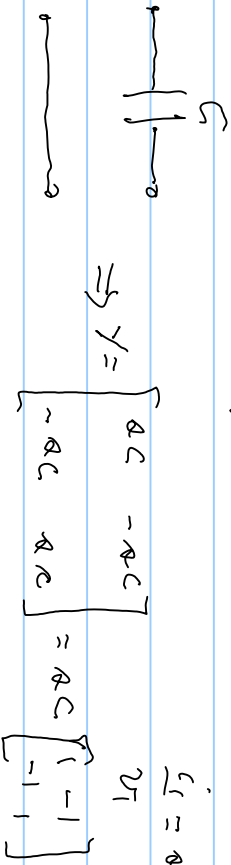
$$\frac{i'_1}{v'_1} = AC = -\frac{i'_2}{v'_2} \Rightarrow \frac{i'_2}{v'_2} = -AC$$



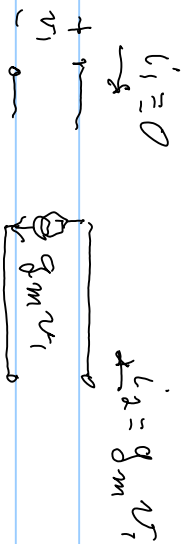


$$Y = \begin{bmatrix} 0 & 0 \\ g_m & 0 \end{bmatrix}$$



$$Y = \begin{bmatrix} g_1 & 0 \\ 0 & 0 \end{bmatrix}$$


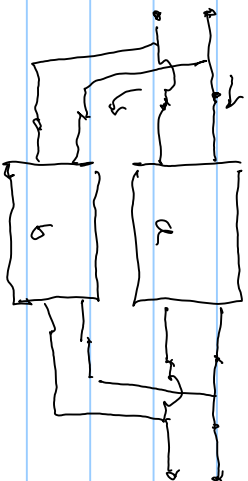
$$Y = \begin{bmatrix} 0 & 0 \\ 0 & g_1 \end{bmatrix}$$



$$i_a = Y_a v_a$$



$$i_b = Y_b v_b$$

$$v_a = v_b = v$$

$$i = i_a + i_b$$

$$i = Y_a v_a + Y_b v_b = (Y_a + Y_b) v \Rightarrow Y = Y_a + Y_b$$


Its equivalent circuit for a BJT

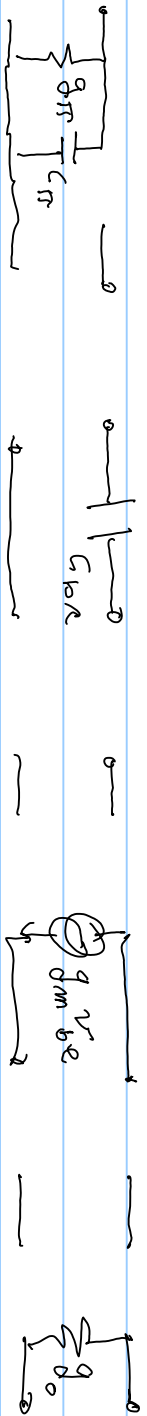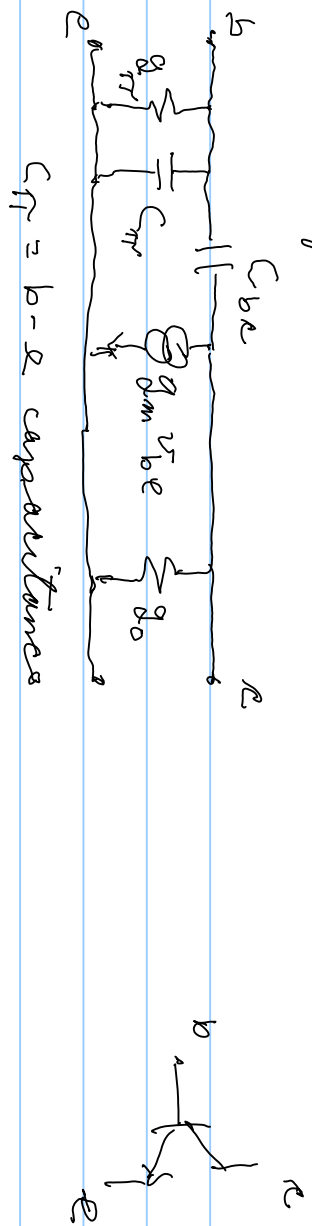

$$Y_{in} = \begin{bmatrix} g_{\pi} + aC_{\pi} + aC_{bc} & -aC_{bc} \\ -aC_{bc} + g_m & aC_{bc} + g_o \end{bmatrix}$$

ideal Y_{in} for the BJT

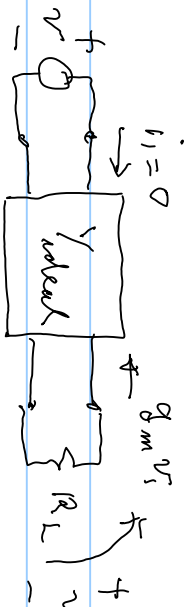
$$Y_{ideal} = \begin{bmatrix} 0 & 0 \\ g_m & 0 \end{bmatrix}$$






$$v_2 \Rightarrow -i_2 = -G_L v_2 = -g_m v_1$$

$$\frac{v_2}{v_1} = -g_m / G_L \approx -g_m R_L = A_v$$

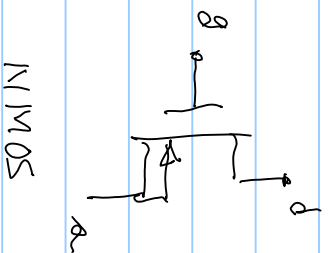
$$V_T = \text{thermal voltage} = \frac{k_B T}{q} \quad ; \quad i_D = I_S \left(e^{v_D/V_T} - 1 \right)$$



NMOS

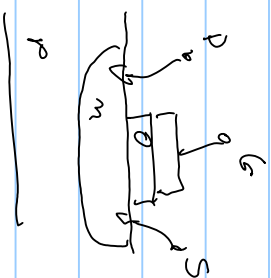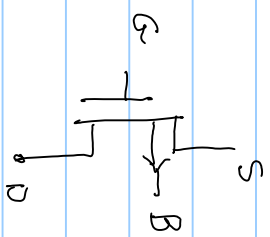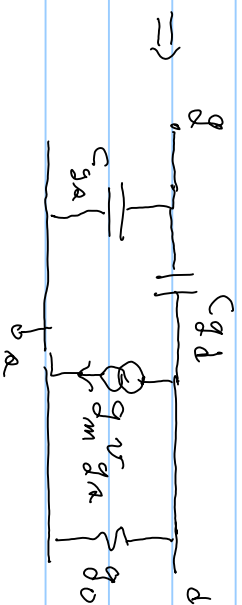

Biasing

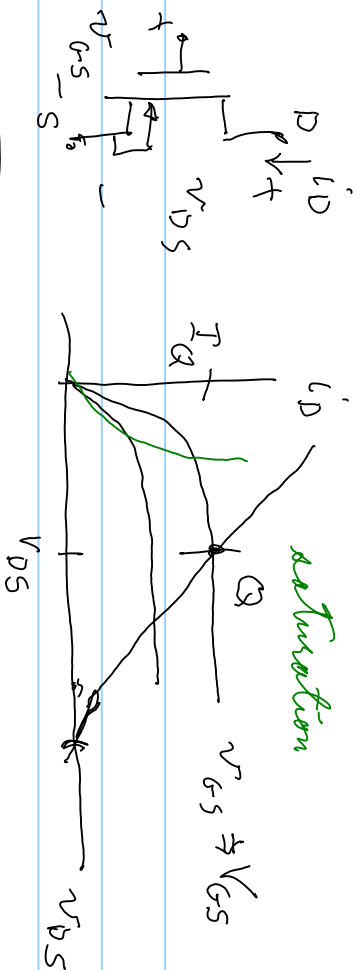

$$V_G = \frac{R_b}{R_a + R_b} \cdot V_{DD}$$

$$V_G = R_S I_D \approx -R_S I_S$$

$$V_{GS} = \frac{R_b}{R_a + R_b} V_{DD} - R_S I_D \approx \frac{1}{1 + \frac{R_b}{R_a}} V_{DD} - R_S I_D$$

Ex: $V_{DD} = 3V$, $I_D = 1mA$, $V_{GS} = V_{T0} \Rightarrow V_{T0} = 1V$

$V_{GS} = 3V$ from curve

Let (choose) $R_S = 100\Omega \Rightarrow R_S I_D = 10^{-1} = 0.1V$

$$\frac{R_b}{R_a + R_b} \cdot 3 - 0.1V = V_{GS} \text{ want fixed } R_b \ll R_a \text{ if } V_{GS} = 3V$$

$$\therefore \text{try } R_G I_D = 1V \Rightarrow R_G = 1/10^{-3} = 1k\Omega$$

$$\frac{R_b}{R_a + R_b} \cdot 3 - 1 = 3 = V_{GS} \Rightarrow \frac{1}{1 + \frac{R_a}{R_b}} = \frac{4}{3} \Rightarrow \text{need a bigger } R_b$$

$$\text{try } V_{DD} = 6V \Rightarrow \frac{6}{1 + \frac{R_a}{R_b}} - 1 = 3 \Rightarrow \frac{4}{6} = \frac{1}{1 + \frac{R_a}{R_b}} \Rightarrow 1 + \frac{R_a}{R_b} = \frac{6}{4} = \frac{3}{2}$$

$$\frac{R_a}{R_b} = \frac{1}{2} \Rightarrow \text{choose large } R_b = 10M\Omega$$

$$R_a = 5M\Omega$$

Need g_m (in saturation)

$$I_D = \frac{K_P}{2} \cdot \frac{W}{L} (V_{GS} - V_{T0})^2 \quad ; \quad g_m = \frac{\partial I_D}{\partial V_{GS}} = 2 \cdot \left(\frac{K_P W}{2L} \right) \cdot \frac{(V_{GS} - V_{T0})}{2} = 2 \frac{I_D}{(V_{GS} - V_{T0})}$$

$$\Rightarrow \rho_m \approx \frac{24 \cdot 10^{-3}}{(3-1)} \approx 10^{-3} \text{ .}$$