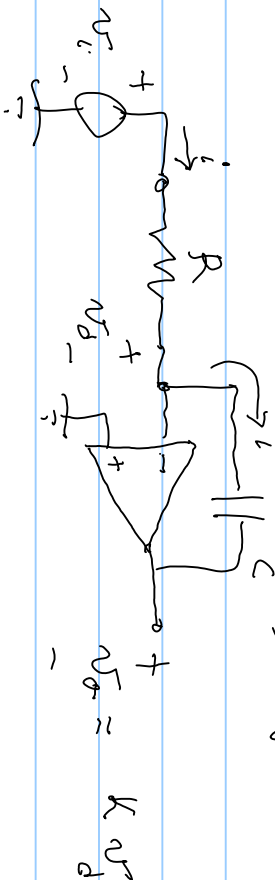


EE 3034

10/6/13

OTA = operational transconductance amplifier }  $\lim_{\omega \rightarrow 0}$

op-amp has  $v_{in}$  &  $v_{out}$ , large  $A_v$







$$i = G(v_i - v_d) = K_C(v_d - v_o) \Rightarrow v_i = v_d + \frac{RC}{G}v_d - \frac{RC}{G}v_o$$

$$(1 + \alpha RC)v_d = v_i + \alpha RC v_o \Rightarrow v_o = K \frac{v_i + \alpha RC v_o}{1 + \alpha RC}$$


$$(1 + \alpha RC)v_o - K\alpha RC v_o = K v_i$$

$$\frac{v_o}{v_i} = A_v = \frac{K}{-K\alpha RC + (1 + \alpha RC)}$$
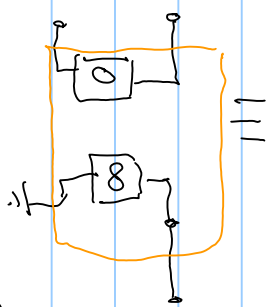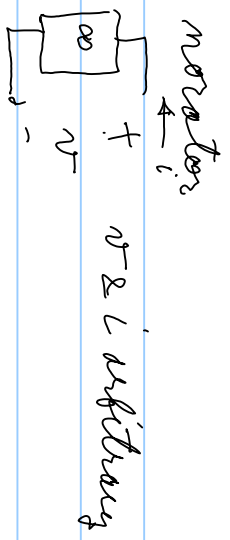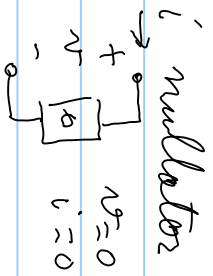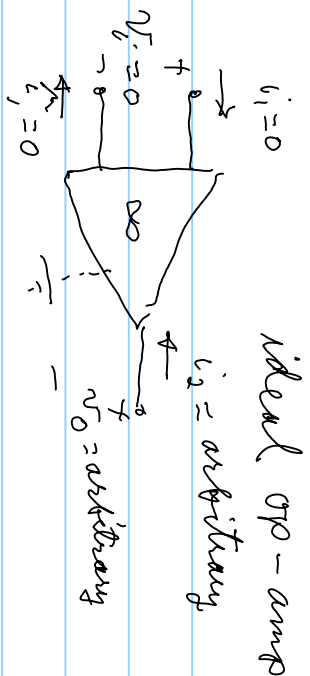
$$\text{if } K \rightarrow \infty \Rightarrow \frac{K}{\alpha RC} \approx -\frac{1}{\alpha RC} = A_v \Rightarrow \text{integrator}$$



Roaltung  $1/x$

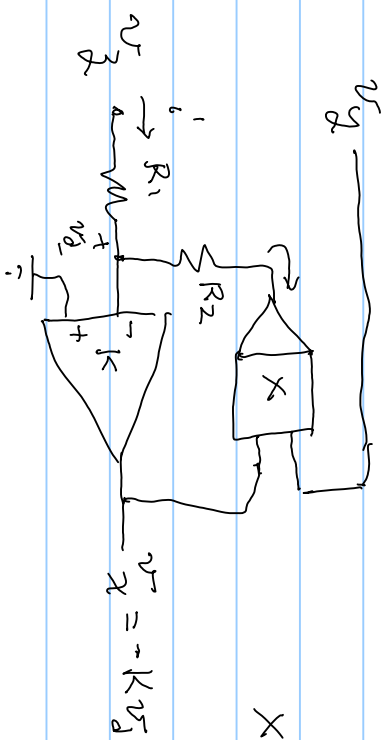

$X \Rightarrow v_{out} = k \cdot v_y \cdot v_x$

$$i = G_1 (v_d - v_g) = G_2 (v_d - k v_y v_x) \Rightarrow (G_1 - G_2) v_d = G_1 v_g - G_2 k v_y v_x$$


$$v_3 = G_1 v_2 - G_2 k v_4 (-k v_3) \Rightarrow (1 - k k G_2 v_4) v_3 = G_1 v_2$$

$$v_x = \frac{-k G_1}{1 - k k G_2 v_4} \cdot v_3 \quad k \rightarrow \infty \Rightarrow v_x = \frac{G_1}{k G_2} \cdot \frac{v_3}{v_4}$$

gives an output  $v_x$  which directly an input  $v_3$  by the  $v_4$

if connect  $v_4 = v_x$

$$v_x^2 = \frac{G_1}{k G_2} \cdot v_3$$

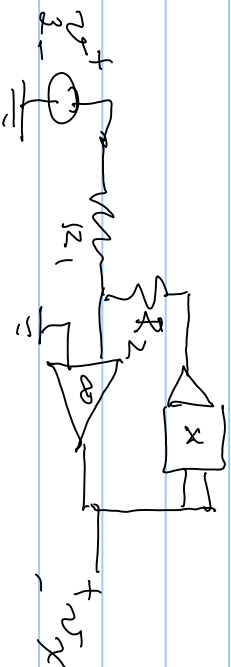

$$\Rightarrow v_x = \pm \sqrt{\frac{G_1}{k G_2} v_3}$$


assume  $v_3 > 0$  if  $k > 0$   
or  $v_3 < 0$  if  $k < 0$

(becomes unstable if  $v_3/k < 0$ )

MDS op amps Ed6 Chap. 8.6.1 p. 652 also see. 12.1 p. 967

Ed7 Chap. 7.6, p. 660 " " 13.1.1 p. 997

circuit for MOS op-amp

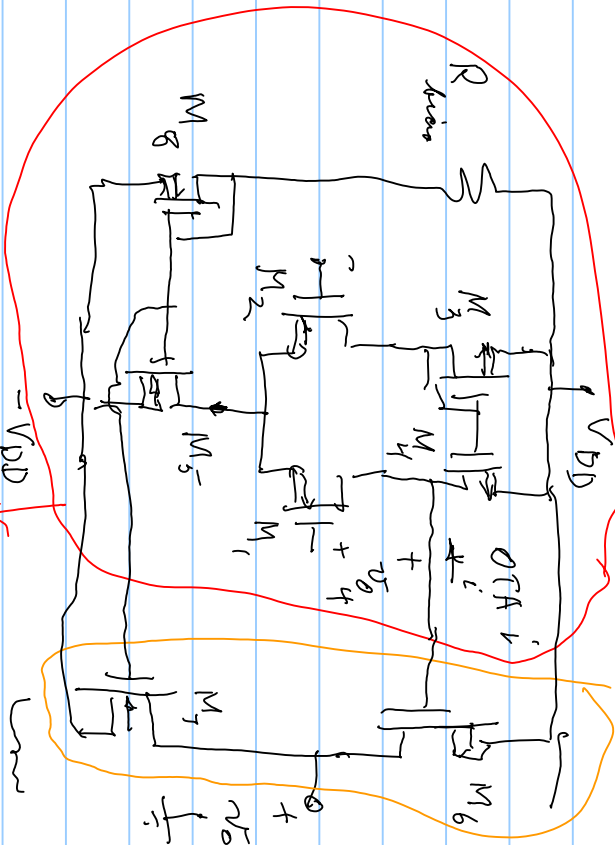

$$A_{v1} = -g_{m1} \times (r_{o3} \parallel r_{o1})$$


$$A_{v2} = -g_{m6} \times (r_{o6} \parallel r_{o1})$$

$$A_{v3} = -g_{m3} \times (r_{o3} \parallel r_{o1})$$




$$A_{v\sigma} = \frac{v_{o\sigma}}{v_i} = \frac{v_{o\sigma}}{v_{o4}} \times \frac{v_{o4}}{v_i} = g_{m1} g_{m6} (r_{o3} \parallel r_{o1}) (r_{o6} \parallel r_{o1})$$

$A_{v\sigma} \quad \parallel \quad A_{v2} \quad \parallel \quad A_{v1}$

MOS

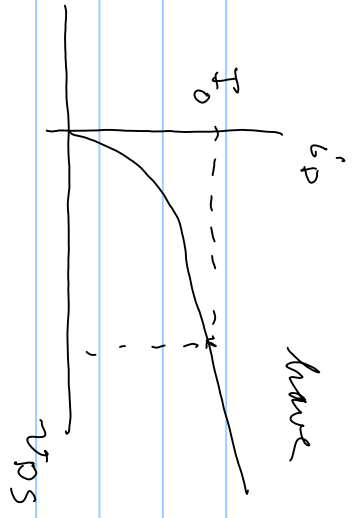


current

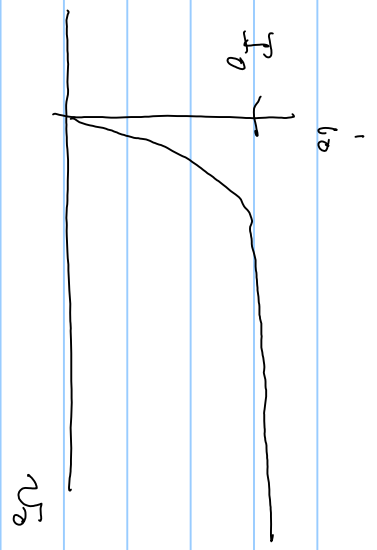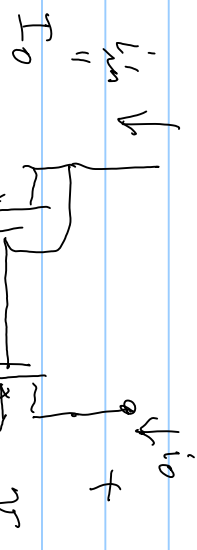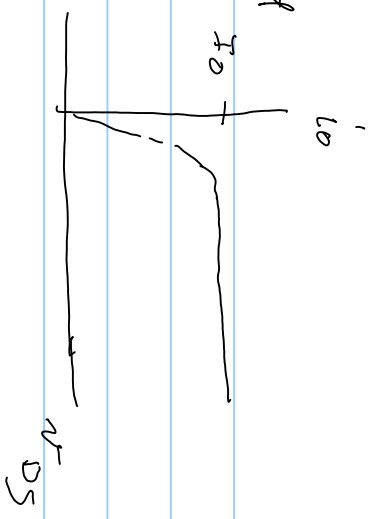

$-V_{DD}$

current

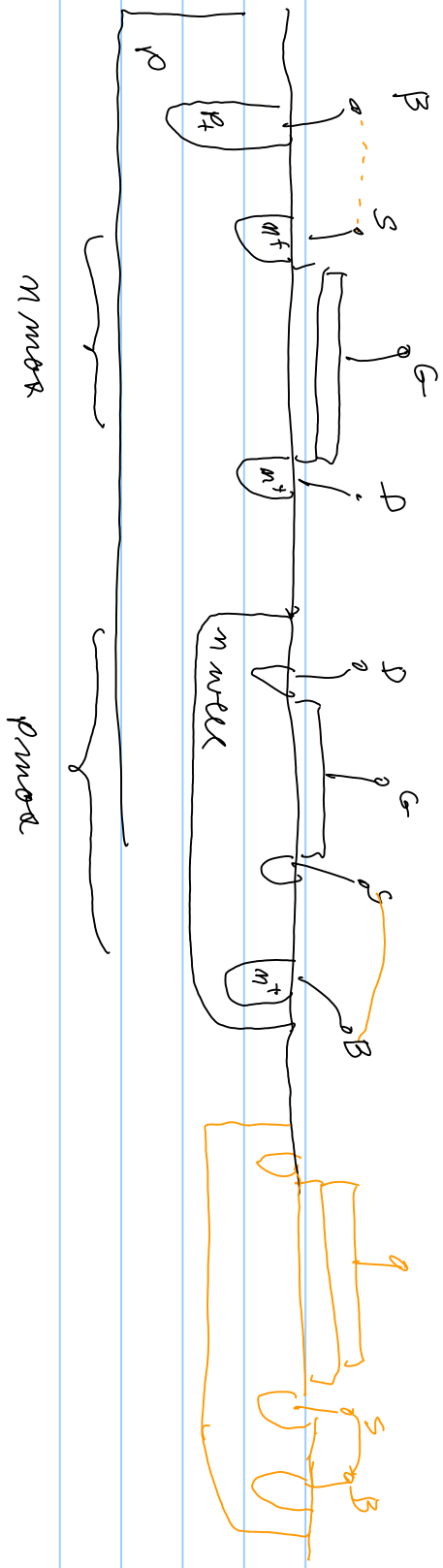

all below the  
room (= the  
windows)