
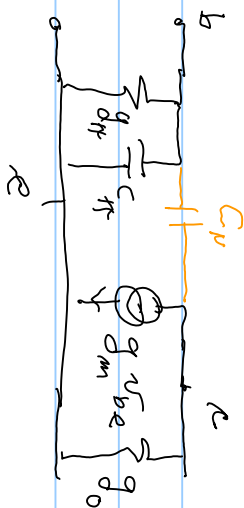
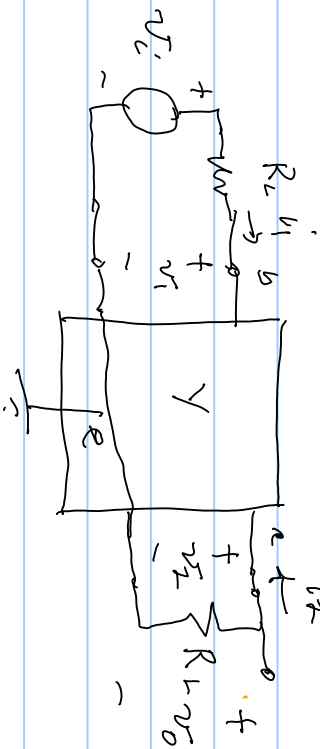


TI RZ 430 look up on web (waterfall)


AC frequency response

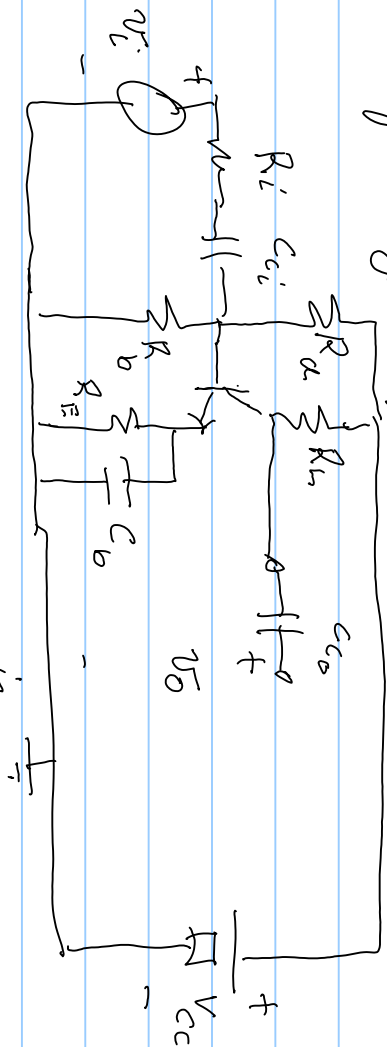

$$Z_c = \frac{1}{sC_c} \quad \left| = \frac{1}{j\omega} \right.$$

$$|Z_c(j\omega)| = \frac{1}{|\omega|} \rightarrow \begin{matrix} \text{out} \\ \omega \rightarrow \infty \\ \omega \rightarrow 0 \end{matrix}$$

DC bias

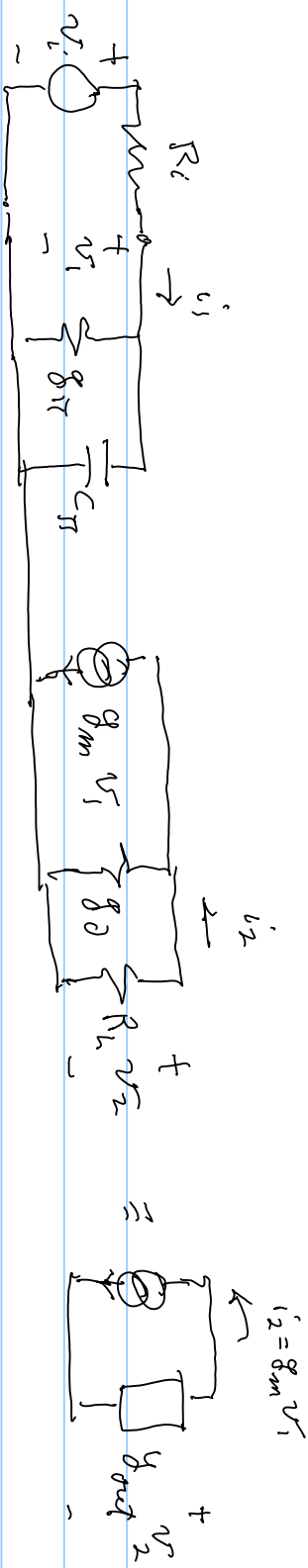

$$v_1 = v_i \times \frac{1}{g_{\pi} + \frac{1}{R_i + g_{\pi} R_e}} \quad g_{\pi} = g_{\pi} + \omega C_{\pi}$$


$$\approx v_i \cdot \frac{1}{1 + R_i g_{\pi}} \Rightarrow g_m v_1 = \frac{g_m}{1 + R_i g_{\pi}} v_i$$

$$v_2 = [-g_m v_1] \times \frac{1}{g_o + G_L} = \frac{-g_m}{1 + R_i (g_{\pi} + \omega C_{\pi})} \cdot \frac{R_L}{g_o R_L + 1} \quad ; R_L = \frac{R_L}{1 + R_L g_o}$$


$$\frac{v_{out}(\omega)}{v_{in}} = \frac{-g_m R_L'}{R_i C_{\pi} \omega + 1 + R_i g_{\pi}} = \frac{-g_m R_L' / (R_i C_{\pi})}{\omega} \quad ; \quad \omega = \sigma + j\omega$$

Phase is @  $\omega_p = - \left( \frac{1 + R_i g_{\pi}}{R_i C_{\pi}} \right)$

$$A_{v}(s) = \frac{v_{out}(s)}{v_{in}(s)} \Big|_{\omega = j\omega} = \frac{-A}{\omega - \omega_p}$$

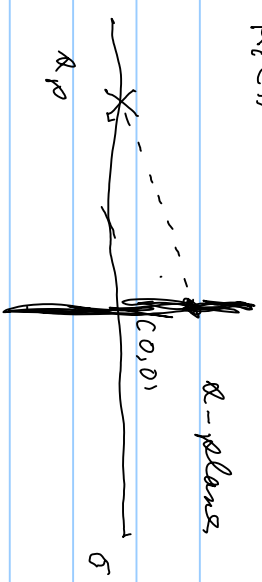

$$|A_{VF}(j\omega)| = \frac{|A|}{|j\omega - \omega_p|} = \frac{A}{\sqrt{(\omega - \omega_p)^2 + \omega^2}}$$

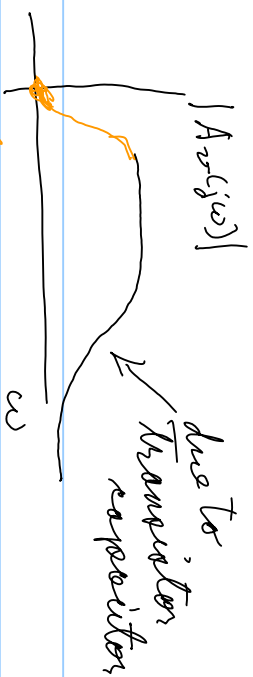


if include  $C_p$   
then get

$$A_{VF}(s) = \frac{aR + b}{s^2 + \frac{\omega_0}{Q}s + \omega_0^2}$$

use  $V_1 = AC$  course for  
approx

do more general case

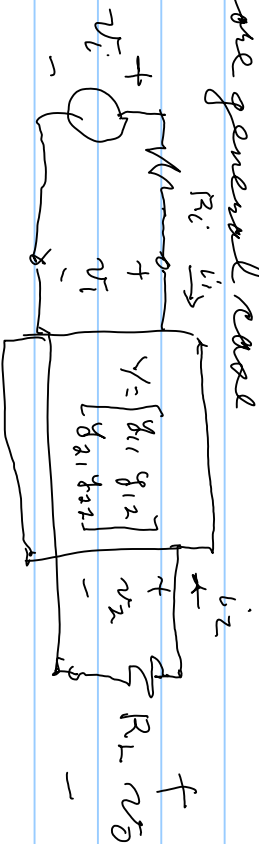

$$I_1 = g_{11} V_1 + g_{12} V_2 = G_i (V_1 - V_2) \Rightarrow V_1 = f(V_2, V_1)$$

$$I_2 = g_{21} V_1 + g_{22} V_2 = -G_L V_2 \quad \leftarrow$$

gives  $V_2$  vs  $V_1$

$$V_1 = R_i I_1 + V_2$$


$$I_1 = G_i (V_1 - V_2)$$

$$V_2 = -R_L I_2 \Rightarrow I_2 = -G_L V_2$$

for degree 2 denominator & degree 0 numerator

$$A_{gs}(s) = \frac{A}{s^2 + \omega_0 s + \omega_0^2}$$

$$|A_{gs}(j\omega)| = \frac{|A|}{d_1(\omega) d_2(\omega)}$$

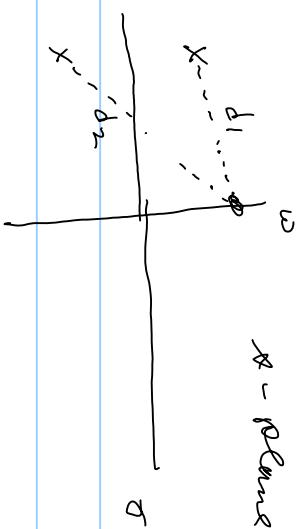


an even function of  $\omega$





$$A_{gs}(s) = H \text{Transfer}(s)$$


$$g(s) = c/s$$

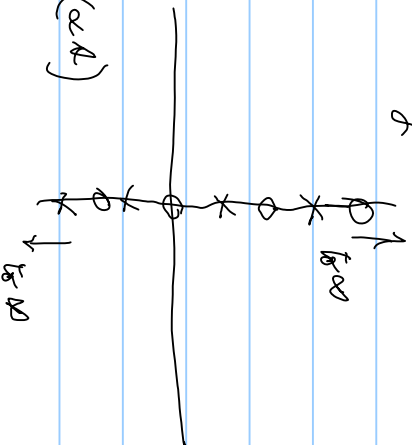Transmission line  $g(s) = g_0 \text{Transfer}(cs)$




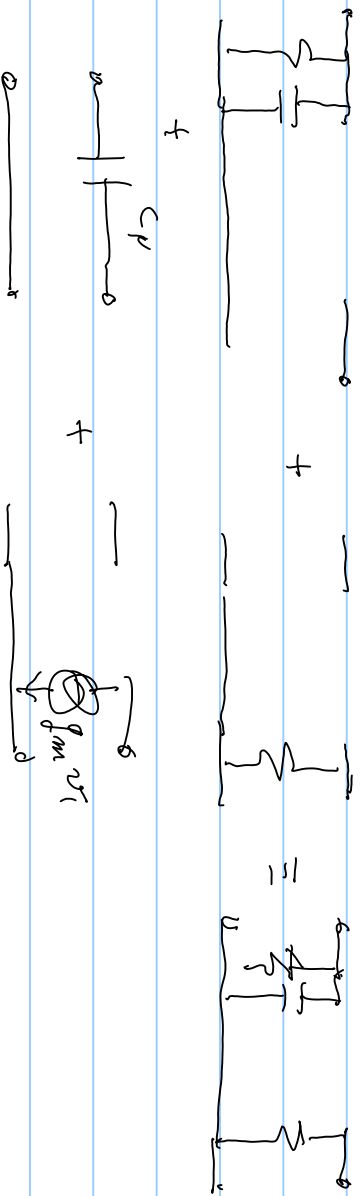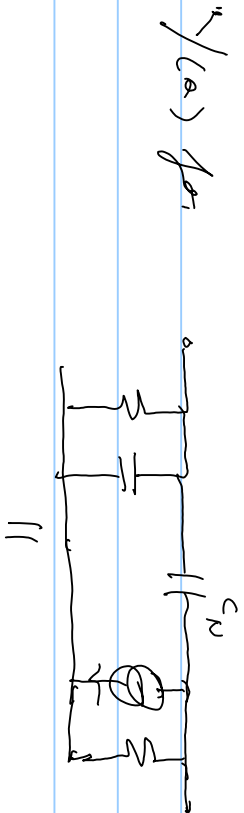
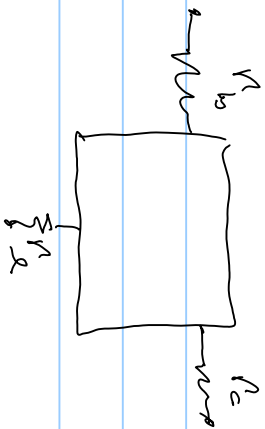
$$Y(\omega) = \begin{bmatrix} g_T + R_{CT} & 0 \\ 0 & 0 \end{bmatrix} + \begin{bmatrix} 0 & 0 \\ 0 & g_0 \end{bmatrix} + \begin{bmatrix} R_{Cp} & -R_{Cp} \\ -R_{Cp} & R_{Cp} \end{bmatrix} + \begin{bmatrix} 0 & 0 \\ g_m & 0 \end{bmatrix}$$



if  $V_2 = 0$

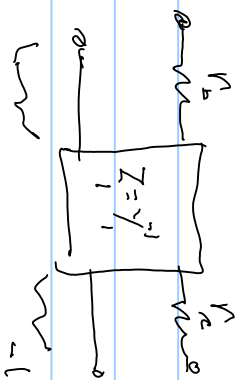

$$\begin{bmatrix} Z_1 + [R_1] & 0 \\ 0 & R_2 \end{bmatrix} = Y \text{ for network circuit}$$