


EECS303H


10/15/15


10/15/2015



Note Title

Para. Transistors = Transmission gates

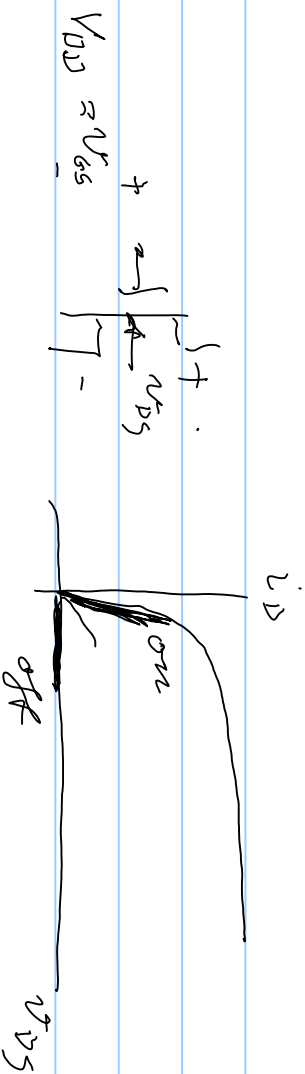



 lowest potential available
 (actually want to connect to the source)

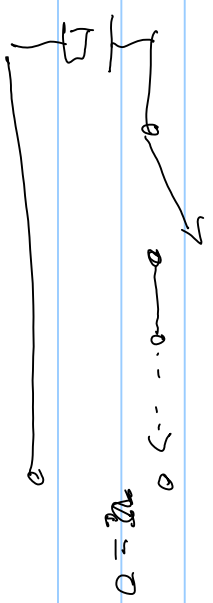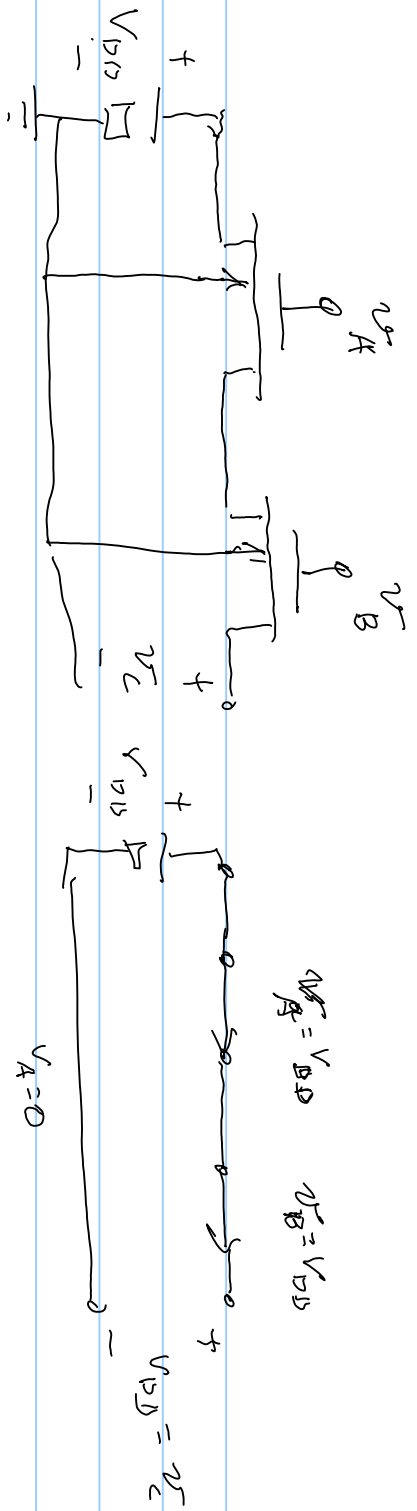
 $v_G \Rightarrow$ large for on = closed
 $v_G =$ small \Rightarrow open





same if $V_B = 0$

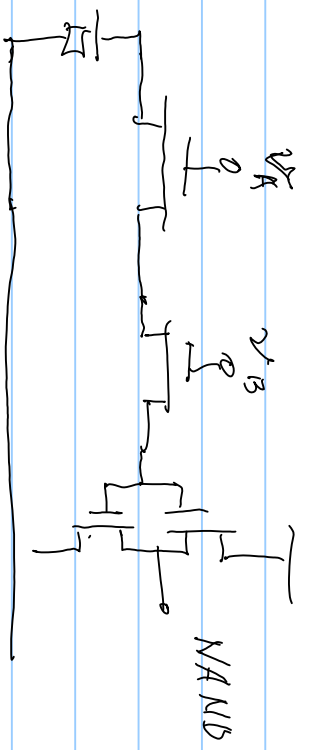

$v_G = v_A > V_{T0}$
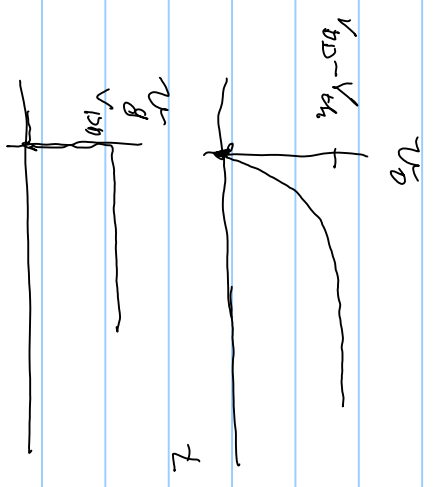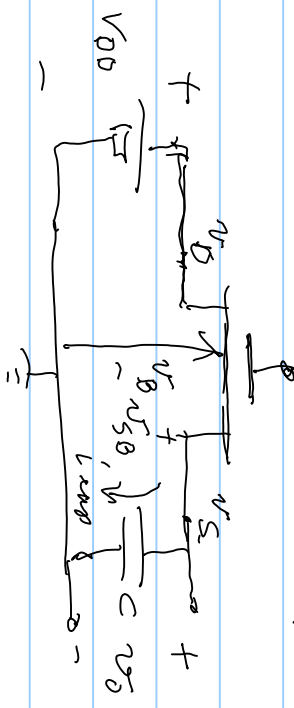
$$v_A = V_{T0} + \beta \left(\sqrt{v_{GS}^2 + Q} - \sqrt{Q} \right)$$



dynamic if $v_{GS} - v_{th} \geq v_{DS}$
 saturated if $v_{GS} - v_{th} \leq v_{DS}$




if $v_G = v_{DD}$ @ $t = 0$ $v_{DS} = v_{DD} - v_D = v_{DD}$
 $v_{DD} - v_{th} \leq v_{DD}$ @ $t = 0 \Rightarrow$ saturation @ $t = 0$

Cap: $C \frac{dv_D}{dt} = i_{cap} = i_D = \frac{K_P}{2} \mu_n (v_{DD} - v_D - V_{T0})^2 \quad (1 + \gamma v_{DS})$
 $\uparrow_{t=0} v_{DD} - v_D$

$$C \frac{dv_D}{dt} - \frac{K_P \mu_n}{2} (v_{DD} - v_D - V_{T0})^2 \approx 0 \quad t \gg 0$$

eventually becomes dynamic \uparrow a recursive eq.


CMOS

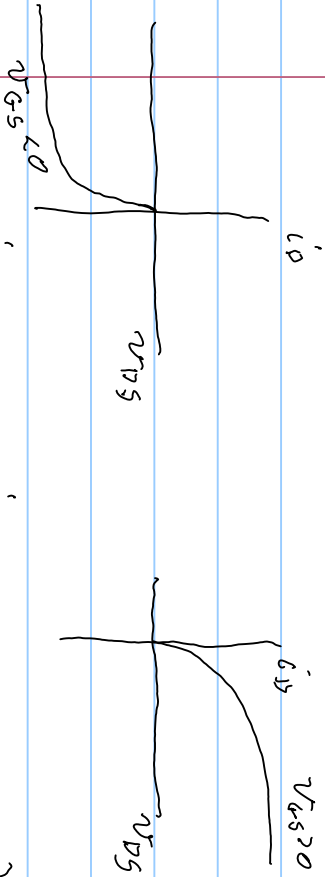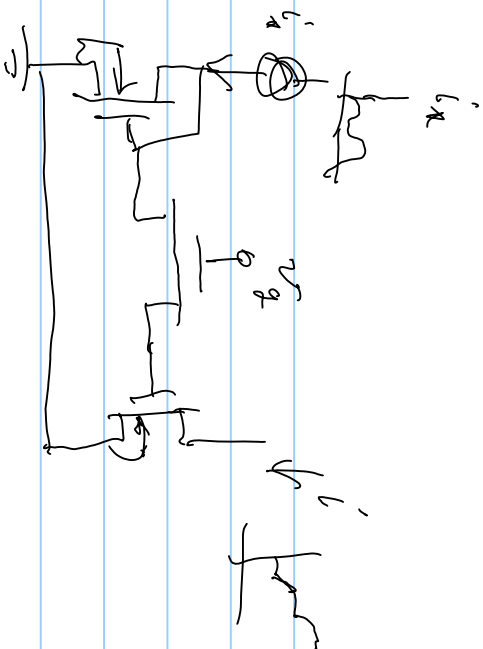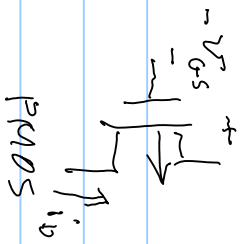


$$i_{D, PMOS} \approx -i_{D, NMOS} \Rightarrow \frac{\partial i_D}{\partial V_{DS}} \Big|_{PMOS} = \frac{\partial (-i_D)}{\partial V_{DS}} \Big|_{NMOS} = \frac{\partial i_D}{\partial V_{DS}} \Big|_{NMOS}$$

complementary

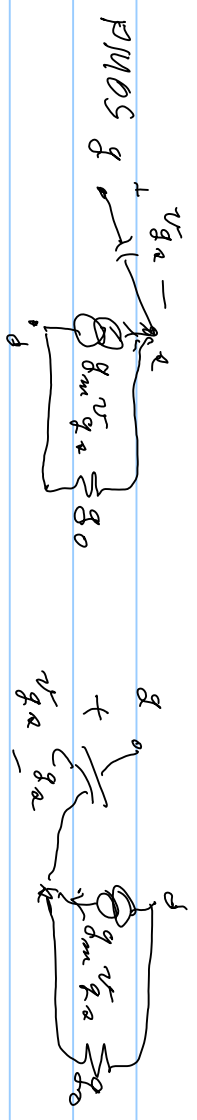\Rightarrow equivalent circuits (small signal) are the same.



Inverter = CMOS

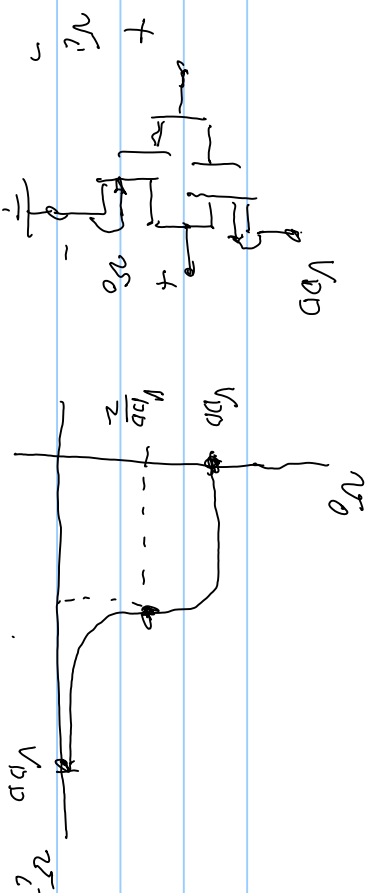

$$-I_{D,P} = I_{D,N} \quad \text{where } v_i = V_{DD}/2 \quad \text{(for PMOS) as in solution}$$

$$\left(\frac{K_P W_P}{2 L_P}\right) (V_{DD} - v_i - |V_{T0P}|)^2 = \left(\frac{K_P W_N}{2 L_N}\right) (v_i - V_{T0N})^2$$

if $\left(\frac{K_P W_P}{2 L_P}\right) = \left(\frac{K_P W_N}{2 L_N}\right)$ then $V_{DD} - v_i = V_{T0N} = v_i - V_{T0N}$ if $V_{T0N} = -V_{T0P}$

$$2v_i = V_{DD} \Rightarrow v_i = V_{DD}/2$$