


Exam next Tr = open book open notes (old exam must)
 current mirrors, differential pairs
 small signal equivalents, gain

ALD = advanced linear devices


NMOS ALD 1101

PMOS ALD 1102

diagrams

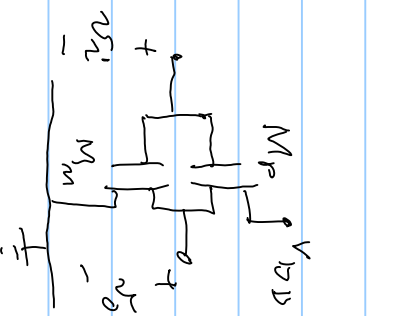


CMOS

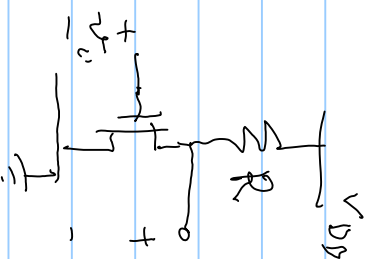

max power


max power when in a given state

is during a transition

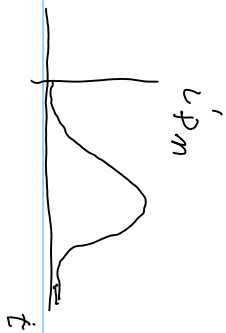


M_n called pull down, M_p is called pull up

1 = V_{DD}, 0 = ground

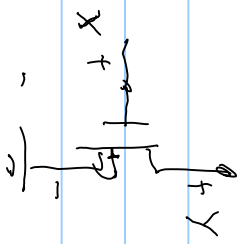

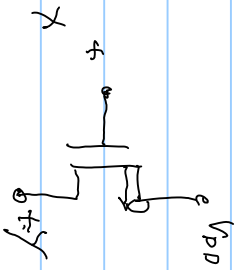$\tilde{Y} = X$ as driving $\bar{\quad}$ = complement




$Y = \bar{X} \Rightarrow \tilde{Y} = X$




if connect $X_n = X_p$, $Y_n = Y_p \Rightarrow Y = \bar{X}$

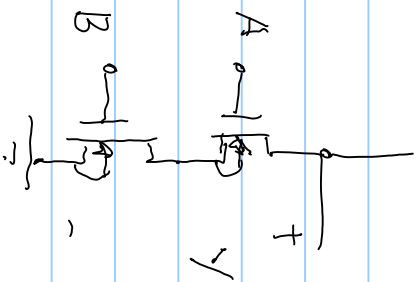For other binary gates, see p. 1112 of Ed. 6



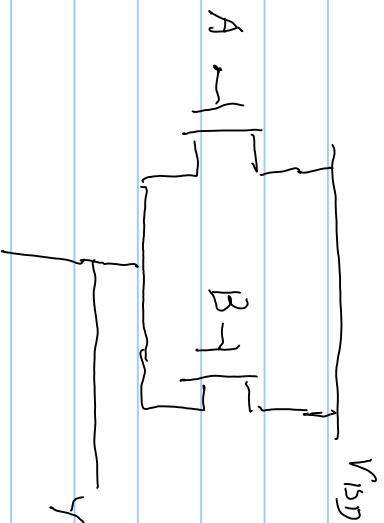$Y = A \cdot B$ $\cdot = \text{and}$, $+ = \text{or}$, $\bar{} = \text{complement}$
a pull down for $Y = A \cdot B$



$Y = A + B \Rightarrow \bar{Y} = \bar{A} \cdot \bar{B}$

pull up

to get a nand $y = \overline{A \cdot B}$ pull down $\Rightarrow Y = \overline{A \cdot B}$ pull up


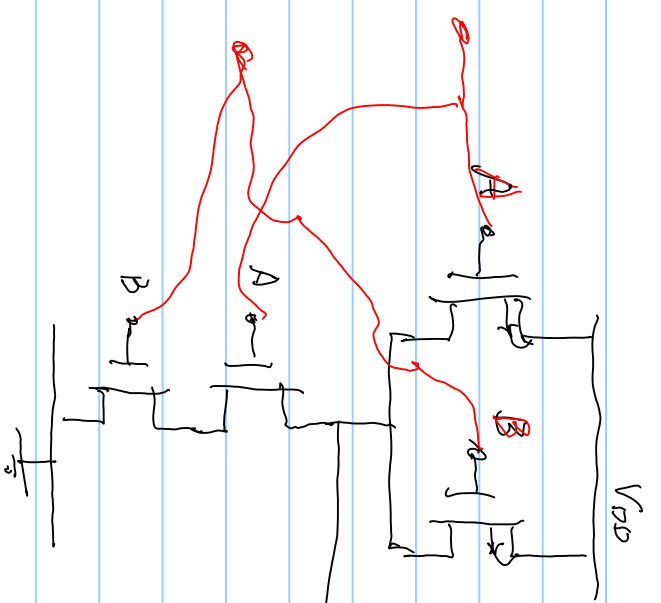
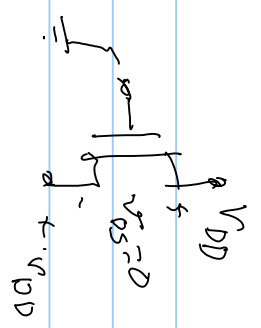



Fig 13.32

a CMOS NAND


$$Y = \overline{A \cdot B}$$

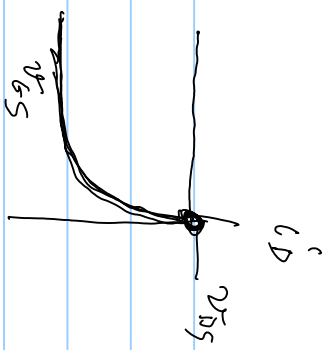

if $v_{GS} = 0$

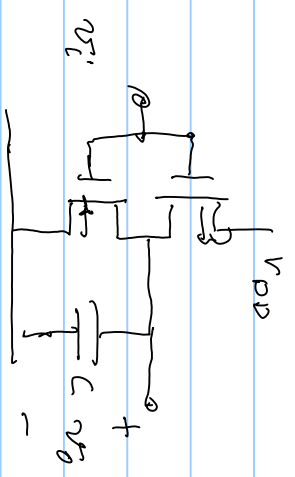


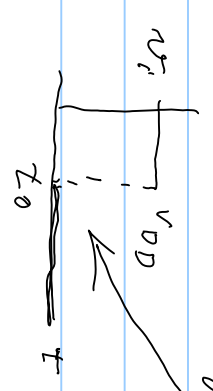$i_D \approx C \frac{dv}{dt}$ if $i_D = \text{constant}$



after t_0 M_n is off so i_D is zero

$v_{DS} = 0$ for $t \geq t_0$

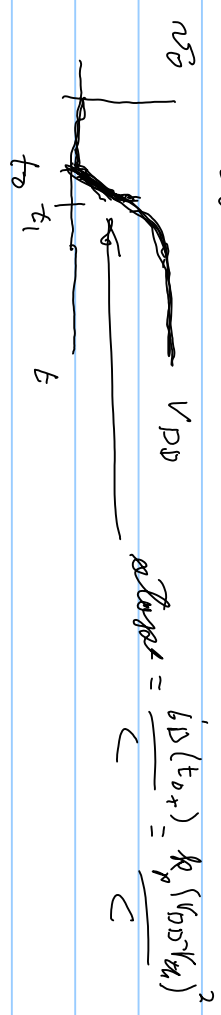

$i_{D(av)} = \frac{i_D(t_{0+}) \cdot R_p(V_{DD} t_{0+})}{C}$

$t_0 =$ initially M_p is in saturation

when M_p changes to ohmic (= triode) then

$$-C_D P' = I_C' = \mu_{KP} (2(V_{DD} - V_{T0}) \cdot V_{SD} - V_{SD}^2) \quad \text{mit } V_{SD} = V_{DD} - V_D(t)$$

$$C \frac{dV_D}{dt} = \mu_{KP} (2(V_{DD} - V_{T0})(V_{DD} - V_D) - (V_{DD} - V_D)^2)$$

$$C \frac{d(V_{DD} - V_D)}{dt} =$$

$$\frac{dV_D}{dt} = -aV_D + bV_D^2$$

$$a = \mu_{KP} \cdot 2(V_{DD} - V_{T0})$$

$$b = \frac{\mu_{KP}}{C}$$

not a single time constant system

$$\frac{dV_D}{aV_D + bV_D^2} = dt \quad \int_{V_D(t_1)}^{V_D(t)} \frac{-dV_D}{V_D(a - bV_D)} = \int_{t_1}^t dV_D = (t - t_1)$$

$$\frac{1}{V_D(a - bV_D)} = \frac{R_1}{V_D} + \frac{R_2}{V_D - a/b} \Rightarrow \text{partial fraction expansion}$$

$$= \frac{1/a}{V_D} + \frac{-1/a}{V_D - a/b} \quad R_1 = \frac{1}{a} \Rightarrow \frac{V_D}{V_D(a - bV_D)} \Big|_{V_D=0} = R_1 + \frac{R_2 V_D}{V_D - a/b} \Big|_{V_D=0}$$

$$\begin{aligned}
 & x(t) \int_{x(t_1)}^{x(t)} \frac{1}{x} dx + \int_{x(t_1)}^{x(t)} \frac{c_2}{x - a/b} dx = \frac{1}{a} \ln \left(\frac{x(t)}{x(t_1)} \right) + c_2 \ln \left(\frac{x(t) - a/b}{x(t_1) - a/b} \right) \\
 & \frac{1}{a} \ln \left(\frac{x(t)}{x(t_1)} \right) + c_2 \ln \left(\frac{x(t) - a/b}{x(t_1) - a/b} \right) \quad t = T, \\
 & x = V_{SD} - v_0
 \end{aligned}$$

allows an analytic solution for changing C from a gate reverse time.