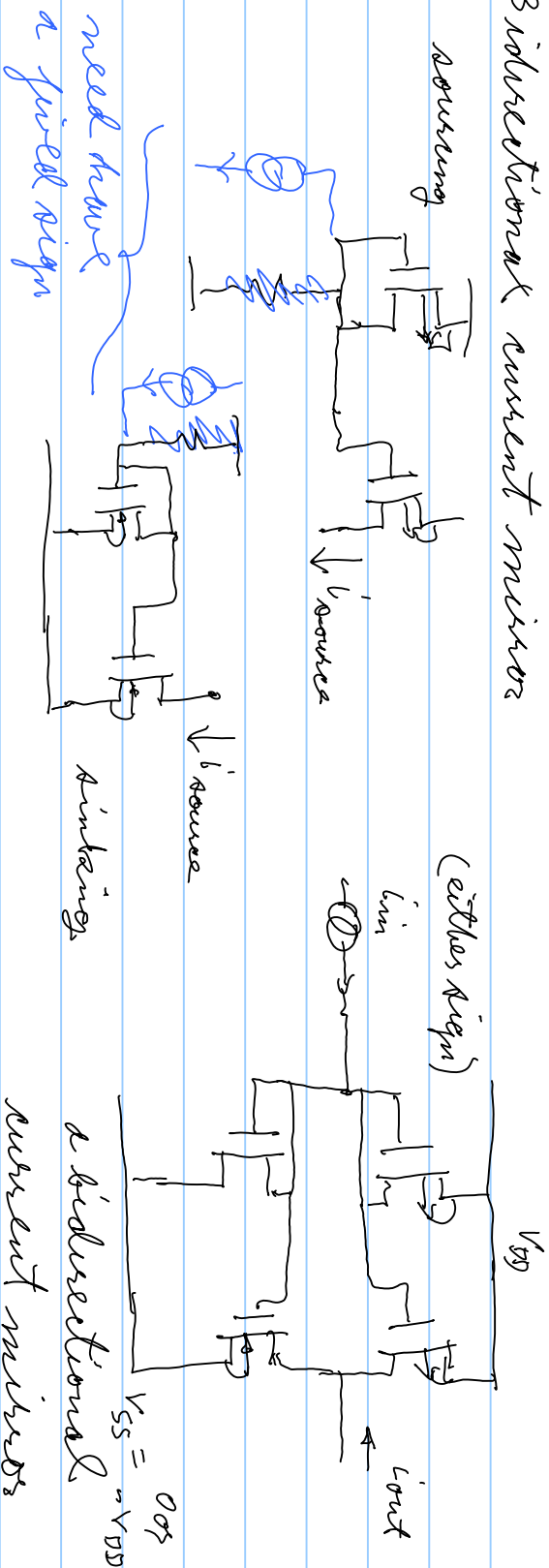


Exam on Th. open book open notes



1. calculating g_m , MOS, BST
2. current sources & current mirrors
3. Transmission gates
4. capacitors load & charging C's

Bidirectional current mirrors




saturation

$$i_D \approx k_n (v_{GS} - V_{th})^2$$

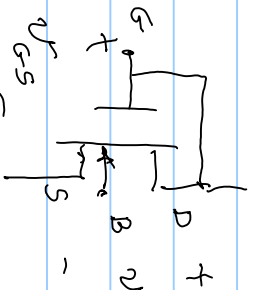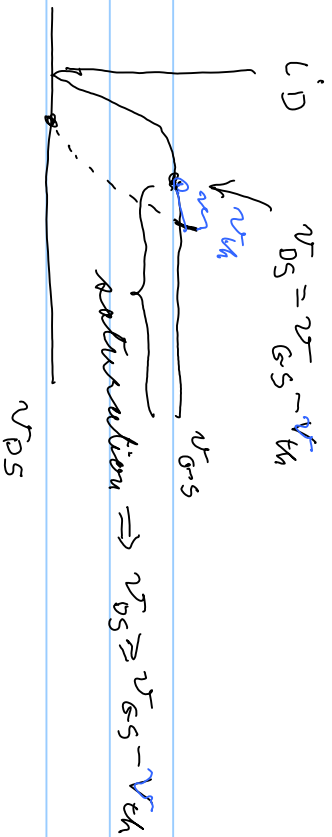


$$v_{GS} = v_{DS} = v \quad v_{DS} = v \quad v_{GS} - V_{th} = v - V_{th}$$
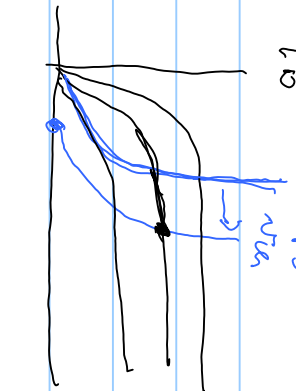
$$i_D \Rightarrow v_{GS} = v_{DS} = v \quad \Rightarrow \text{if } v_{th} > 0$$



$$\frac{k_n \cdot W}{2 \cdot L}$$

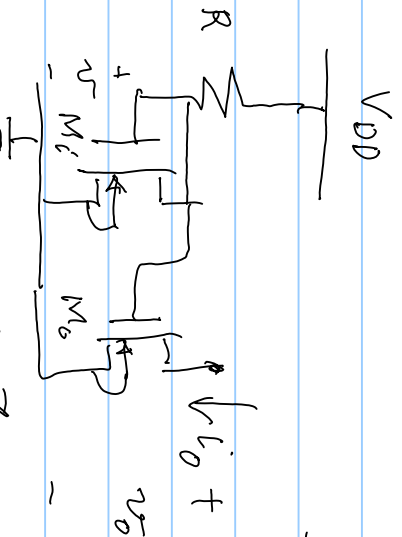

$$v_{GS} = v_{DS} = v \quad v_{GS} = v \quad v_{DS} = v$$


$$i_D = k_n (v_{GS} - V_{th}) v_{DS} = k_n (v - V_{th}) v$$

$$v_{GS} = v_{DS} = v \quad \Rightarrow \text{if } v_{th} > 0$$

needs v_D for part V_D also in saturation

GAMMA

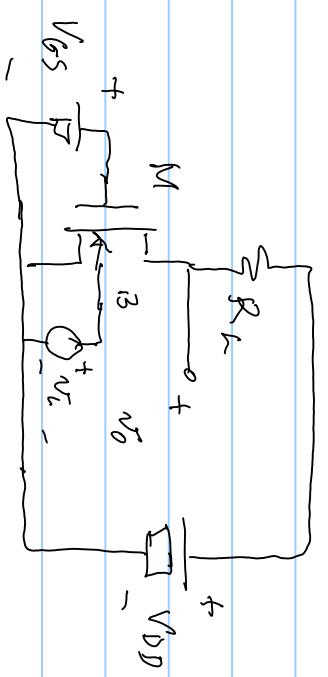We have $V_{th} = V_{TD} + \gamma \left(\sqrt{V_{SB} + 2\phi_s} - \sqrt{2\phi_s} \right)$ body effect
here $V_{SB} + 2\phi_s > 0$ eq. 5.107 GTed




low freq $\frac{v_o}{v_i} \approx -g_m R_L$

$$g_m = \frac{\partial i_D}{\partial v_i} = \frac{\partial i_D}{\partial v_{th}} \cdot \frac{\partial v_{th}}{\partial v_{gs}} \cdot \frac{\partial v_{gs}}{\partial v_i} =$$

assume $V_{BS} = 0$
take @ source potential when $v_i = 0$

assume M is in saturation $i_D = k_n (v_{GS} - V_{th})^2$
 ignore body effect ($\gamma [1 + \lambda V_{DS}]$) $\Rightarrow \frac{\partial i_D}{\partial v_{th}} = 2k_n (v_{GS} - V_{th})(-1)$
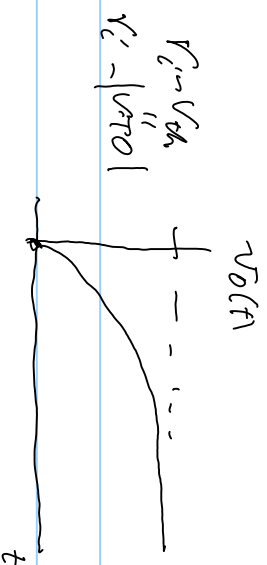
$$\frac{\partial v_{th}}{\partial v_{gs}} = \frac{\gamma \cdot 1/2}{\sqrt{V_{SB} + 2\phi_s}}$$



$$i_c = c \frac{dx}{dt} = c \frac{dv_0}{dt} = i_s = k_p (v_{sg} - |v_{T0}|)^2 = k_p (v_i - v_0 - |v_{T0}|)^2$$

$$x = v_i - |v_{T0}| - v_0 \quad \frac{cd}{dt} (-[v_i - |v_{T0}| - v_0]) = k_p (v_i - v_0 - |v_{T0}|)^2 \Rightarrow -c \frac{dx}{dt} = k_p x^2$$

$$\frac{dx}{x^2} = -\frac{k_p}{c} dt \quad \int \frac{dx}{x^2} = -\int \frac{k_p}{c} dt$$

$$x(t) = v_i - |v_{T0}|$$

$$= -\frac{1}{x} \Big|_{x(t)} = -\frac{k_p}{c} t \Rightarrow \text{can find } v_0(t)$$